
Clocking, clock distribution, and clock management in wireline and wireless subsystems

Mozhgan Mansuri, Intel
mozhgan.mansuri@intel.com

February 14, 2021

Self Introduction


- ❑ B.S. and M.S. degrees from Sharif University of Technology, Iran, in 1995 and 1997
- ❑ Ph.D. degree from University of California, Los Angeles, in 2003
- ❑ “Kavoshgaran Consulting Engineers”, Tehran, Iran (1997-1999)
- ❑ Intel corporation, Hillsboro, OR (2003-present)
- ❑ My interests are in clock synthesis/recovery circuits (PLLs and DLLs), variation-tolerant circuits, optical/electrical and memory I/O links



Bandwidth Growth




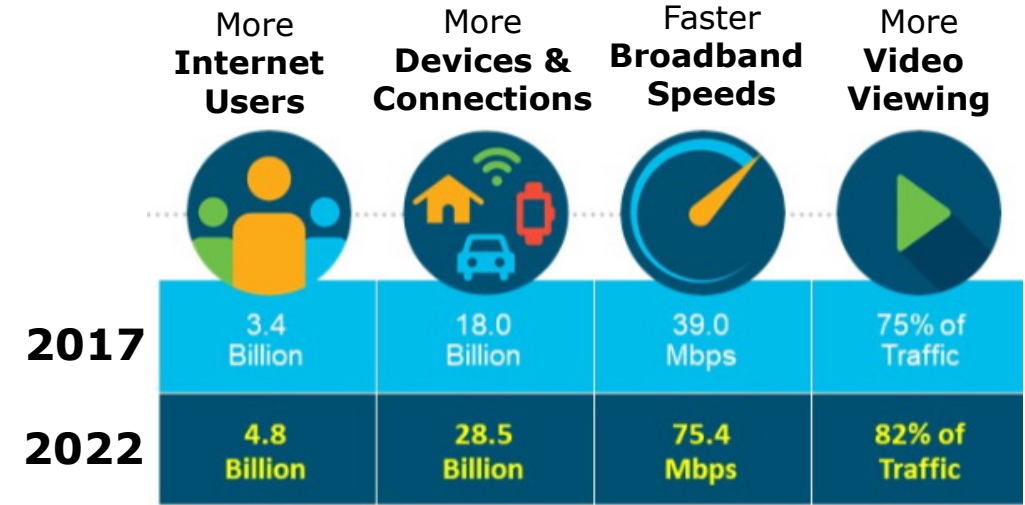- Many users, many devices and connections
- Bandwidth demand is growing rapidly
 - Worldwide international bandwidth, between 2017 and 2019, is more than doubled to reach ~1,500 Tbps*.



* Source: TeleGeography; This data does not reflect the impact of COVID-19.


Wireline Per Lane Data Rate Trends

 

T. Musah, "Wireline Link Standard," [Online]. Available: <https://mics.engineering.osu.edu/iostandards>

- Aggressive data rate scaling
 - Per-lane data rate doubles every 3 years across diverse I/O standards

Multi-Gb/s Wireline Connectivity

 


- ❑ To enable multi-Gb/s
 - Improved channel and co-optimized TX & RX equalization
 - TX clock synthesis to retune data at the TX
 - Clock and data recovery to sample data at the receiver
 - Optimized TX and RX clock jitter

Clocking Design in Microprocessor Systems


- ❑ Process technology optimized for low-power digital design
 - Suboptimum transistors (Rout, gain, ft, matching)
 - Feature limited (inductors, resistors, and capacitors)
- ❑ Process scaling
 - Variation
 - Density, reliability and power constraints
- ❑ Platform
 - Bandwidth limited channel
 - Supply/substrate noise
 - Low-cost low-quality reference clock

Challenges in generating and distributing high-quality clock

Multi-Gb/s Wireless Connectivity

 


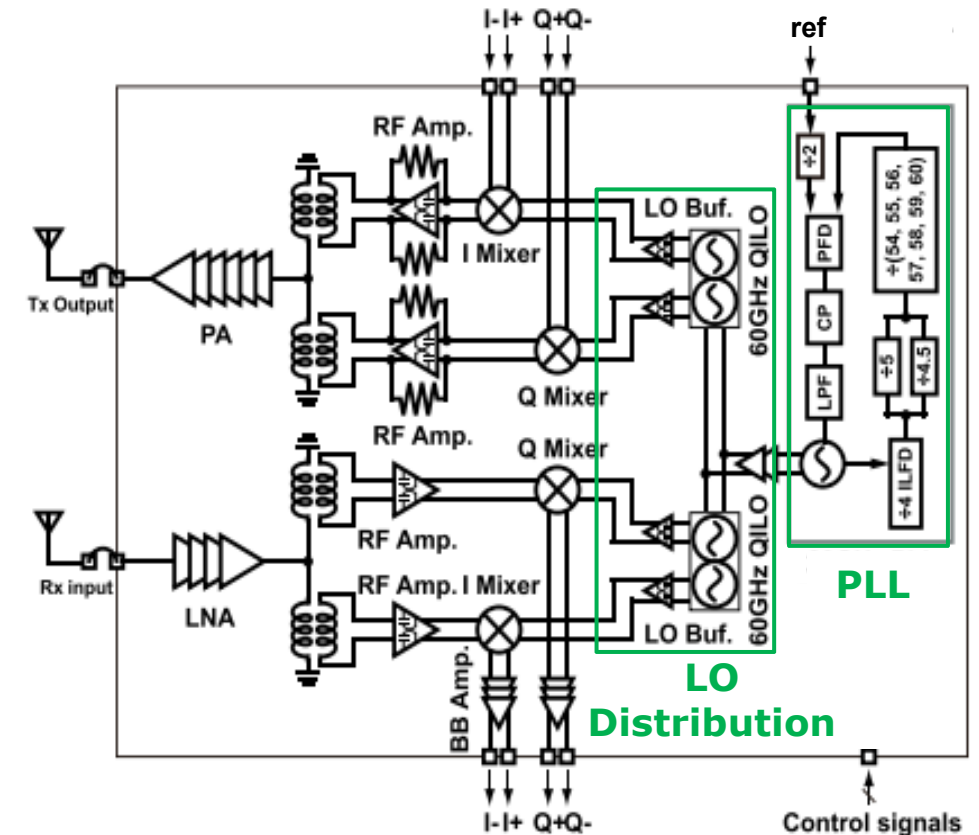- To enable multi-Gb/s
 - mmWave phased arrays (beamforming)
 - Channel-bonding capability and higher order modulation
 - Optimized phase noise of local oscillator (LO) and distribution
 - Clock jitter of analog-to-digital converter (ADC)/digital-to-analog converter (DAC)



Clocking Design in Wireless Systems

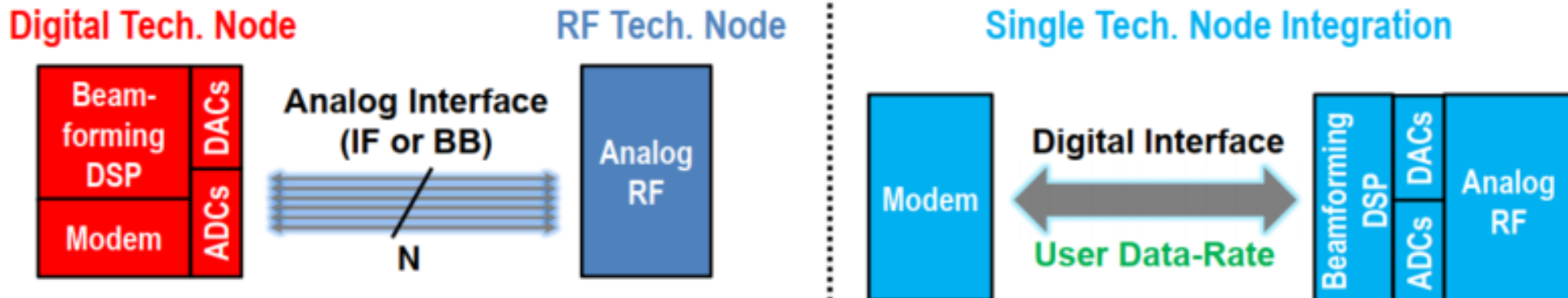S. Pellerano, et al. "A Scalable 71-to-76GHz 64-Element Phased-Array Transceiver ...", ISSCC 2019




- ❑ Process technology requirement: RF performance vs. scalability (IO & DSP)
- ❑ Process scaling
 - Variation, density, reliability and power constraints
- ❑ Platform
 - LO leakage, supply/substrate noise

Design tradeoffs in generating and distributing high-quality LO

Outline


- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management

Clock Non-Idealities

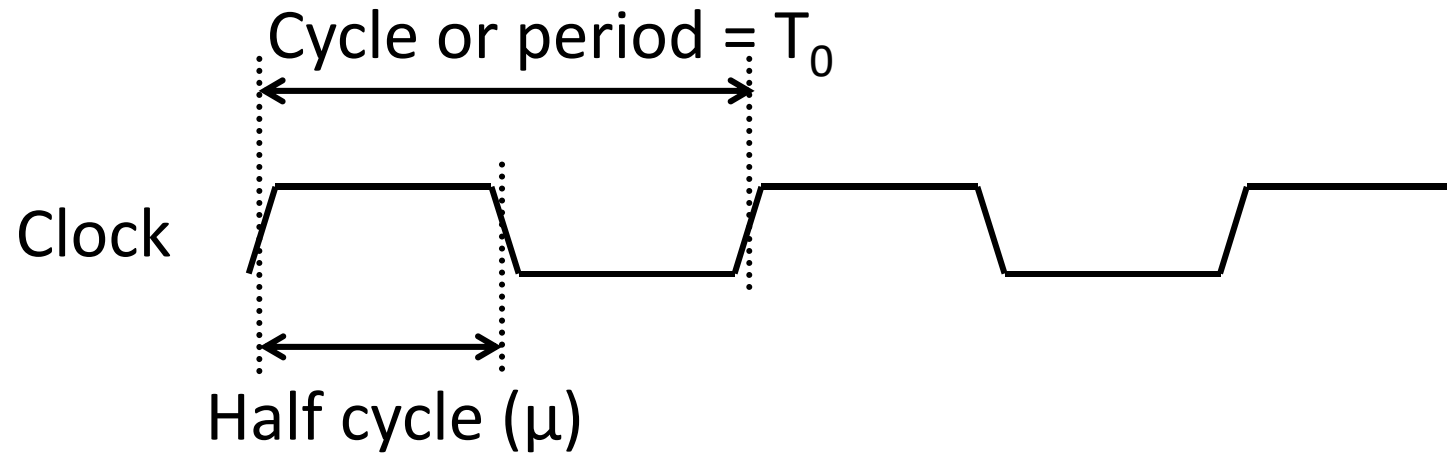


- ❑ Clock jitter/phase noise metrics are at the foundation of most industry specifications
- ❑ Crucial to analyzing and designing clock architectures
- ❑ Deviation of clock from an ideal edge
 - Skew is "static"
 - Jitter is "dynamic"

Clock Skew

 


- ❑ Caused by process variation and design/layout imperfections
- ❑ Deterministic and can be detected/corrected
- ❑ Examples
 - Duty-cycle error (DCE)
 - Multi-phase clock such as quadrature error

Clock Jitter

 



- Jitter can be random or deterministic, due to
 - Device noise such as thermal and flicker noise (random)
 - Supply/substrate noise, channel induced jitter (deterministic)
- Frequency content of “Jitter” is better metric for clock quality
 - In many cases, much of the jitter may be tracked by the RX

Jitter Metrics

 


- Cycle jitter = $\mu_i - \bar{\mu}$
 - Cycle-to-cycle jitter = $\mu_{i+1} - \mu_i$
 - N-cycle jitter = $\sum_1^N (\mu_i - \bar{\mu})$
- } High frequency content of jitter
- Accumulation aspect of jitter

N-Cycle Jitter Example

  

- Free-running oscillator
 - Jitter accumulates as edge propagates circularly

Differential Jitter

 


- Similar to absolute jitter, but with reference being another clock/data
- Example: forwarded clock (FC) applications
 - Clock-data jitter

System-Level Jitter Metrics


- ☐ Jitter generation
- ☐ Jitter transfer
- ☐ Jitter amplification
- ☐ Jitter tolerance

Jitter Generation

 

- ❑ Represents the intrinsic jitter at the output of a component when all other inputs are ideal
- ❑ Applicable to clock synthesizer and distribution
- ❑ A PLL example is shown


Jitter Transfer

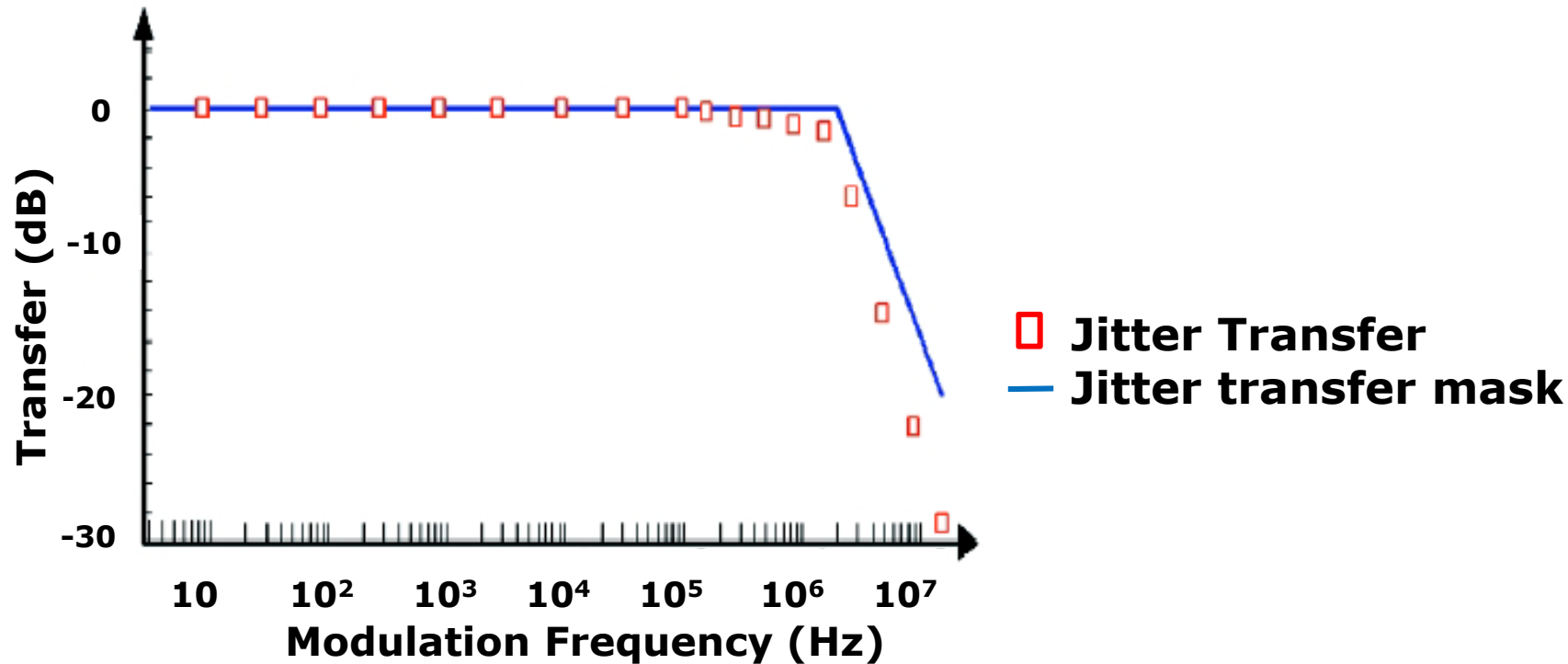

- Represents how a component shapes the input jitter
 - Ratio of output to input jitter as a function of frequency
- Mask is representative of target/standard requirement


Jitter Transfer vs. Frequency Response

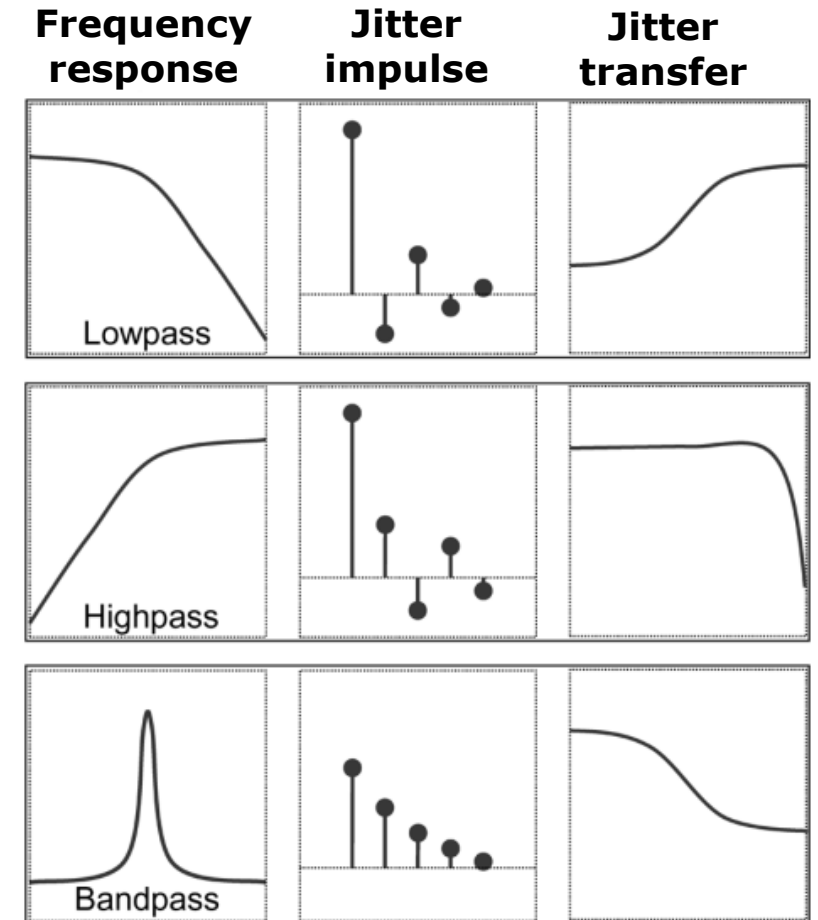- A bandwidth limited clock component amplifies jitter at high frequencies
 - Examples: Buffer, clock distribution
- A high-pass system with a pole \ll clock frequency passes all frequencies of jitter
 - Example: AC-coupled system
- A band-pass system with the center frequency aligned with the fundamental clock frequency, filters high frequency jitter
 - Example: Clock resonant network



B. Casper et al., "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links-A Tutorial," TCAS-I, Jan 2009.


Jitter Amplification

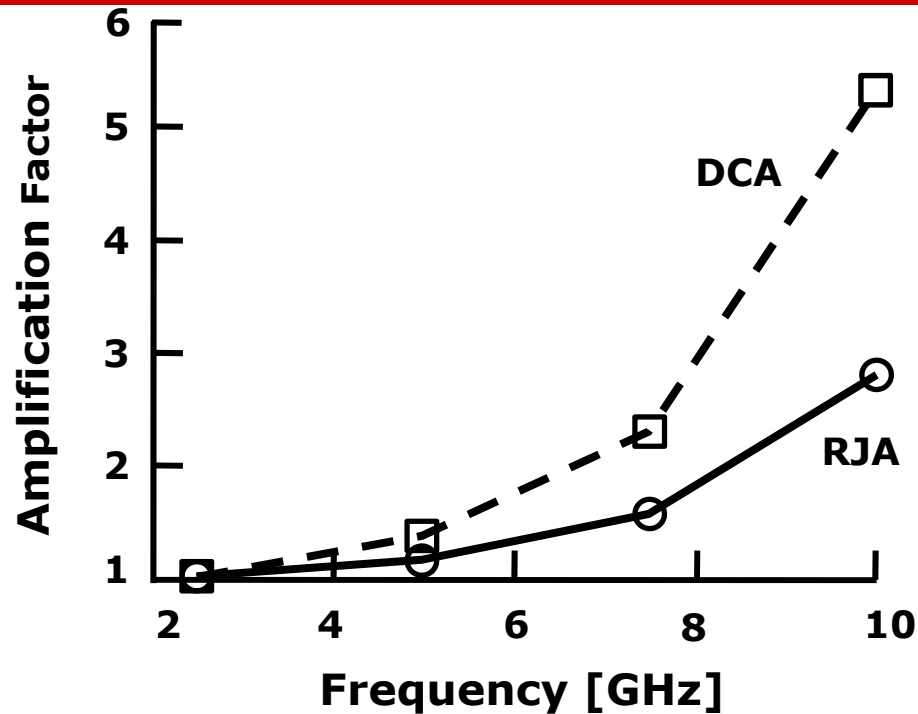

B. Casper et al., "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links-A Tutorial," TCAS-I, Jan 2009.

- Metric for bandwidth limitation of clock driver/distribution
 - Random jitter amplification (RJA) of input clock
 - Clock distribution signal integrity

Jitter Tolerance

 

- How well a receiver can tolerate input jitter
 - Achieving target bit error rate (BER) when subjecting the input to a sinusoidal phase modulated source at specified frequency and amplitude
- Mask is representative of target/standard requirement


Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management

Clock Synthesizer Techniques

- ❑ Phase-locked loops (PLLs)
- ❑ Multiplying delay-locked loops (M-DLLs)
- ❑ Sub-sampling PLLs
- ❑ Sub-harmonic injection-locked oscillators (ILOs)

Phase-Locked Loops (PLLs)

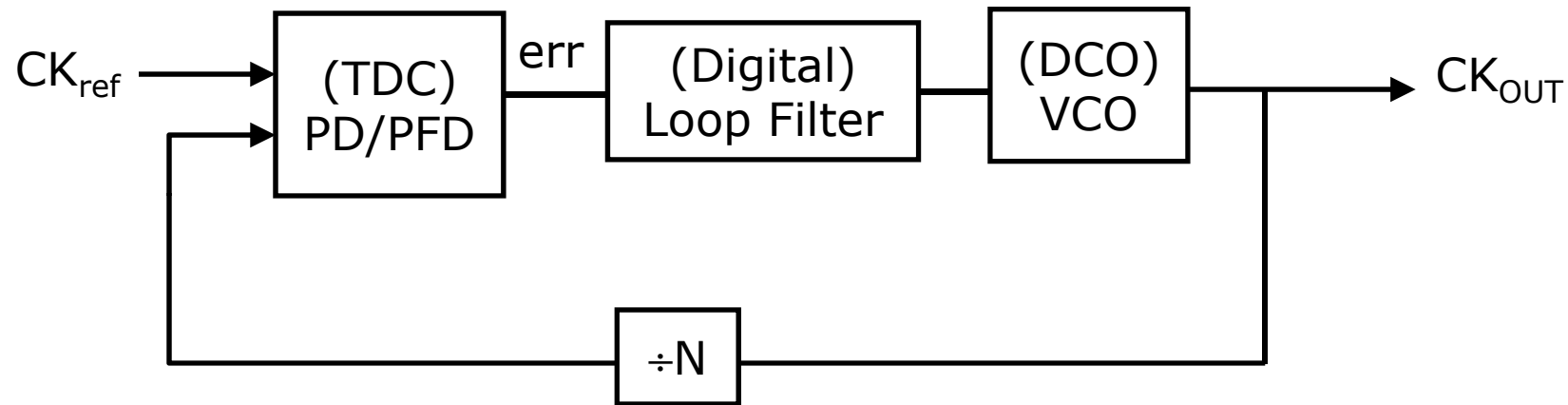

- PLLs multiply and filter external reference clock (CK_{ref})
 - PD/PFD* compares CK_{ref} with divided VCO** clock and produces an error signal
 - The error signal is low-pass filtered and drives the VCO
 - The negative feedback loop locks the VCO phase to the reference clock phase


* Phase detector (PD) or phase/frequency detector (PFD)

** Voltage-controlled oscillator (VCO)

PLL Loop Types


□ Type I

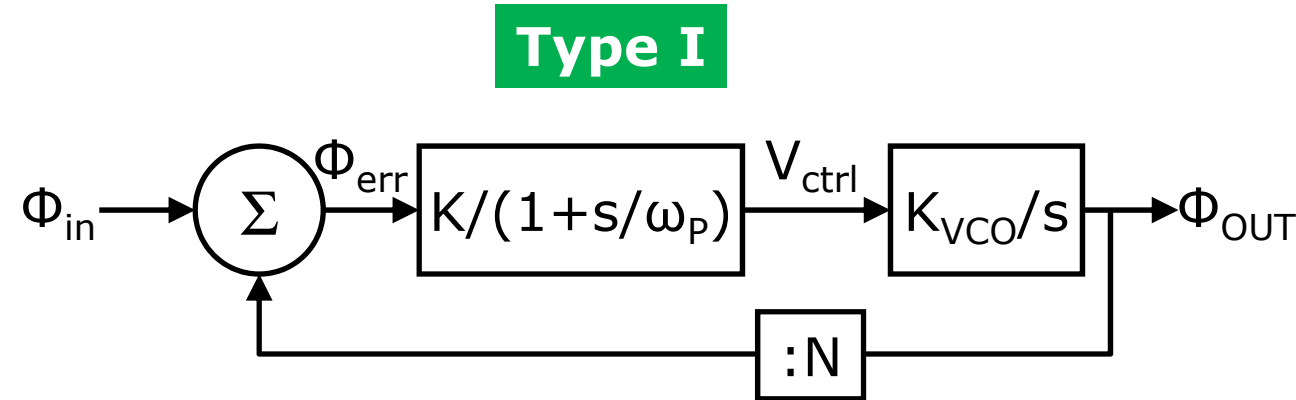- Proportional (P) feedback
- Static phase error
- Unconditionally stable





□ Type II

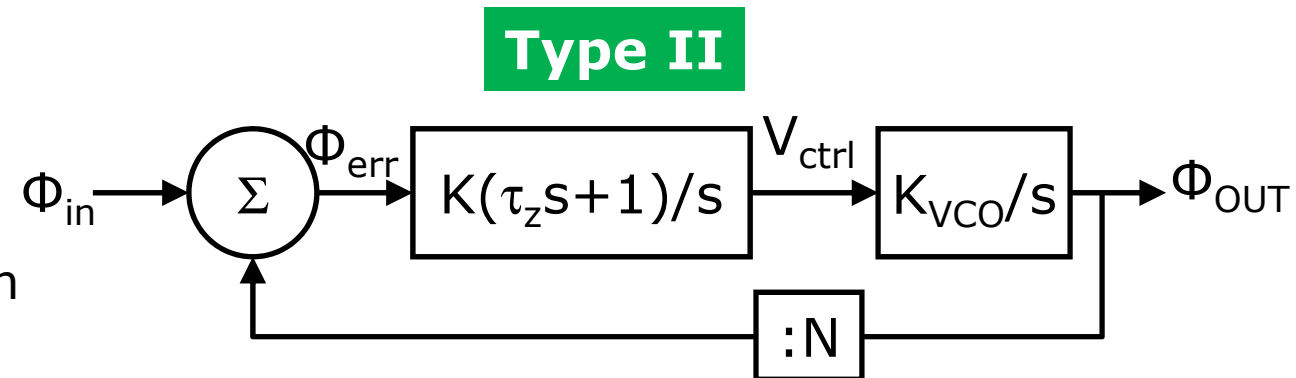- Proportional-integral (P-I) feedback
- No static phase error
- 2 poles @ DC → requires stabilization



Type II PLL: Jitter Transfer & Generation

 
 
- PLL bandwidth tradeoffs
 - Lowering PLL bandwidth (BW) rejects input jitter
 - Increasing PLL BW rejects VCO jitter



 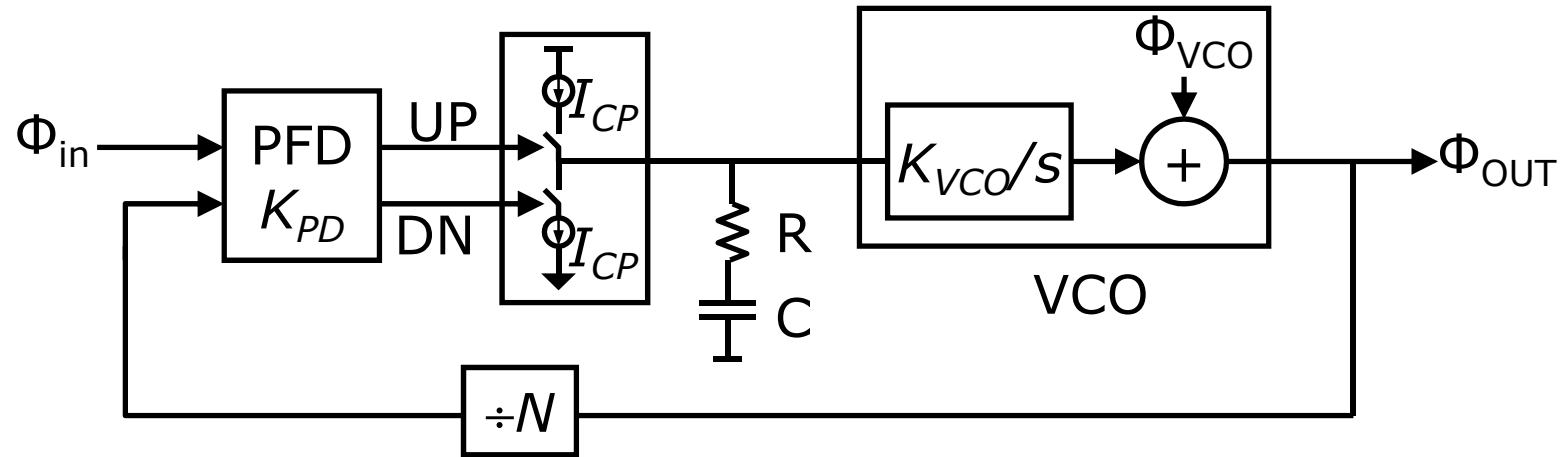A. Sheikholeslami, "Basics of high-speed chip-to-chip and backplane signaling", ISSCC Tutorial 2008

Type II PLL: Closer look at Jitter Transfer

- Jitter transfer peaking is a function of zero and poles location
- Minimizing the peaking is desirable as it amplifies the input jitter





T. Lee, The Design of CMOS Radio-Frequency Integrated Circuits, Cambridge University Press, 1998, p. 458.

PLL Jitter/Phase Noise Components

- ☐ Voltage-controlled oscillator (VCO)
- ☐ Input reference clock
- ☐ Divider
- ☐ Phase/frequency detector (PD/PFD)
- ☐ Charge-pump (CP)


VCO Jitter

  - ❑ Jitter accumulates as uncertainty in earlier transitions affects the following ones
- ❑ Thermal noise is uncorrelated
$$\sigma_{\Delta T} = k \cdot \sqrt{\Delta T}, \Delta T = N \cdot T_0$$
- ❑ Flicker and supply noise induced jitter are correlated
$$\sigma_{\Delta T} = \delta \cdot \Delta T, \Delta T = N \cdot T_0$$
- ❑ κ and δ are determined by VCO design



A. Hajimiri et al., "Jitter and phase noise in ring oscillators," JSSC, June 1999

VCO Phase Noise

 


$$\text{N-cycle jitter (rms)} = \frac{\Delta f}{f_0^{3/2}} \cdot 10^{\frac{L(\Delta f)}{20}} \cdot \sqrt{N}$$

A. Hajimiri et al., "Jitter and phase noise in ring oscillators," JSSC, June 1999

- Phase noise metric is widely used in wireless/mmwave
- Convert phase noise to N-cycle jitter
 - Thermal noise dominated
 - No amplitude modulation


PLL Phase noise & Jitter: Noisy VCO

 

A. Hajimiri, "Noise in Phase-Locked Loops [Invited]," SSMSD, Feb. 2001

- Assuming an ideal input clock & 1st-order PLL
 - PLL filters the VCO phase noise for frequencies $<$ PLL BW
 - Jitter accumulates up to PLL BW \rightarrow The higher the BW, the lower the VCO jitter


PLL Phase noise & Jitter: Noisy Input

 

A. Hajimiri, "Noise in Phase-Locked Loops [Invited]," SSMSD, Feb. 2001

- Assuming an ideal VCO & 1st-order PLL
 - PLL filters the input phase noise for frequencies outside PLL BW

Impact of Divider on PLL Phase noise

 


A. Hajimiri, "Noise in Phase-Locked Loops [Invited]," SSMSD, Feb. 2001

- An ideal frequency divider increases
 - Input phase noise (by $20\log(N)$)
 - Charge-pump/phase detector phase noise (by $20\log(N)$)
- Divider white noise adds to the input noise

Clock Synthesizer Techniques

- ☐ Phase-locked loops (PLLs)
- ☐ Multiplying delay-locked loops (M-DLLs)
- ☐ Sub-sampling PLLs
- ☐ Sub-harmonic injection-locked oscillators (ILOs)


Delay-Locked Loops (DLLs)

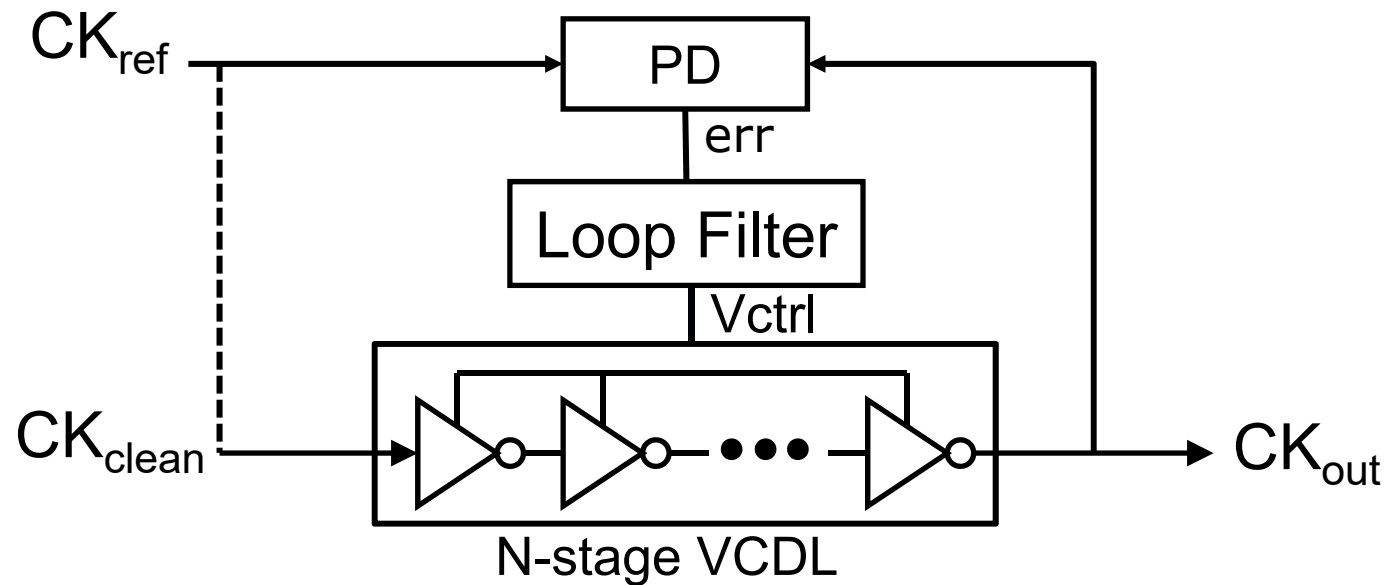

- Similar to PLL
 - PD compares reference clock and voltage-controlled delay line (VCDL) output clock and produces an error signal
 - The error signal is low-pass filtered to control the delay of N-stage VCDL
- VCDL input can be either a reference clock or a clean clock signal

DLL vs. PLL

 
- ✓ Unlike VCO, VCDL does not accumulate jitter
- ✓ DLL is unconditionally stable
- ✓ Loop filter can be an integrator or accumulator
- ✗ No filtering on input clock
 - Requires an additional clean clock
- ✗ False lock to harmonics
- Multiplication?




- **PLL and DLL**
 - Same BW
 - Same delay elements
- **PLL is 2nd-order with $\zeta=1$**

B. Razavi, Phase locking in high-performance systems Wiley-IEEE Press Press, 2003.

Multiplying DLL

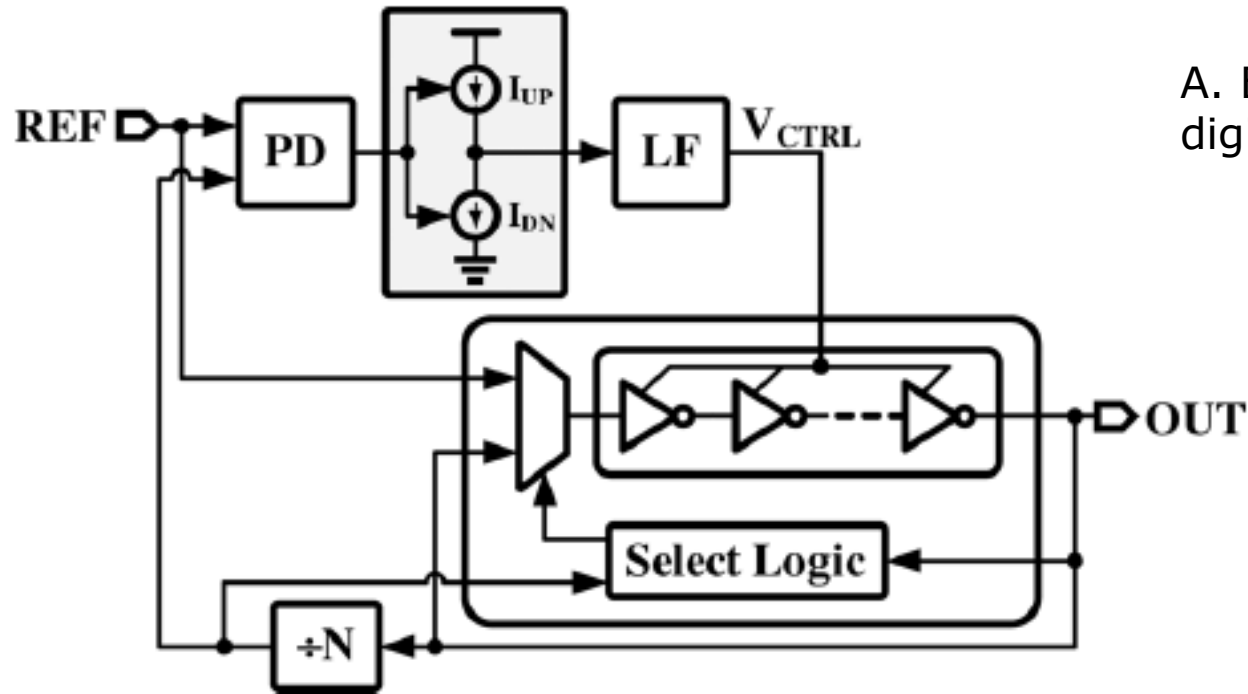

 A. Elshazly et al., "Clock multiplication techniques using digital multiplying delay-locked loops," JSSC 2013.




- ❑ Generates a phase-locked output clock at a multiple of the reference clock
- ❑ At every reference cycle, accumulated jitter of output clock is reset

Clock Synthesizer Techniques

- ❑ Phase-locked loops (PLLs)
- ❑ Multiplying delay-locked loops (M-DLLs)
- ❑ Sub-sampling PLLs
- ❑ Sub-harmonic injection-locked oscillators (ILOs)


Sub-Sampling PLL

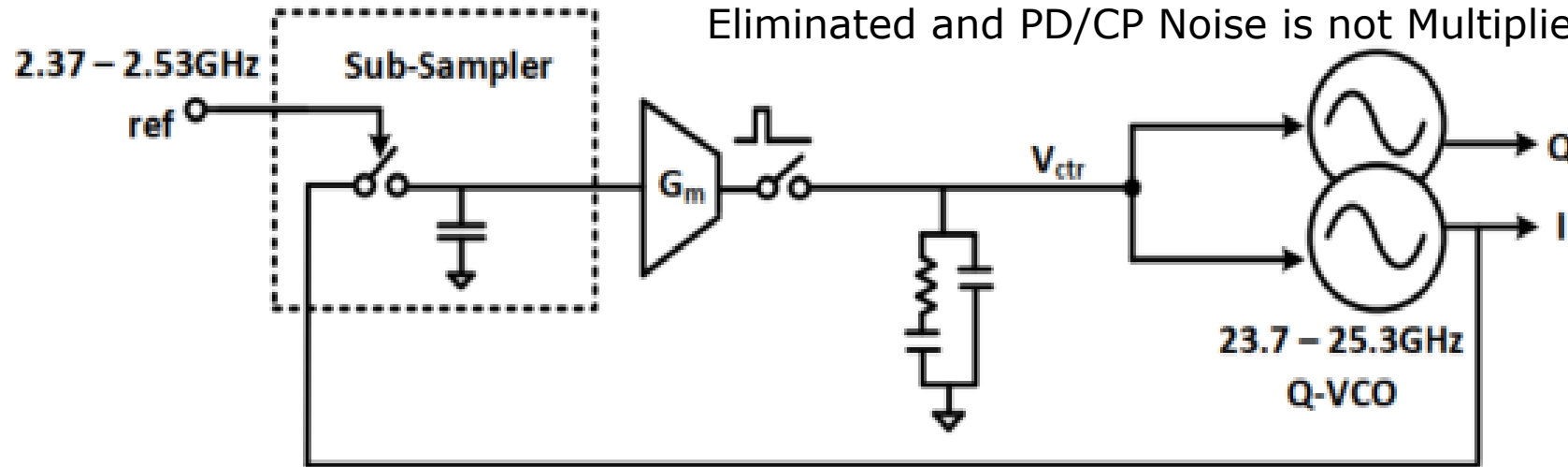X. Gao et al., "A Low Noise Sub-Sampling PLL in Which Divider Noise is Eliminated and PD/CP Noise is not Multiplied by N^2 ," *JSSC*, Dec. 2009



- ❑ Sub-sampling VCO by a reference clock (no divider)
- ❑ Direct sampling of VCO output (no high-frequency/mmwave buffer)
- ❑ Phase/timing error converted into voltage error

Sub-Sampling vs. Classical PLL

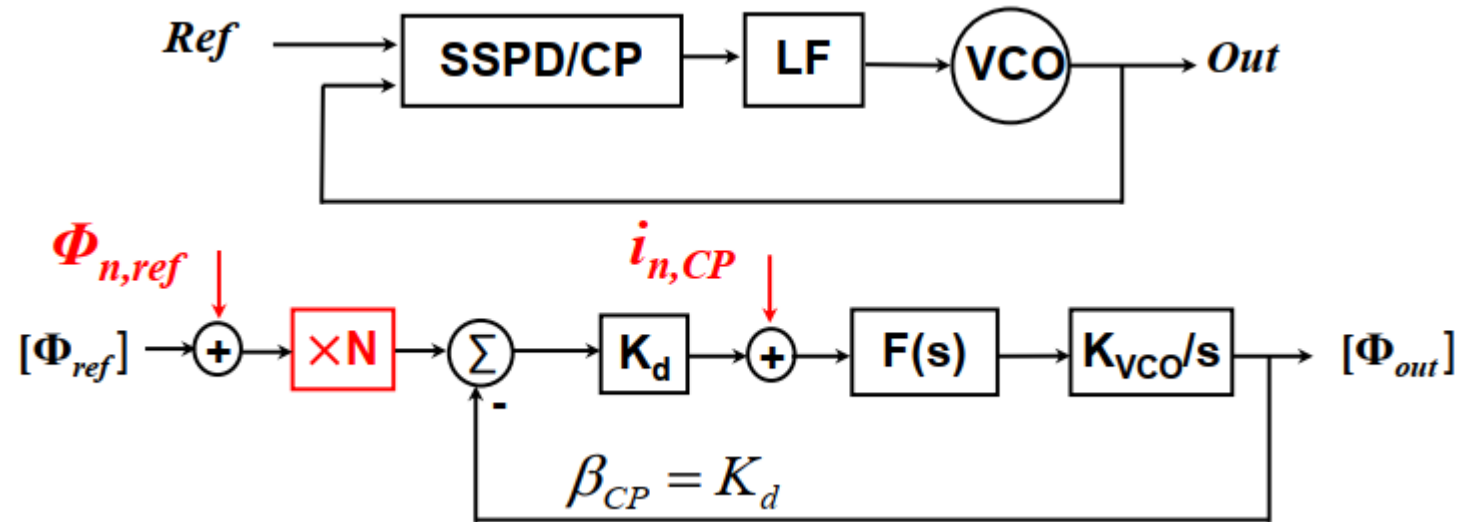


- ☐ "Ref" phase noise increases by $20\log(N)$ due to virtual multiplier, same as a PLL
- ☒ Charge pump (CP) phase noise is suppressed (no divider)
- ☒ Higher PLL BW and better VCO phase noise suppression
- ☒ May lock to harmonics
 - ☒ Can be addressed by frequency locked loop
- ☒ Larger capacitor due to high phase detection gain

Clock Synthesizer Techniques



- Phase-locked loops (PLLs)
- Multiplying delay-locked loops (M-DLLs)
- Sub-sampling PLLs
- Sub-harmonic injection-locked oscillators (ILOs)

Injection-Locked Oscillators (ILOs)

 

- ❑ Locks to injected clock (within its lock range)
- ❑ 1st-harmonic ILO ($f_{inj} = f_o$)
- ❑ Sub-harmonic ILO ($f_{inj} = f_o/N$)
 - Frequency multiplier, similar to PLL/MDLL
 - False lock, similar to sub-sampling PLL/MDLL
- ❑ Behaves like a type-I PLL
 - Frequency mismatch causes phase offset

Injection Locking Theory

 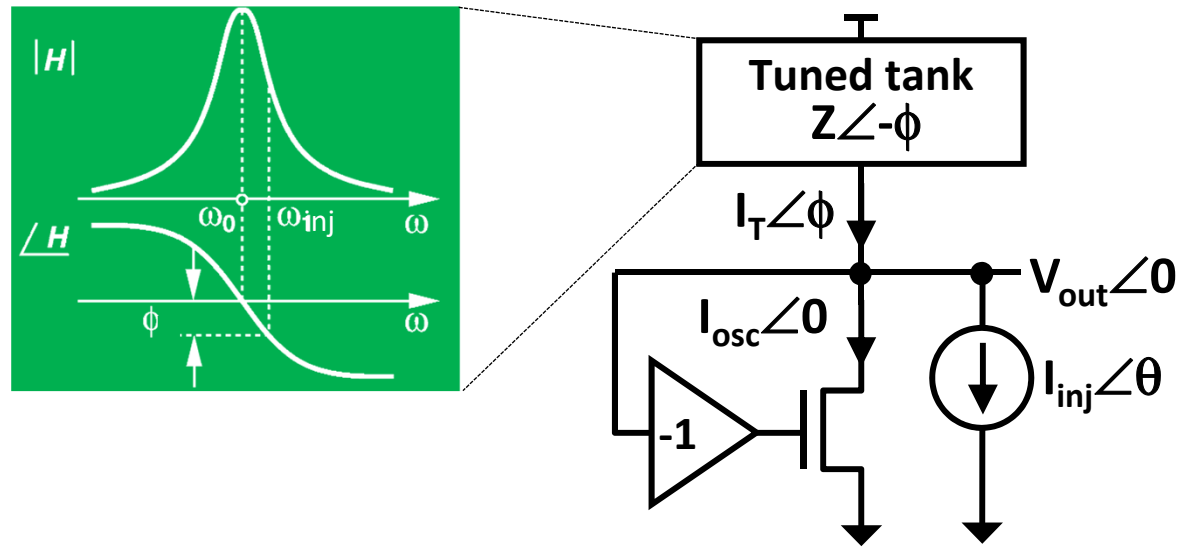


$$\tan \phi = \frac{I_{inj} \cdot \sin \theta}{I_{osc} + I_{inj} \cdot \cos \theta} = \frac{K \cdot \sin \theta}{1 + K \cdot \cos \theta}, \quad K = \frac{I_{inj}}{I_{osc}}$$

K is injection strength

- Phase offset between injection and output clock if $\omega_{inj} \neq \omega_0$
- $BW = \frac{f_0}{2Q} \frac{K}{K+1}$ (for $f_{inj} = f_0$)
 - Bandwidth increases with K and reduces with Q

ILO vs. PLL

 
- ☐ 1st-harmonic ILO
 - ☒ Can achieve higher BW and thus, better VCO noise performance
 - ☒ Low-bandwidth loop to set $f_0 = f_{inj}$
- ☐ Sub-harmonic ILO
 - ☐ Harmonic generation results in lower K and thus lower BW
 - ☒ A PLL to set $f_0 = N * f_{inj}$
- ☒ Phase rotation in clock recovery applications



S. Shekhar, et al., "Strong injection locking in low-Q LC oscillators: modeling and application in a forwarded-clock I/O receiver," JSSC 2009

ILO-Based Phase Rotation

 - ILO can recover and rotate the clock phase
 - Clock recovery sets VCO free-running frequency and thus rotates the phase
- Phase resolution and linearity vs. VCO tuning range
 - The higher the K , the better linearity/resolution
 - The lower the K , the smaller the tuning range





S. Shekhar, et al., "Strong injection locking in low-Q LC oscillators: modeling and application in a forwarded-clock I/O receiver," JSSC 2009

ILO-Based vs. Conv. Phase Interpolator

- ✓ Rotating the clock by tuning VCO frequency
 - ✓ No need for multi-phase generation or MUX
 - ✓ Low power and low area
- ✗ Limited vs. full phase rotation in PI
- ✗ BW varies with phase shift (Max BW @ phase = 0)
 - ✓ Dual feedback to reduce BW variation

 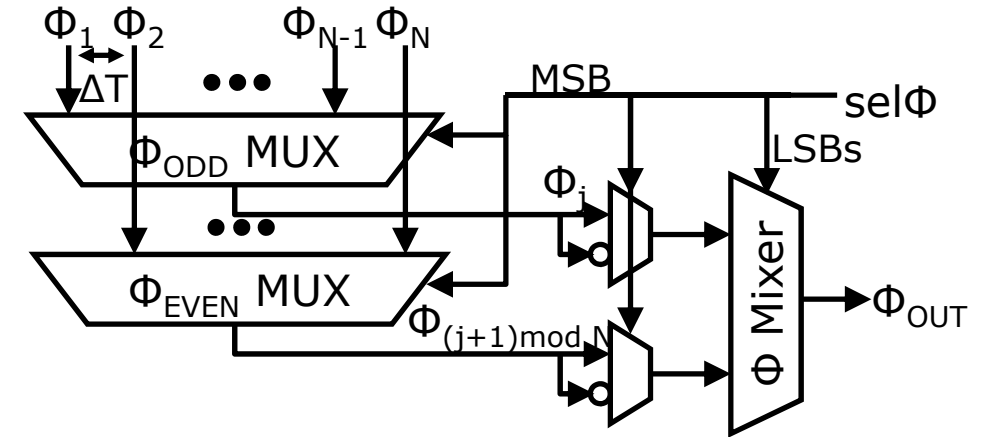J-H Seol, et al. "An 8Gb/s 0.65mW/Gb/s forwarded-clock receiver using an ILO with dual feedback ...," ISSCC 2013



Clock Synthesizer Summary

- Generate a low-jitter multi-GHz clock from a low-frequency reference clock
 - Design tradeoffs between jitter transfer & jitter generation
- M-DLLs and ILOs are alternatives to PLLs
 - Lower jitter accumulation benefit
- Sub-sampling PLLs are widely used in wireless applications
 - Lower phase noise by suppressing CP/PD and eliminating divider phase noise
- ILO is an alternative to conventional PI for clock phase rotator

Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management

Voltage Controlled Oscillators (VCOs)


- ☐ Jitter/phase noise performance
- ☐ Supply noise sensitivity
- ☐ Operating frequency
- ☐ Tuning range
- ☐ Power
- ☐ Area

VCO Topologies

- ❑ LC-VCO
- ❑ Current-mode logic (CML) based VCO
- ❑ Inverter-based VCO

LC-VCO

 
- ✓ Excellent jitter/phase noise performance
 - ✗ Process support for integrated inductor
 - ✗ Lower Q in CMOS digital process
- ✓ Low supply noise sensitivity
- ✗ Large area due to passives
- ✗ Narrow frequency tuning range
- ✗ Portability challenges




□ **Different LC VCO topologies**
➤ Colpitts oscillator,
quadrature LC-VCO, etc

CML-Based VCO

 - ✓ Wide frequency tuning range
- ✓ Power vs. frequency scaling
- ✓ Portable
- ✗ Poor jitter performance
- ✗ High bias/supply noise sensitivity





“Symmetric-Load” (SL) delay cell

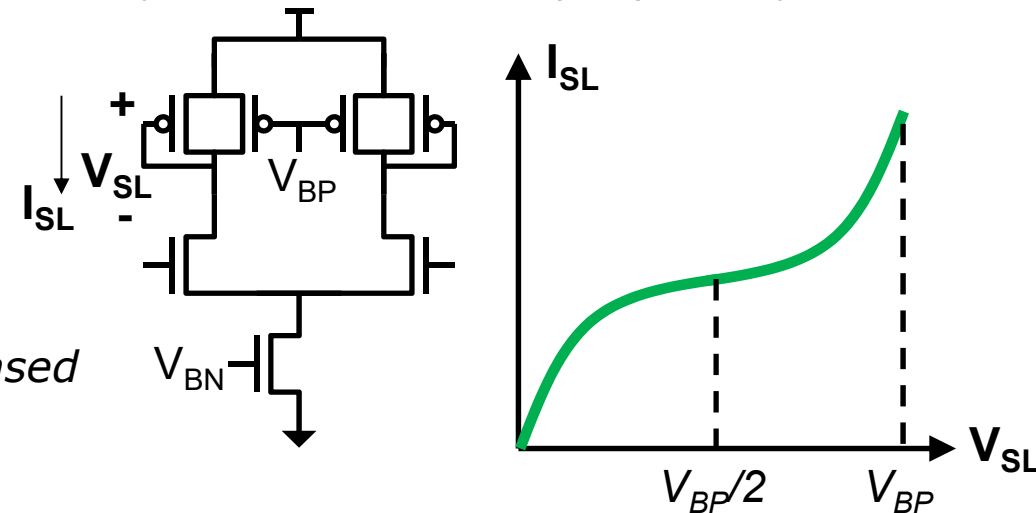

J. Maneatis, "Low-jitter process-independent DLL and PLL based self-biased techniques", JSSC, pp. 1723-1732, Nov. 1996

Inverter-Based VCO

  - ✓ Wide frequency tuning range
- ✓ Power vs. frequency scaling
- ✓ Portable
- ✓ More variation-tolerant than CML-based
- Jitter performance
 - ✓ Better than CML-based
 - ✗ Worse than LC-VCO
- ✗ High supply noise sensitivity





□ **Variants on CMOS delay cells**
➤ **Current, capacitively or digitally controlled**

VCO Comparison Summary


	Inv-Based VCO	CML-Based VCO	LC VCO
Jitter/ Phase Noise	2 nd best	X	✓ Best
Supply noise sensitivity	X needs regulator	2 nd best	✓ Best
Frequency range	✓ Wide	✓ Wide	X Narrow
Area	X Including regulator	✓ Yes	X
Portable	✓ Yes	✓ Yes	X No

Regulated Inverter-Based VCO

  


- ❑ 10-40dB power supply noise rejection ratio (PSRR)
- ❑ Regulator degrades power/current efficiency
- ❑ Bandwidth vs. power/area tradeoff
 - To avoid peaking in PSRR: Amplifier pole (ω_a) > regulator output pole (ω_o)
 - If inside the PLL/DLL loop, the regulator BW should be higher than loop BW

Examples of Regulator Topologies

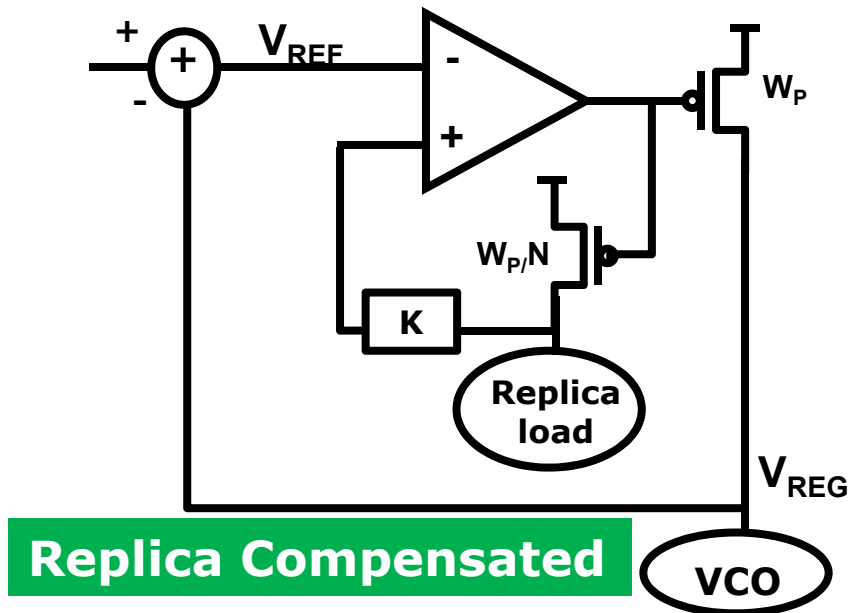

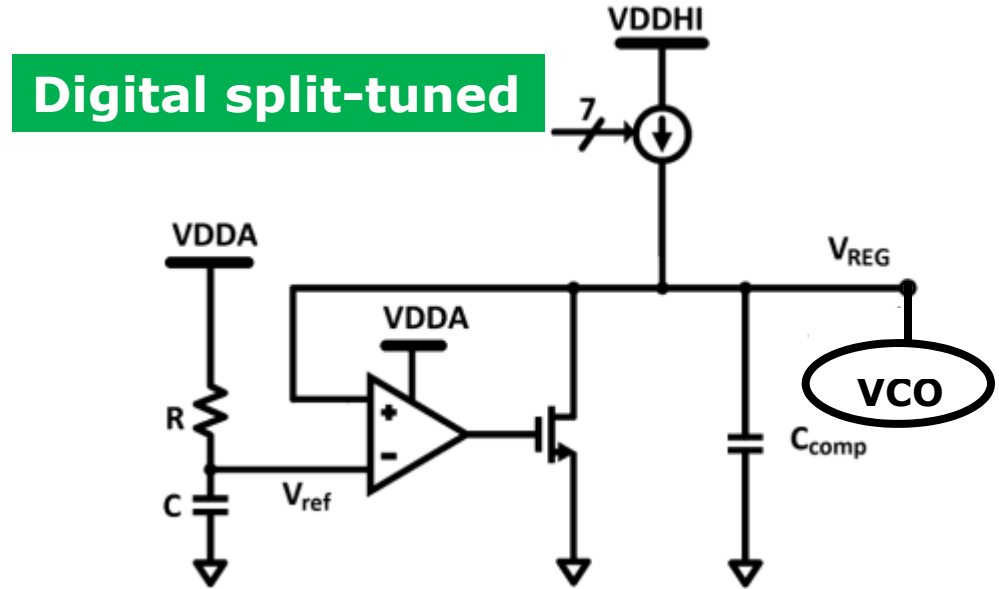E. Alon et al., "Replica Compensated Linear Regulators for Supply-Regulated Phase-Locked Loops", JSSC 2006



T. Musah, et al., "A 4–32 Gb/s Bidirectional Link With 3-Tap FFE/ 6-Tap DFE and Collaborative CDR in 22 nm CMOS," JSSC 2014



- ❑ Improving PSRR response with minimum power and area penalty
 - Using "replica" or "split-tuned" to push amplifier pole to higher frequency
- ❑ Faster response time
 - Fast wakeup and clock power management

Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management


Clock Distribution Design Considerations

  - Distribution from clock synthesizer to TX and RX lanes
 - Jitter/phase noise
 - Bandwidth/slew rate
 - Operating frequency range
 - Distribution vs. local clock frequency
 - Power (dynamic vs. static)
 - Area
 - Latency
 - Mismatch between IQ phases



Wireline Clock Distribution Example

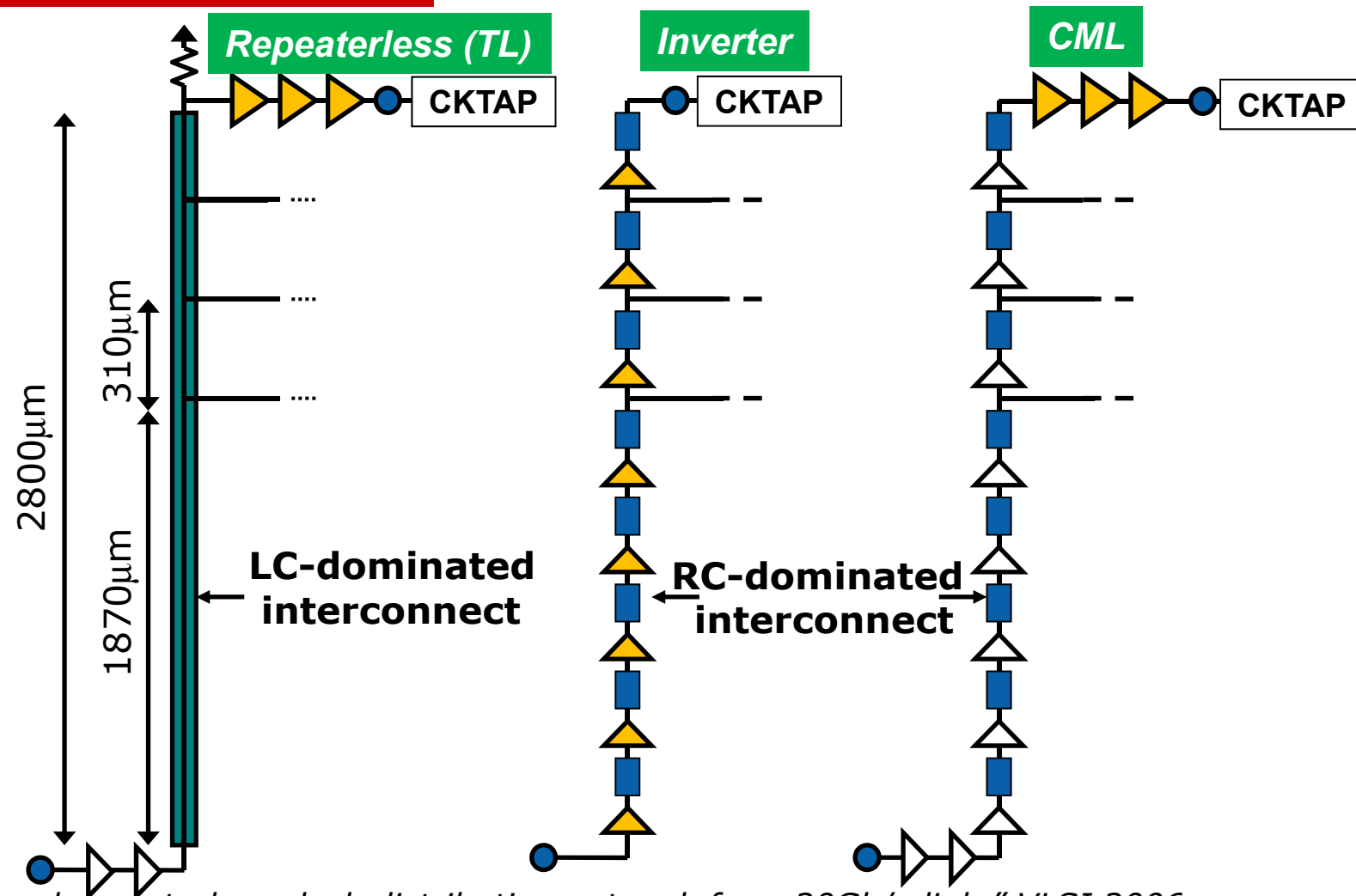- Clock distribution common topologies
 - Repeaterless (on-die transmission lines)
 - CMOS inverter buffers
 - CML buffers



F. O'Mahony et al, "A low-jitter PLL and repeaterless clock distribution network for a 20Gb/s link," VLSI 2006

Comparison Summary (10GHz)


	Jitter [\pm ps] with $\pm 5\%$ Vcc noise	Latency [ps]	Power [mW]
Repeaterless (TL)	1.0	79	73
Inverter	3.2	96	53*
CML	1.4	142	110

* Zero static power

- Repeaterless
 - 3.2x (10dB) better PSRR with 38% more power compared with inverter
 - 1.4x (3dB) better PSRR with 34% less power compared with CML
 - Area hungry and integration un-friendly
- Inverters are power and area efficient at cost of poor PSRR
 - Easy power management due to zero static current
 - Regulated supply: jitter vs. power/area/wakeup time

Repeaterless TL Topologies

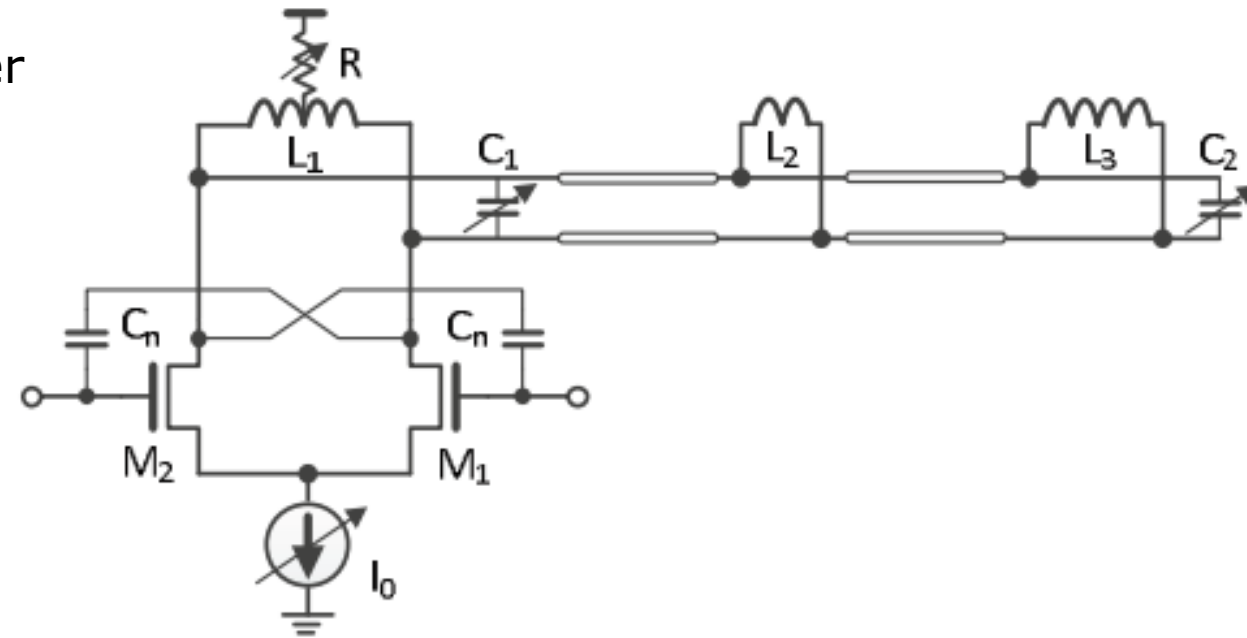
- Open-drain buffer w/ termination at output
 - ✓ Amplitude matched
 - ✗ Phase mismatched
 - ✗ Low-swing clock → needs level converter
- Standing wave based
 - ✓ 3-5x power reduction
 - ✓ Near full-swing clock
 - ✓ Phase matched
 - ✓ Minimized amplitude mismatch
 - ✗ Narrowband frequency
 - ✗ Routing < fraction of clock wavelength



 G. Li et al, "Standing Wave Based Clock Distribution Technique with Application to a 10 × 11 Gbps Transceiver in 28 nm CMOS," IEEE Asian Solid-State Circuits Conference 2015



Clock Distribution Jitter Optimization

- Clock distribution can limit jitter/phase noise performance
 - Jitter generation
 - Input random jitter amplification (RJA)
- Power vs. jitter amplification
 - Ex: Inverter chain with lower fan-out (FO) minimizes RJA at cost of power
- Improving jitter and power
 - Self-oscillating clock networks or tuned LC to resonate with line capacitance



B. Casper et al., "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links-A Tutorial," TCAS-I, Jan 2009.


Resonant Clock Network Example

 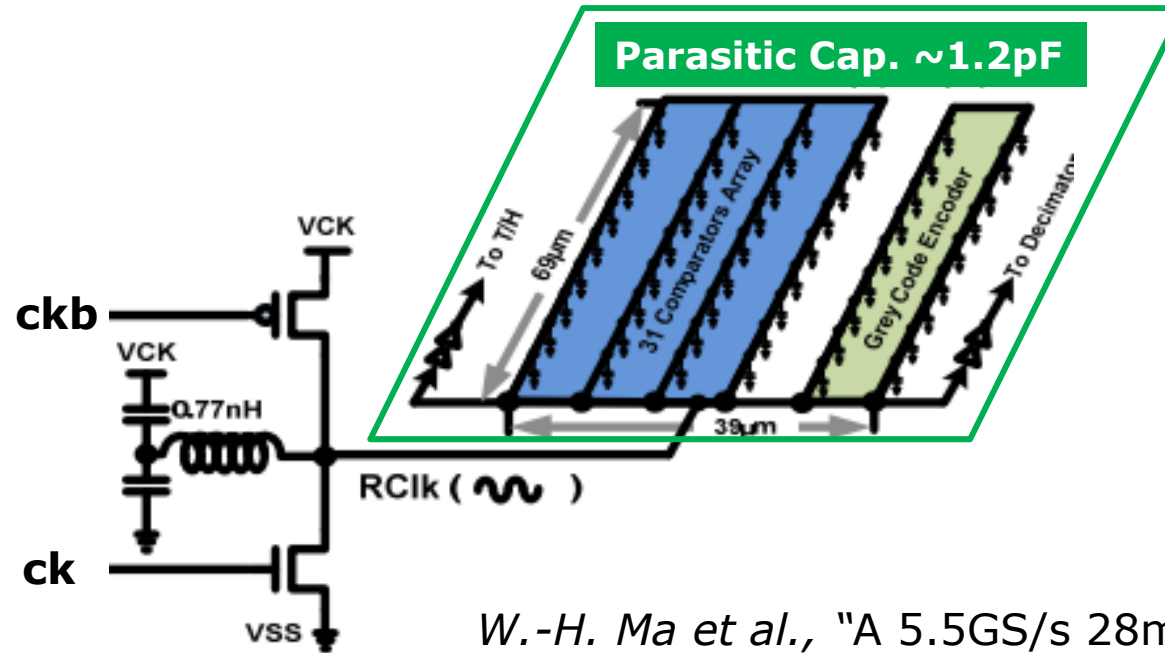


W.-H. Ma et al., "A 5.5GS/s 28mW 5-bit Flash ADC with Resonant Clock Distribution," ESSCIRC 2011.

- ❑ Resonant clock distribution to drive a flash ADC
- ❑ 50% lower power compared to conventional inverter buffers (CV^2f)

Wireless LO Distribution Example

 

 S. Pellerano et al., "A Scalable 71-to-76GHz 64-Element Phased-Array Transceiver ...", ISSCC 2019



☐ mmWave LO distribution

- ☒ Many gain stages
- ☒ I & Q mismatches
- ☒ Lossy match to 50ohm TLs

☐ Low frequency reference distribution

- ☒ Minimize distribution power
- ☐ Local mmWave synthesizer
- ☒ Better noise/power trade off

Clock Distribution Summary

- Circuit architecture and techniques to minimize
 - Jitter
 - Power
 - Area
- Repeaterless is an alternative to CMOS/CML distribution
- Resonant clock network achieves better BW/jitter and power performance
- Sub-harmonic LO distribution for better noise, power and IQ matching


Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management

Clock Recovery


- ❑ Forwarded clock (FC) systems
- ❑ Embedded clock (EC) systems

Forwarded Clock (FC) Recovery

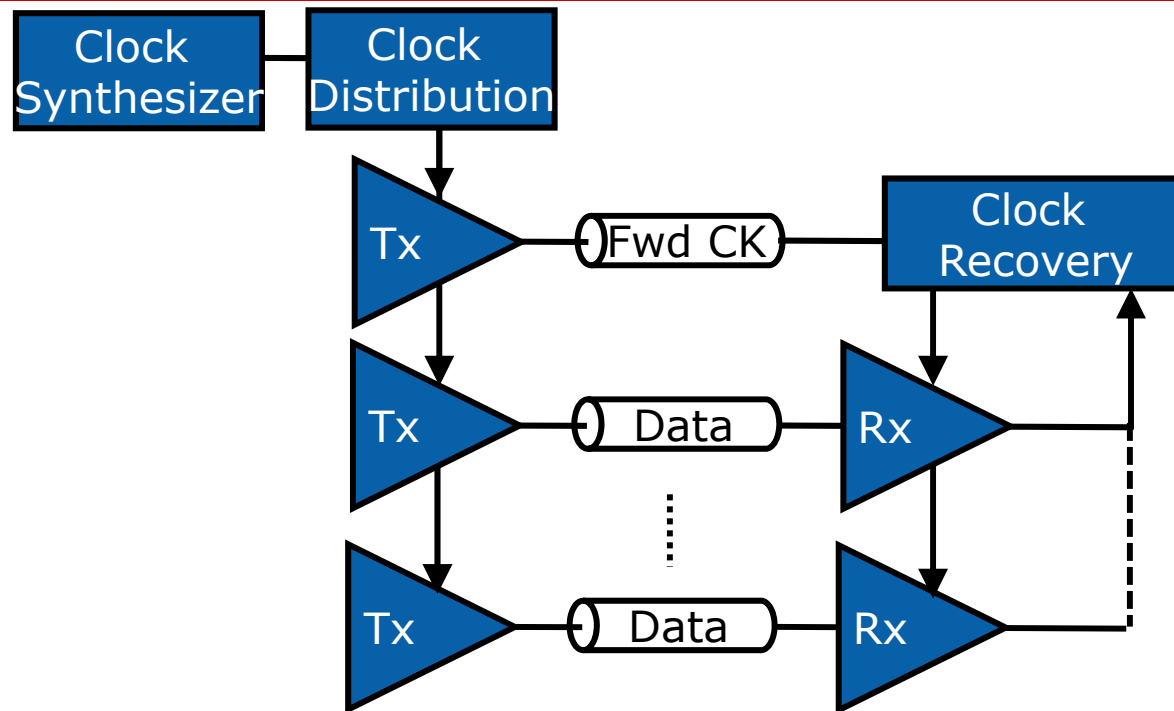

- ❑ Wide parallel link interfaces where Fwd CK overhead is amortized
 - Examples: DDRx, LPDDRx
- ❑ Recovery method
 - Extract timing from FC using training or periodic deskew

Differential Jitter in FC System

 


- Example shown for $3UI$ delay mismatch between Fwd CK and data path
- Effective RX sampling jitter = Differential jitter between "FWCK" and "din"

FC Recovery Design Considerations


- Data-FC tracking is a key advantage
 - Jitter accumulation up to delay difference between two paths
 - Minimize delay mismatch between two paths
- Fwd CK jitter amplification due to channel loss
 - No filtering for DLL-based clock recovery (CR)
 - Filtering high frequency jitter using PLL or ILO-based CR
- Clock recovery
 - Low-bandwidth loop to compensate for voltage/temperature drift
 - Fine phase tuning of Fwd CK for optimum RX data sampling
 - DLL/PI vs. VCO/ILO-based forwarded clock

DLL-Based FC Recovery

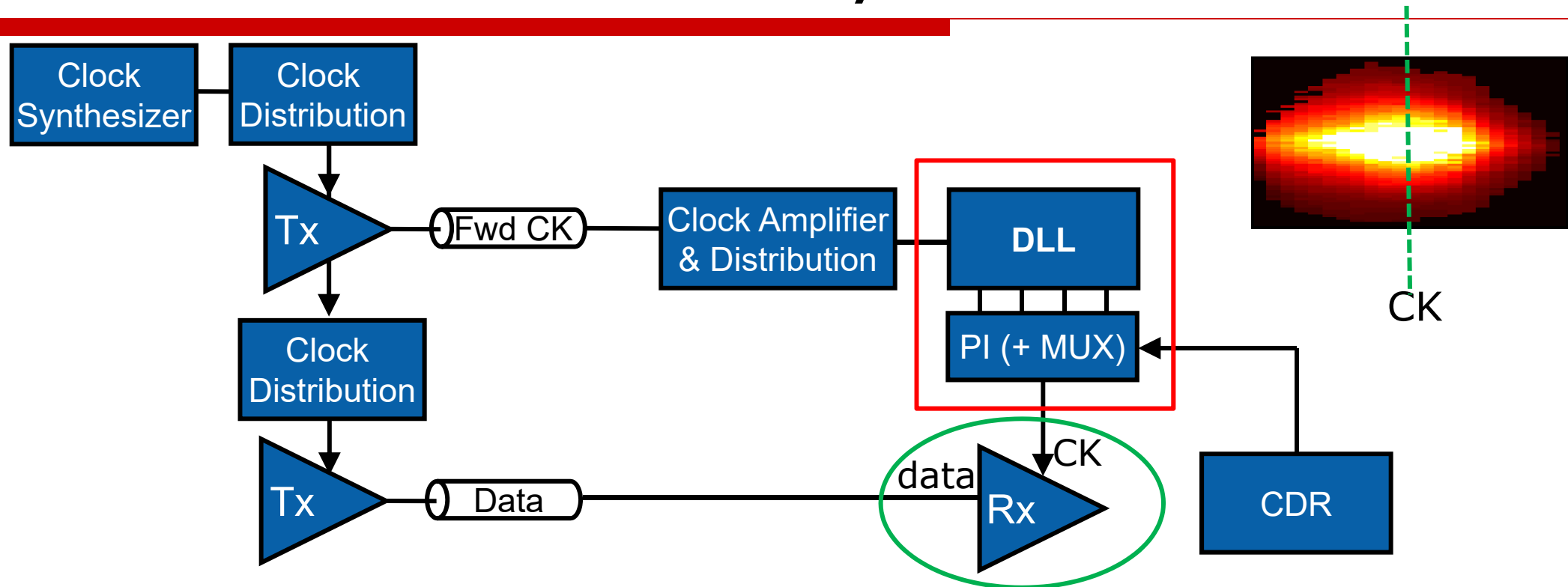


- ❑ Multi-phase DLL and phase interpolator (PI) samples RX data at optimum point
 - ✓ Low-BW clock and data recovery (CDR) which sets PI code
 - ✓ No additional jitter accumulation (owing to DLL)
 - ✗ No filtering on Fwd CK

PLL-Based FC Recovery

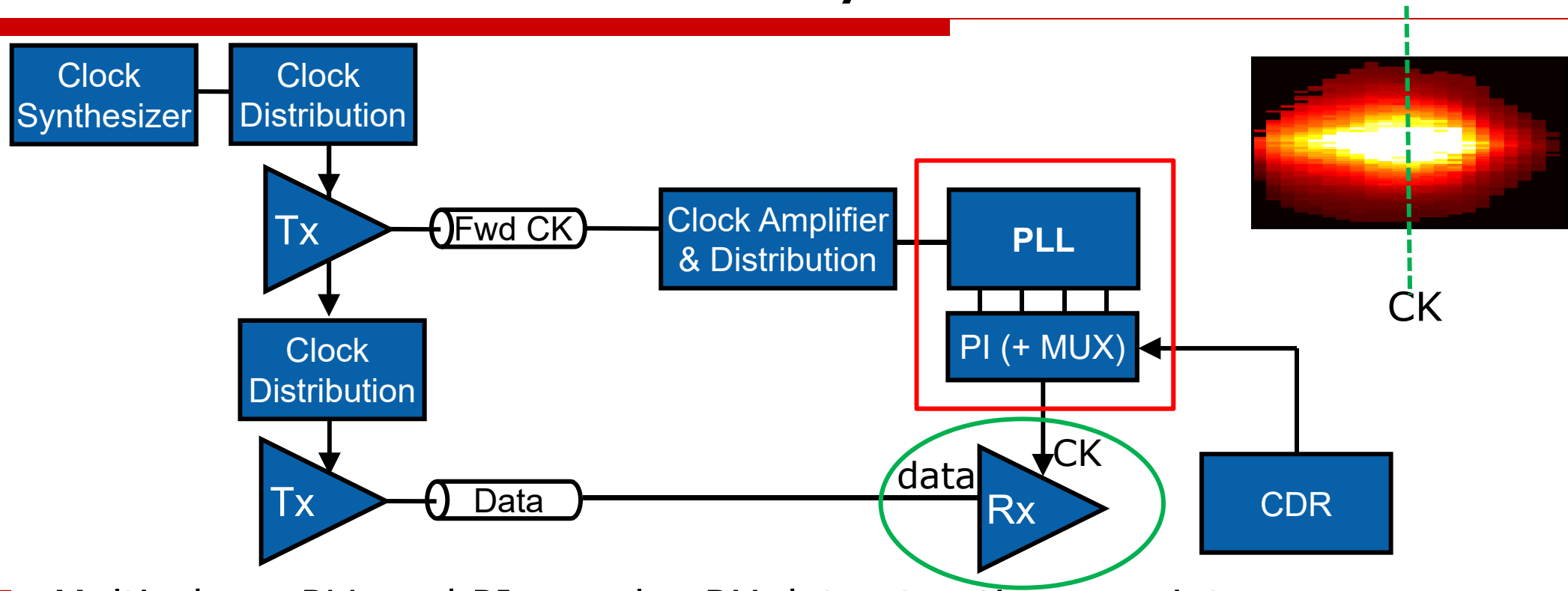


- ❑ Multi-phase PLL and PI samples RX data at optimum point
 - ✓ Low-BW CDR which sets PI code
 - ✓ Filters Fwd CK high frequency jitter
 - ✗ Reduces tracking BW between data and Fwd CK
 - ✗ Jitter accumulation

ILO-Based FC Recovery

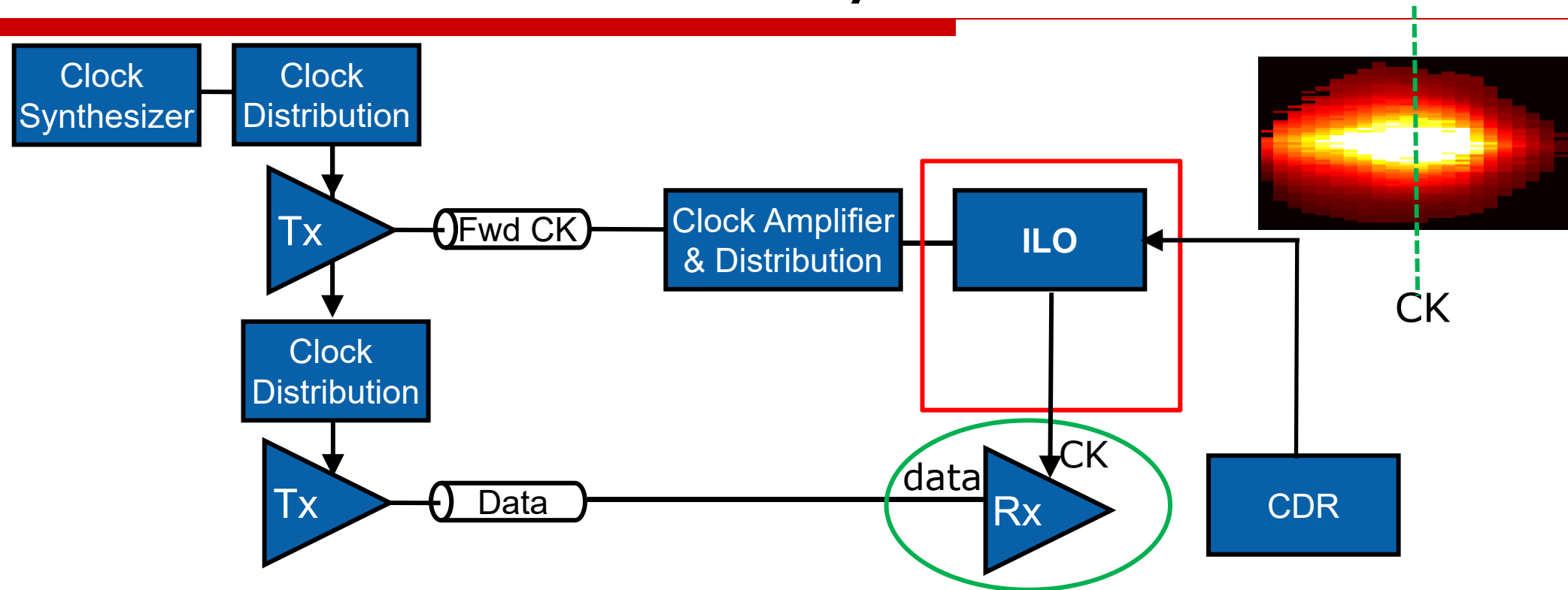


- ILO samples RX data at optimum point
 - ✓ Low-BW CDR which sets free-running frequency of VCO in ILO
 - ✓ Filters Fwd CK high frequency jitter (similar to PLL-based)
 - ✓ Higher tracking BW and less jitter accumulation than PLL-based

Embedded Clock (EC) Recovery

 



- ❑ SERDES interfaces
 - Examples: PCI-Express, USB
- ❑ Recovery method – Extract timing (phase & frequency) from data transitions
 - Timing info encoded (embedded) in data transitions → scrambling, 8b/10b, 64b/66b

PI/Mixer-Based EC Recovery

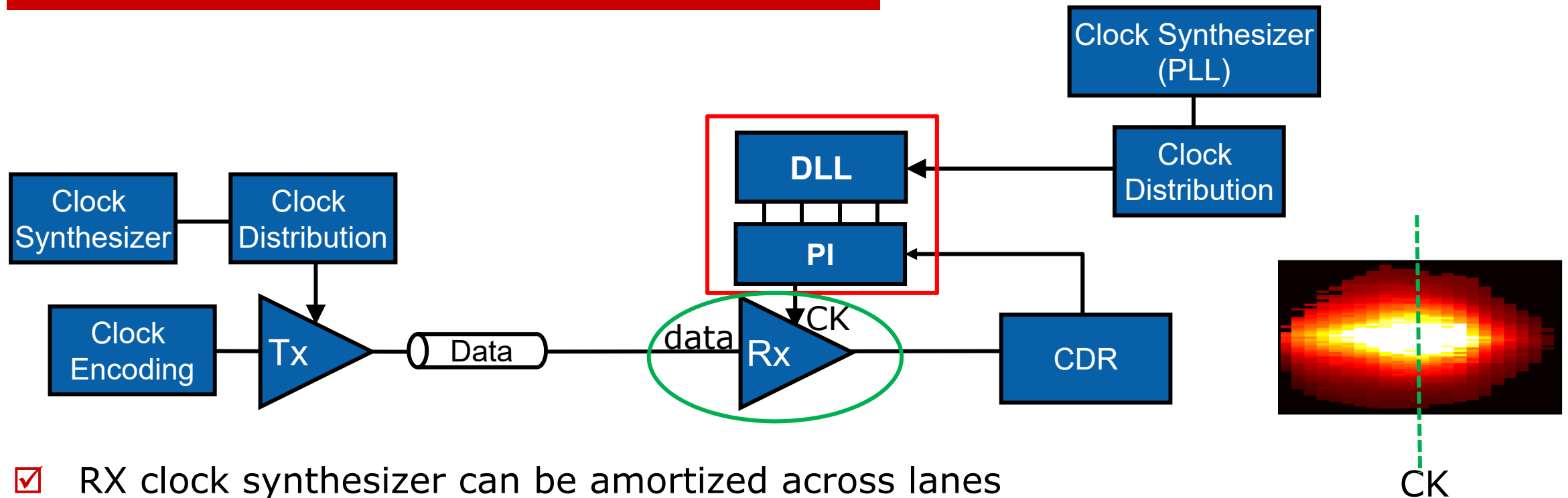

- ✓ RX clock synthesizer can be amortized across lanes
- ✗ Jitter accumulation and delay variation on RX clock path
- ✓ No Jitter accumulation in local CDR
- ✗ CDR must handle frequency difference between 2 clock domains
- ✗ Dynamic glitch in PI must be addressed


VCO-Based EC Recovery

  

- ✓ One clock domain, within local RX
- ✗ VCO jitter accumulation
- ✗ Injection locking concern
- ✗ Larger area compared to PI-based

Jitter Tolerance Comparison

 - ❑ DLL-based FC achieves best tolerance to input jitter (especially at higher frequency)
- ❑ VCO-based EC shows the worst tolerance to input jitter



Clock Recovery Summary


- Clock recovery architecture is often defined by standard/specification
- FC achieves better jitter and power performance, at cost of an additional clock channel
- Different architecture considerations for FC and EC
 - Tracking bandwidth and jitter performance
 - Power and area tradeoffs

Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management

Process Scaling

 - Data rate scaling enabled in part by process scaling
 - Past: optimized for performance/bandwidth
 - Present: optimized for power
- Process variation increases by scaling due to smaller device area
- Interleaving techniques to mitigate process limitation
 - Complex multi-phase clocking circuits
 - Variation-tolerant techniques such as duty-cycle & multi-phase correction




$$\sigma V_T = \frac{1}{\sqrt{2}} \left(\frac{C_2}{\sqrt{W_{eff} \cdot L_{eff}}} \right)$$


K. J. Kuhn, "Reducing variation in advanced logic technologies: Approaches to process and design for manufacturability of nanoscale CMOS," IEDM, Dec. 2007

Clocking in Interleaving Architecture


Full-rate clock

 

1/2-rate clock

 

1/4-rate clock

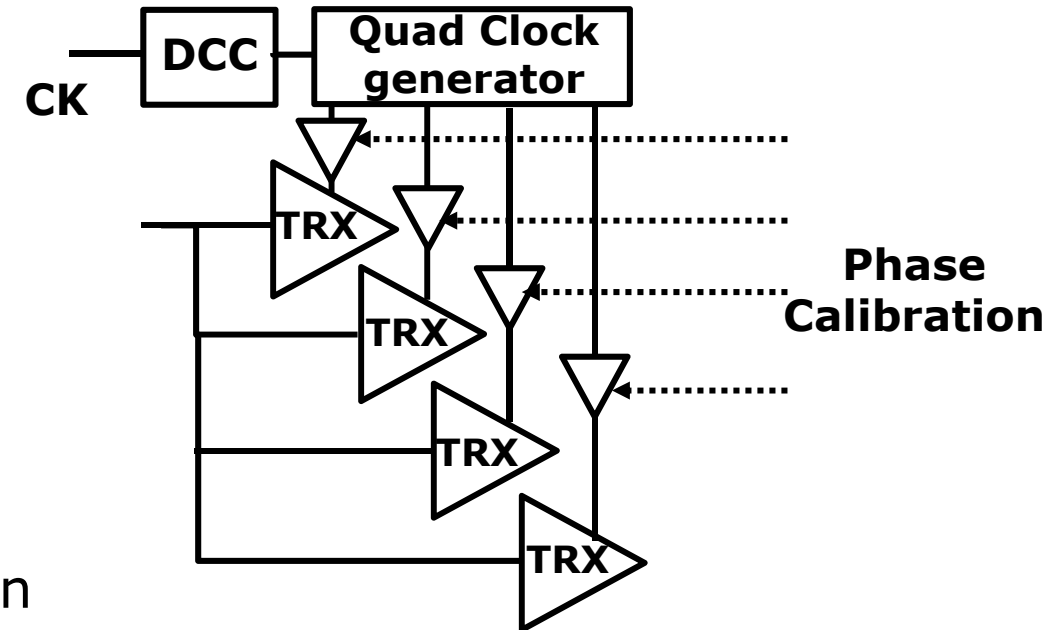


- ❑ Interleaving to alleviate process BW limitation
- ❑ Additional complexity of clock circuit design & calibration
 - Duty-cycle correction
 - Multi-phase clock generator (such as quadrature phases)

Clock calibration to detect/correct for process variation induced error


Quadrature Clocks in Wireless Applications

- ❑ Quadrature (IQ) clock phases at mm-wave
- ❑ Higher-order modulation (16/32/64-QAM)
- ❑ I & Q mismatches in mmwave
 - Constellation error
 - Calibration is required

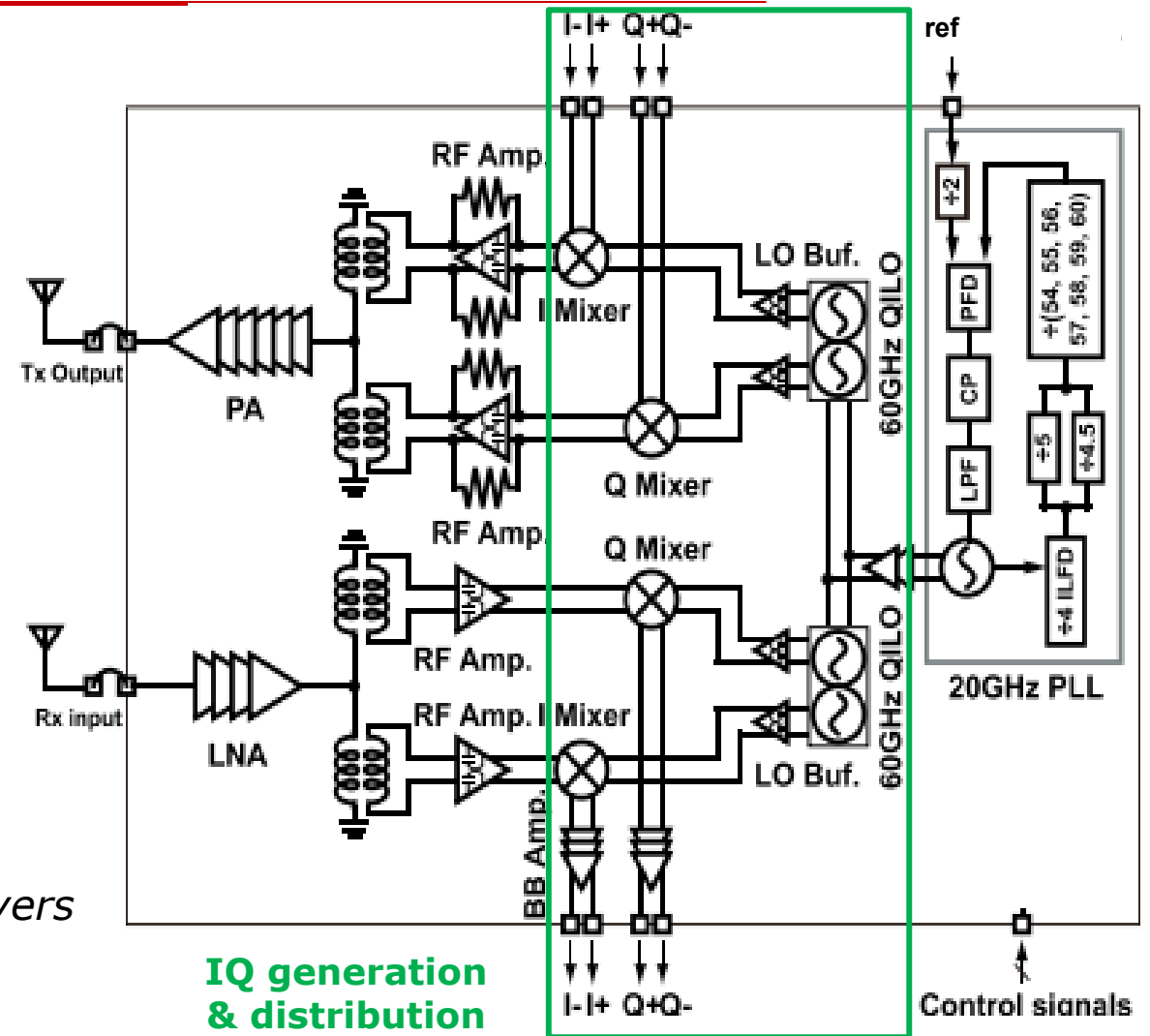R. Wu, et al., "64-QAM 60-GHz CMOS Transceivers for IEEE 802.11ad/ay," JSSC, Nov. 2017




Conventional Duty-Cycle Detector (DCD)

 

- ❑ Clock is sampled by an amplifier & low-pass filtered to generate error
- ❑ Error code drives a variable offset amplifier (VOA) to correct for DCE
- ❑ Feedback Loop is mostly analog
 - Self-calibration of “Amplifier” to correct for induced offset
 - Large analog loop filter

All-Digital DCD

 


- ❑ VCO runs asynchronously with clock under test to generate uniform edge density
- ❑ Average-based technique
- ❑ Duty cycle error (DCE) is equal to probability* of "1s"
- ❑ Differential measurement limits effect of sampler non-idealities

$$\text{DCE} \propto (\text{Prob. of "1s" for ck0} - \text{Prob. of "1s" for ck180})$$


* ratio of measured "1s" to total VCO cycles

DCC & Quadrature Error Detector

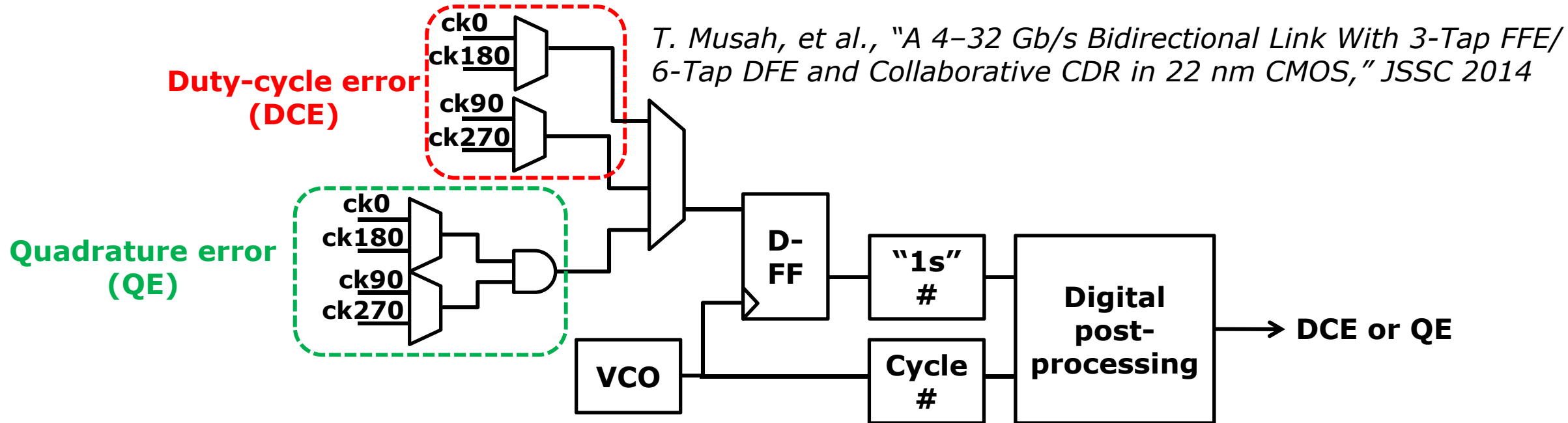

- ❑ Fully digital implementation, including VCO
- ❑ Small area, mainly occupied by counters
 - Counter bits set measured accuracy
- ❑ DCC/QEC can be done during training and/or as background calibration


Delay Analyzer for PI Characterization

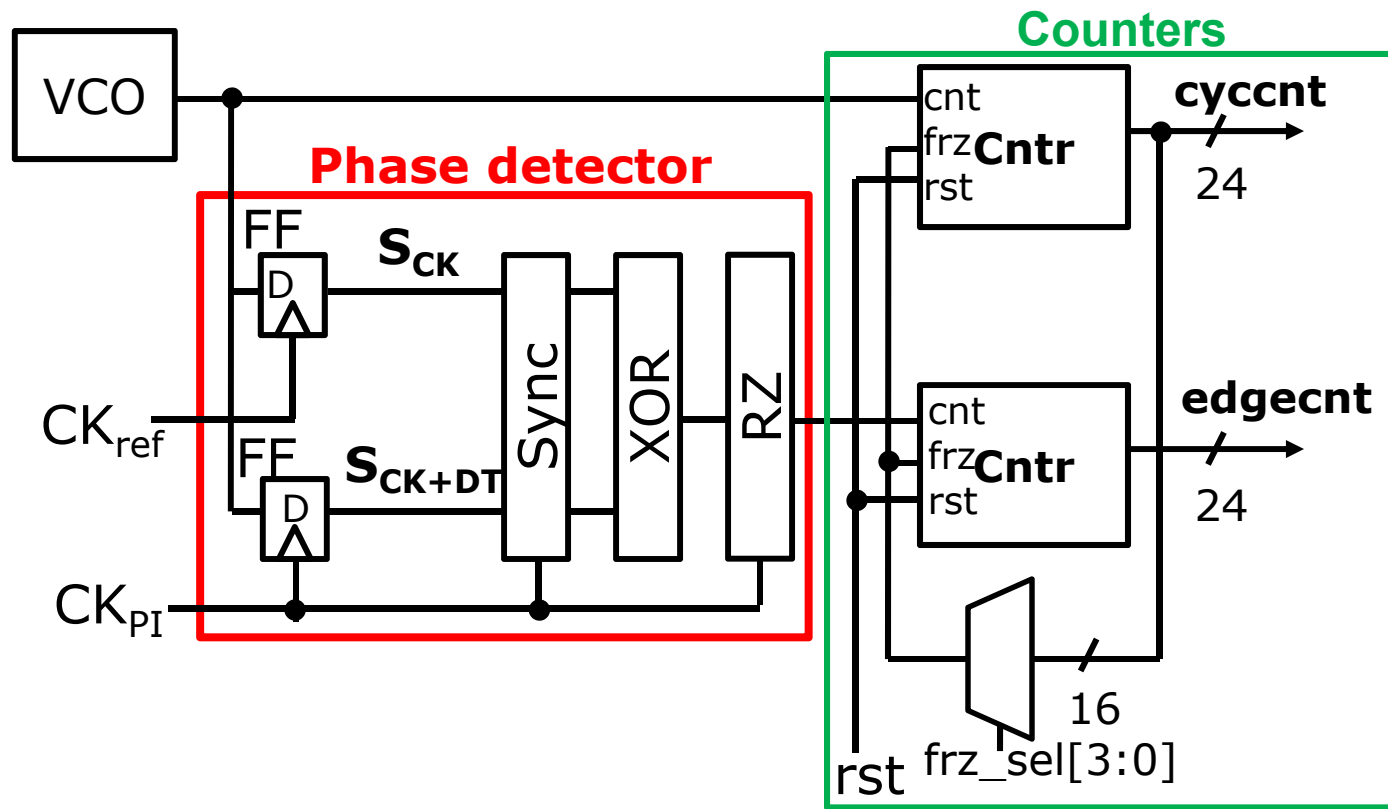


M. Mansuri, et al., "An On-Die All-Digital Delay Measurement Circuit with 250fs Accuracy," VLSI 2012

- PI characterization to calibrate and correct for INL and DNL
- Phase detector + VCO and counters (similar to DCD/QED)

Delay Analyzer for PI Characterization

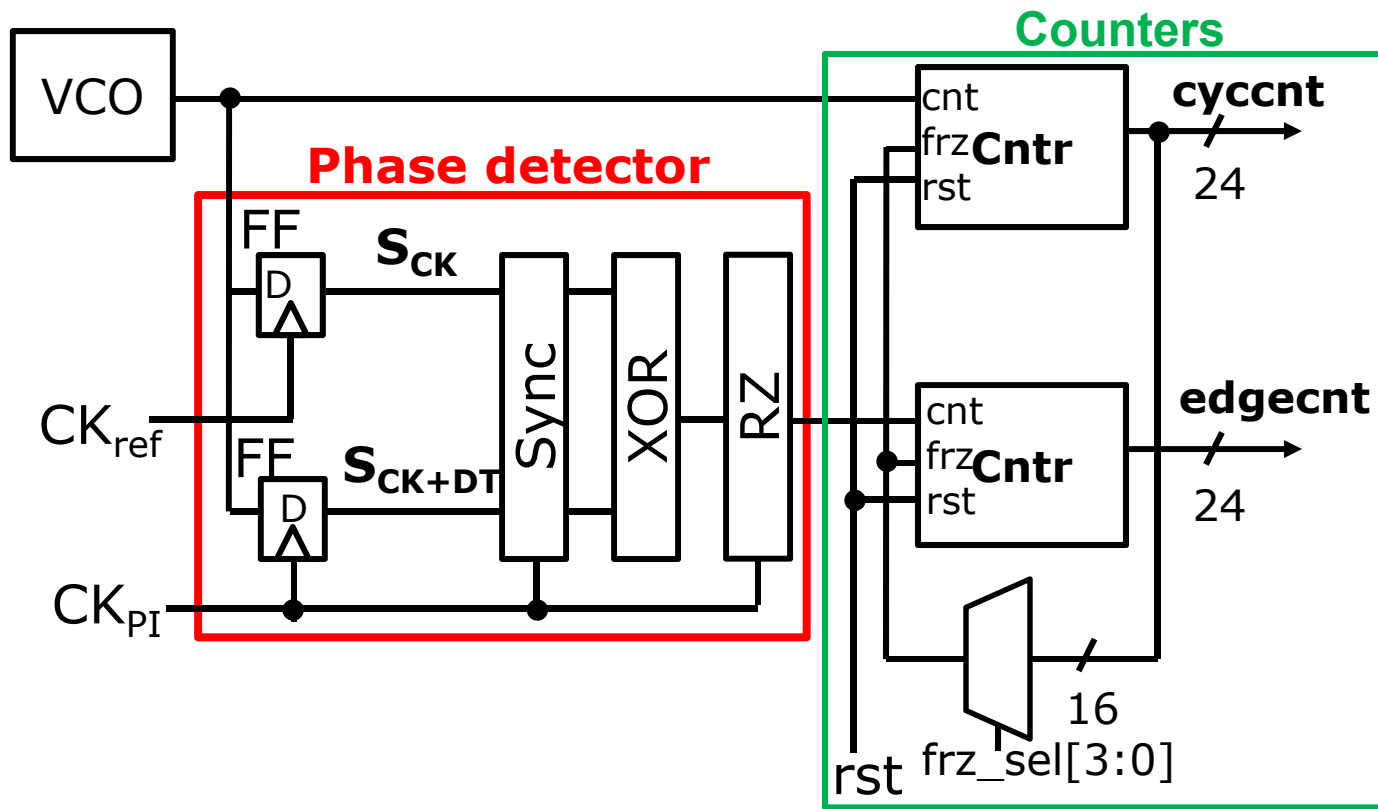

 M. Mansuri, et al., "An On-Die All-Digital Delay Measurement Circuit with 250fs Accuracy," VLSI 2012



- PI characterization to calibrate and correct for INL and DNL
- Phase detector + VCO and counters (similar to DCD/QED)


Clock Calibration Summary

- ❑ Clock calibration is a must to mitigate process variation
- ❑ In-situ measurement & correction
- ❑ Accuracy tradeoffs
 - Measurement time (average-based implementation)
 - Detector residual self-induced error
- ❑ Small area and low leakage
- ❑ All digital & scalable
 - No analog circuit or bias
 - Digital filter instead of RC filter

Outline

- Clock quality terminology
- Clocking architectures and circuits
 - Clock synthesizer
 - VCO
 - Clock distribution
 - Clock recovery
- Clock calibration
- Clock amortization and power management


Clocking Circuits Power

 


■ TX clock ■ RX clock ■ TX ■ RX

- Clocking circuits power is a good portion of system power
 - Example: clocking is 67% of total power
- Innovation in clocking circuits and amortization
- Power management

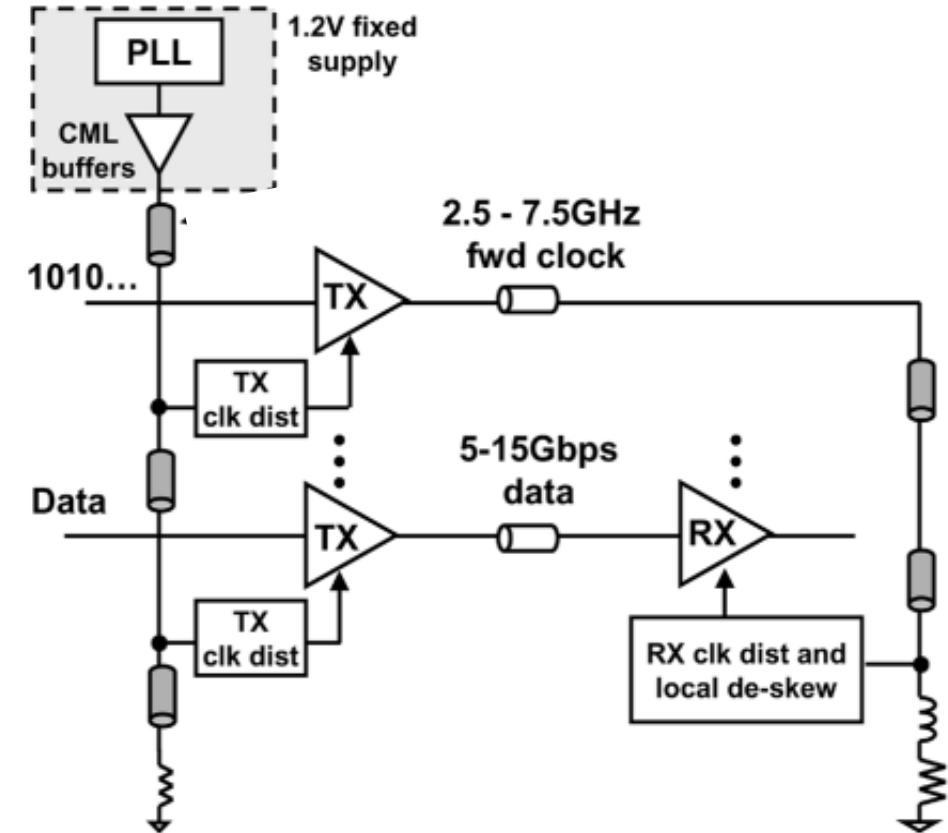G. Balamurugan, et al., "A Scalable 5–15 Gbps, 14–75 mW Low-Power I/O Transceiver in 65 nm CMOS," JSSC 2008




Clock Power Amortization

 


- Sharing clock to reduce clock power & area overhead
 - Bundle clock & collaborative CDR to share across lanes
 - Power-efficient clock distribution
 - Example: clocking power reduces from 67% to 45%

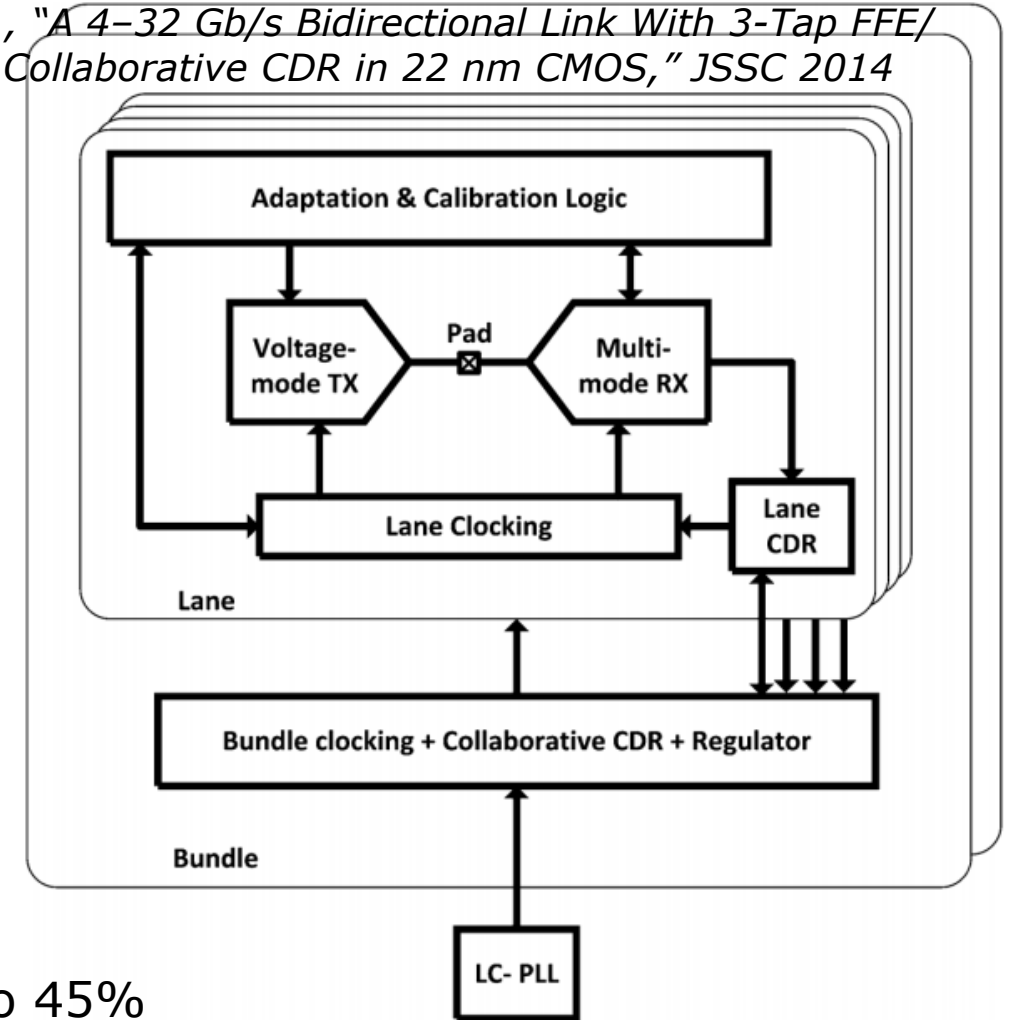T. Musah, et al., "A 4–32 Gb/s Bidirectional Link With 3-Tap FFE/6-Tap DFE and Collaborative CDR in 22 nm CMOS," JSSC 2014



Clock Power Management

Hypothetical Link BW Demand

 

F. O'Mahony et al., "A 47x10Gb/s 1.4mW/(Gb/s) parallel interface in 45nm CMOS," JSCC, Dec. 2010

- ❑ Various power states: sleep, standby, active
- ❑ Minimum static power
- ❑ Frequency scaling as BW demand changes (to non-linearly save power)
- ❑ Fast frequency hopping and wakeup time (to reduce transition latency)
 - Challenges due to feedback loop latency (PLLs, DLLs, LDOs,...)

Clock Amortization and Power Management Summary

- ❑ Clocking power optimization to meet overall system power budget
- ❑ Global clock amortization among multi lanes and minimizing local clock power
- ❑ Power-efficient clock distribution
- ❑ Clocking design tradeoffs to enable fast wakeup time and frequency hopping for optimum power management

Summary

- ❑ Accurate clocking solutions are key enablers to aggressively scale data rate
- ❑ Clocking architecture/design tradeoffs, such as clock synthesis, recovery and distribution, for optimum jitter/phase noise and power performance
- ❑ Variation-tolerant clocking circuits to mitigate process scaling challenges
- ❑ Clocking circuit innovation and amortization to reduce power/area overhead
- ❑ Fast clock wakeup techniques with minimum standby power to enable aggressive power management

References

- ❑ B. Casper et al., "Clocking analysis, implementation and measurement techniques for high-speed data links-A tutorial," TCAS-I, Jan. 2009.
- ❑ J. A. McNeill, "Jitter in Ring Oscillators," JSSC 1997.
- ❑ A. Hajimiri et al., "Jitter and phase noise in ring oscillators," JSSC 1999.
- ❑ A. Demir et al., "Phase noise in oscillators: A unifying theory and numerical methods for characterization," DAC 1998.
- ❑ A. Hajimiri, "Noise in phase-locked loops," SSMSD, Feb. 2001.
- ❑ J. Maneatis, "Low-jitter process-independent DLL and PLL based self-biased techniques", JSSC, pp. 1723-1732, Nov. 1996.
- ❑ A. Sheikholeslami, "Basics of high-speed chip-to-chip and backplane signaling", ISSCC Tutorial 2008.
- ❑ T. Lee, "The Design of CMOS Radio-Frequency Integrated Circuits," Cambridge University Press, 1998, p. 458.
- ❑ B. Razavi, "Phase locking in high-performance systems," Wiley-IEEE Press, 2003.
- ❑ J. Lee, "Study of subharmonically injection-locked PLLs," JSSC 2009.

References

- ❑ T. Musah, "Wireline link standard," [Online]. Available: <https://mics.engineering.osu.edu/iostandards>
- ❑ X. Gao et al., "A low noise sub-sampling PLL in which divider noise is eliminated and PD/CP noise is not multiplied by N^2 ," JSSC, Dec. 2009.
- ❑ J. Sharma et al., "A Dividerless reference-sampling RF PLL with -253.5dB Jitter FOM and <-67dBc reference spurs," ISSCC 2018.
- ❑ A. Elshazly et al., "Clock multiplication techniques using digital multiplying delay-locked loops," JSSC 2013.
- ❑ S. Shekhar et al., "Strong injection locking in low-Q LC oscillators: modeling and application in a forwarded-clock I/O receiver," JSSC 2009.
- ❑ E. Alon et al., "Replica Compensated Linear Regulators for Supply-Regulated Phase-Locked Loops", JSSC 2006.
- ❑ Y. Lu et al., "A 0.65ns-response-time 3.01ps FOM fully-integrated low-dropout regulator with full-spectrum power-supply-rejection ...," ISSCC 2014.
- ❑ J-H Seol et al. "An 8Gb/s 0.65mW/Gb/s forwarded-clock receiver using an ILO with dual feedback and quadrature injection scheme," ISSCC 2013.

References

- ❑ F. O'Mahony et al., "A 27 Gb/s forwarded-clock I/O receiver using an injection-locked LC-DCO in 45nm CMOS," ISSCC 2008.
- ❑ J. Bulzacchelli et al., "A 28 Gb/s 4-tap FFE/15-tap DFE serial link transceiver in 32nm SOI CMOS technology," JSSC 2012.
- ❑ G. Balamurugan et al., "A scalable 5-15 Gbps, 14-75 mW low-power I/O transceiver in 65nm CMOS," JSSC 2008.
- ❑ B. Casper et al., "A 20Gb/s forwarded clock transceiver in 90nm CMOS," ISSCC 2006.
- ❑ J. Jaussi et al., "A 20Gb/s embedded clock transceiver in 90nm CMOS", ISSCC 2006.
- ❑ M. Mansuri et al., "A Scalable 0.128-1Tb/s, 0.8-2.6pJ/bit, 64-lane Parallel I/O in 32nm CMOS," JSSC 2013.
- ❑ T. Musah et al., "A 4-32 Gb/s Bidirectional Link with 3-Tap FFE/6-Tap DFE and Collaborative CDR in 22nm CMOS" JSSC 2014.
- ❑ F. O'Mahony et al., "A 47x10Gb/s 1.4mW/(Gb/s) parallel interface in 45nm CMOS," IEEE J. Solid-State Circuits, vol. 45, no. 12, pp. 2828-2837, Dec. 2010.
- ❑ T. Hsueh et al., "A 25.6Gb/s differential and DDR4/GDDR5 dual-mode transmitter with digital clock calibration in 22nm CMOS," ISSCC 2014.

References

- M. Mansuri et al., "An on-die all-digital delay measurement circuit with 250fs accuracy," Symp. VLSI Circuits, June 2012.
- K. J. Kuhn, "Reducing variation in advanced logic technologies: Approaches to process and design for manufacturability of nanoscale CMOS," IEDM , Dec. 2007.
- S. Pellerano et al., "A Scalable 71-to-76GHz 64-Element Phased-Array Transceiver Module with 2×2 Direct-Conversion IC in 22nm FinFET CMOS", ISSCC 2019.
- R. Wu et al., "64-QAM 60-GHz CMOS Transceivers for IEEE 802.11ad/ay," JSSC 2017.
- F. O'Mahony et al., "A low-jitter PLL and repeaterless clock distribution network for a 20Gb/s link," VLSI 2006.
- G. Li et al., "Standing Wave Based Clock Distribution Technique with Application to a 10 × 11 Gbps Transceiver in 28 nm CMOS," IEEE Asian Solid-State Circuits Conference 2015.
- W.-H. Ma et al., "A 5.5GS/s 28mW 5-bit Flash ADC with Resonant Clock Distribution," ESSCIRC 2011