
Introduction to ADCs/DACs: Metrics, Topologies, Trade Space, and Applications

Boris Murmann
Stanford University
Stanford, CA, USA
murmann@stanford.edu

February 2022

Self Introduction


- PhD from UC Berkeley in 2003
- Professor at Stanford University since 2004
- Interests
 - Sensor interfaces
 - Data converters
 - High-speed communication
 - Embedded machine learning



Boris Murmann

Objective

 - Prepare attendees for subsequent deep-dive presentations
 - What are the relevant performance metrics?
 - What are the basic converter topologies?
 - What are the performance trends and limitations?
 - What are the application drivers and considerations?




Outline

- ADCs
 - Metrics
 - Architectures
 - Speed, resolution, energy tradeoffs and trends
 - Building block considerations
 - Application aspects

- DACs
 - Output spectrum & metrics
 - Introduction to current steering
 - Timing and jitter requirements
 - Performance trends
 - Application aspects



Generic A/D Interface

 



Δ = Step size (LSB size)
 ϵ_q = Quantization error

Signal-to-Quantization Noise Ratio for
 B-bit quantizer and full-scale sinusoid
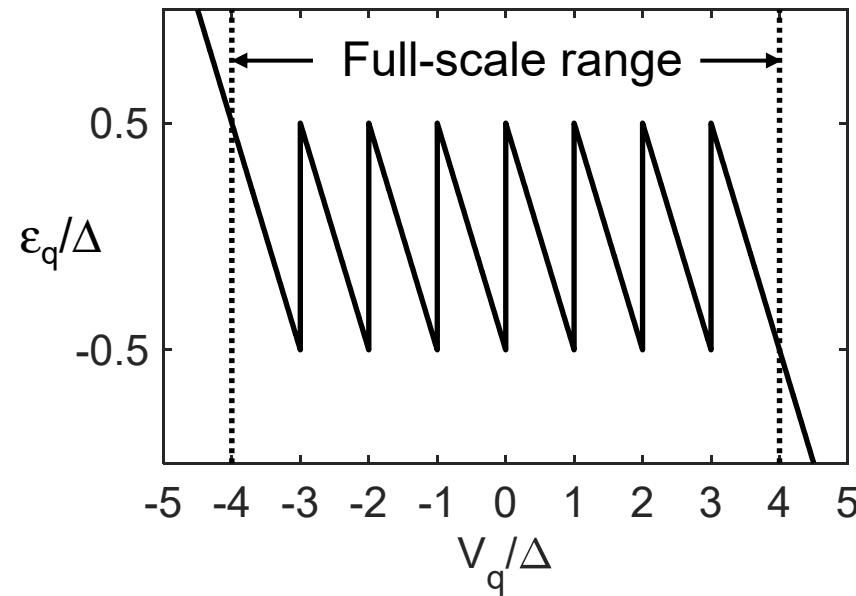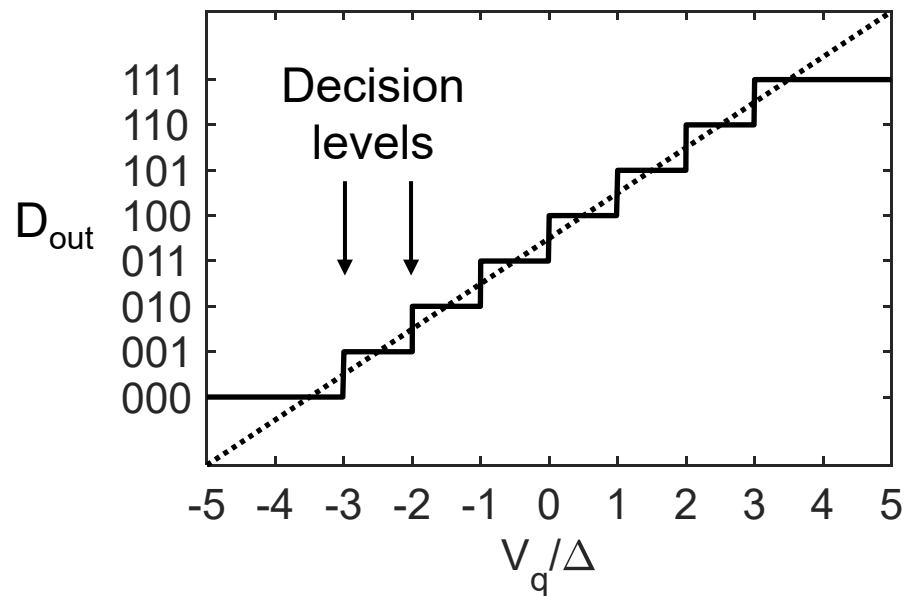
$$SQNR = 6.02 \times B + 1.76 \text{ dB}$$




Static Performance Metrics

  


- Differential nonlinearity (DNL)
 - Relative errors in code width
- Integral nonlinearity (INL)
 - Decision level shifts relative to straight line → running sum of DNL

ADC Spectral Performance Analysis

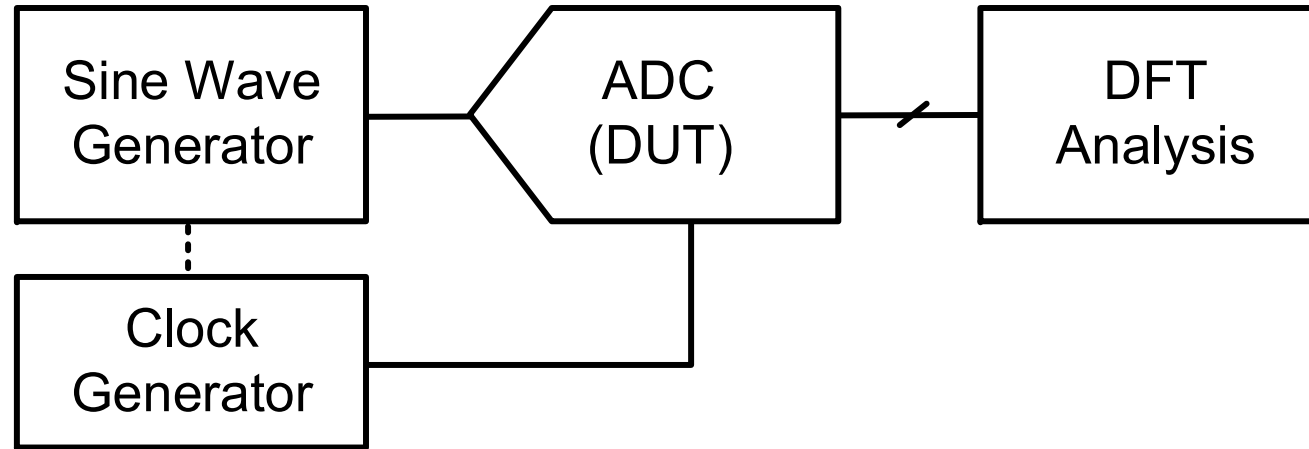

- ❑ Discrete Fourier transform output lets us calculate several useful metrics
 - Signal-to-Noise Ratio (SNR)
 - Signal-to-Noise and Distortion Ratio (SNDR)
 - Spurious-Free-Dynamic Range (SFDR)
 - Harmonic Distortion (HD)

Basic Single-Tone Metrics for ADCs

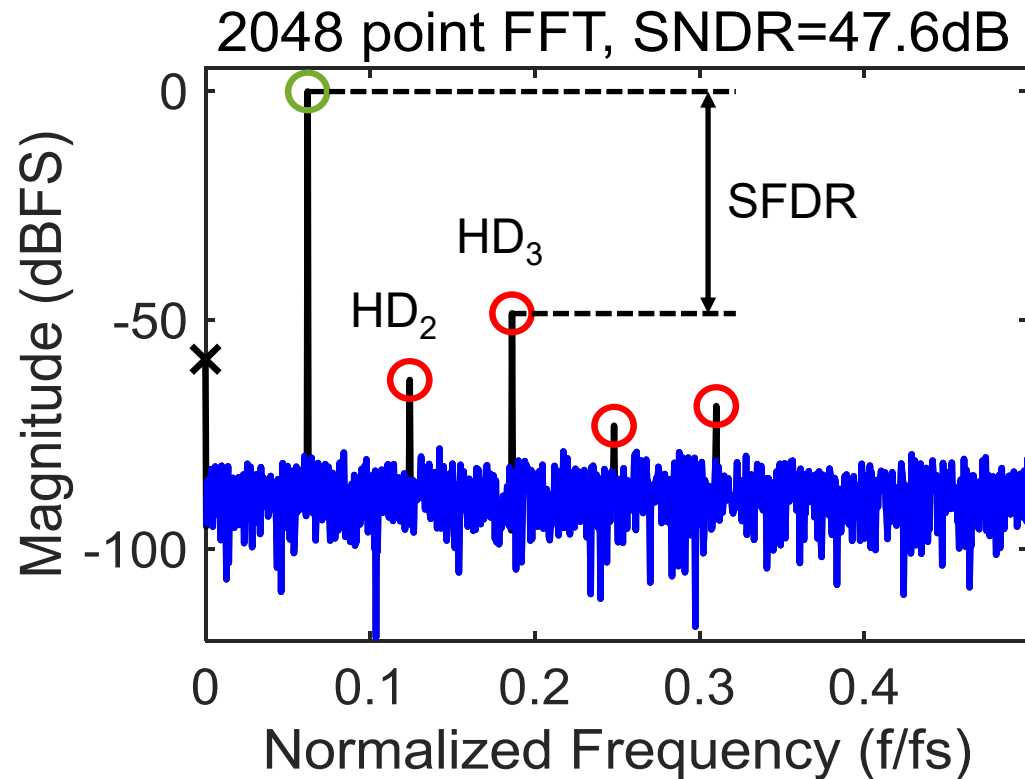


$$SNR = \frac{P_{Sig}}{P_{Noise}}$$

$$SNDR = \frac{P_{Sig}}{P_{Noise} + P_{HD}}$$

$$ENOB = \frac{SNDR(dB) - 1.76}{6.02}$$

$$SFDR = \frac{P_{Sig}}{P_{largest\ spur}}$$

Relationship Between SFDR and INL

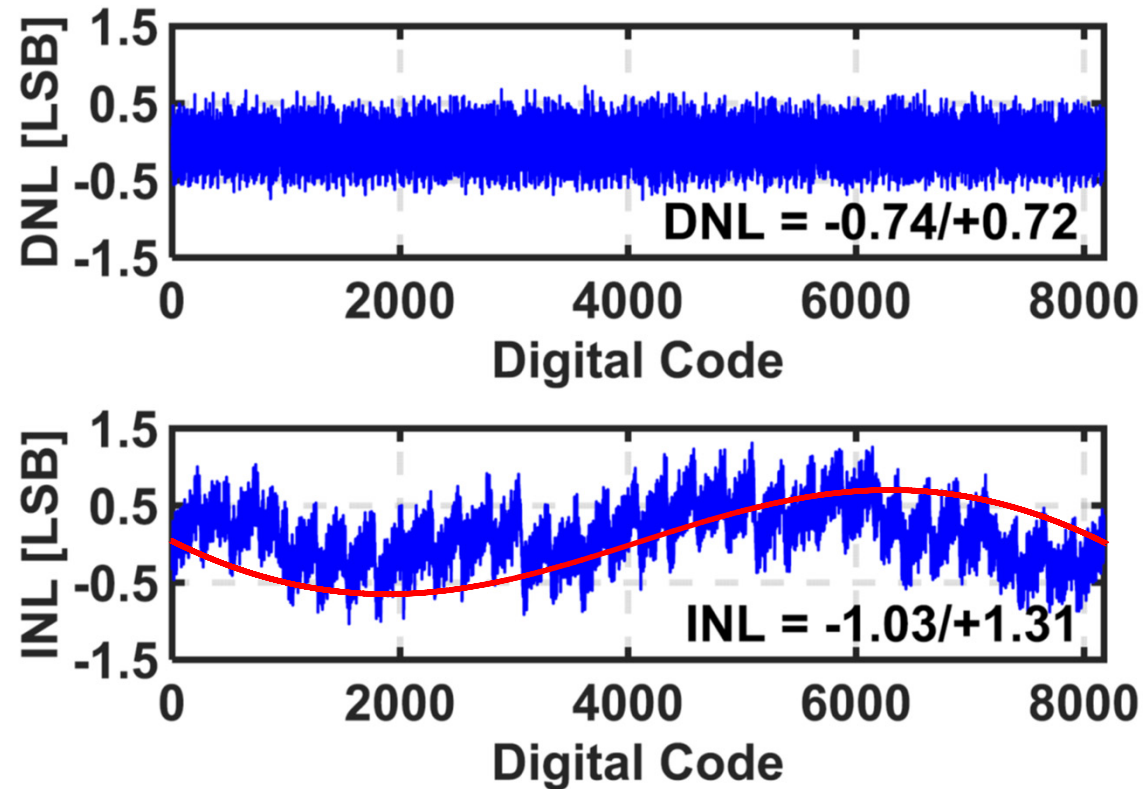

- INL often shows major transitions and cubic/quadratic bows
- For visible bows, we can roughly estimate SFDR using


$$SFDR \approx -20 \log \left(\frac{INL_{fit}}{2^B} \right)$$

$$SFDR \approx -20 \log \left(\frac{0.5}{2^{13}} \right) = 84 \text{ dB}$$

(Measured SFDR is 89 dB)

[Zhang, ISSCC 2019]

Dynamic Range (DR)

 


[Lin, ISSCC 2021]


- Ratio of strongest and weakest signal (@SNR=0dB)
- $DR \geq \text{Peak SNR, SNDR}$

The Need for Advanced Metrics

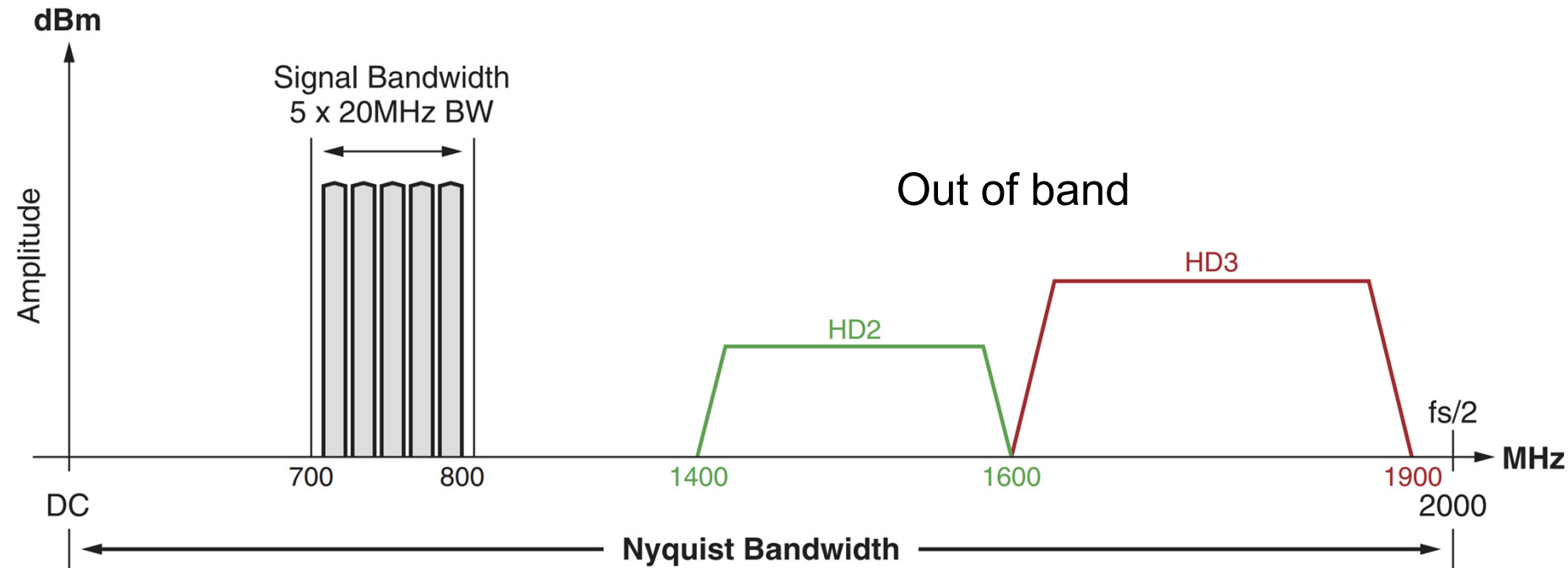- ❑ Consider RF ADC for LTE [Xilinx, 2019]
- ❑ Single-tone metrics like SFDR are irrelevant




Two-Tone Test

 

[Xilinx, 2019]


Adjacent Channel Leakage Ratio (ACLR)

 - Ratio of modulated signal power and power leaked into adjacent channels



[Xilinx, 2019]

Noise Spectral Density (NSD)

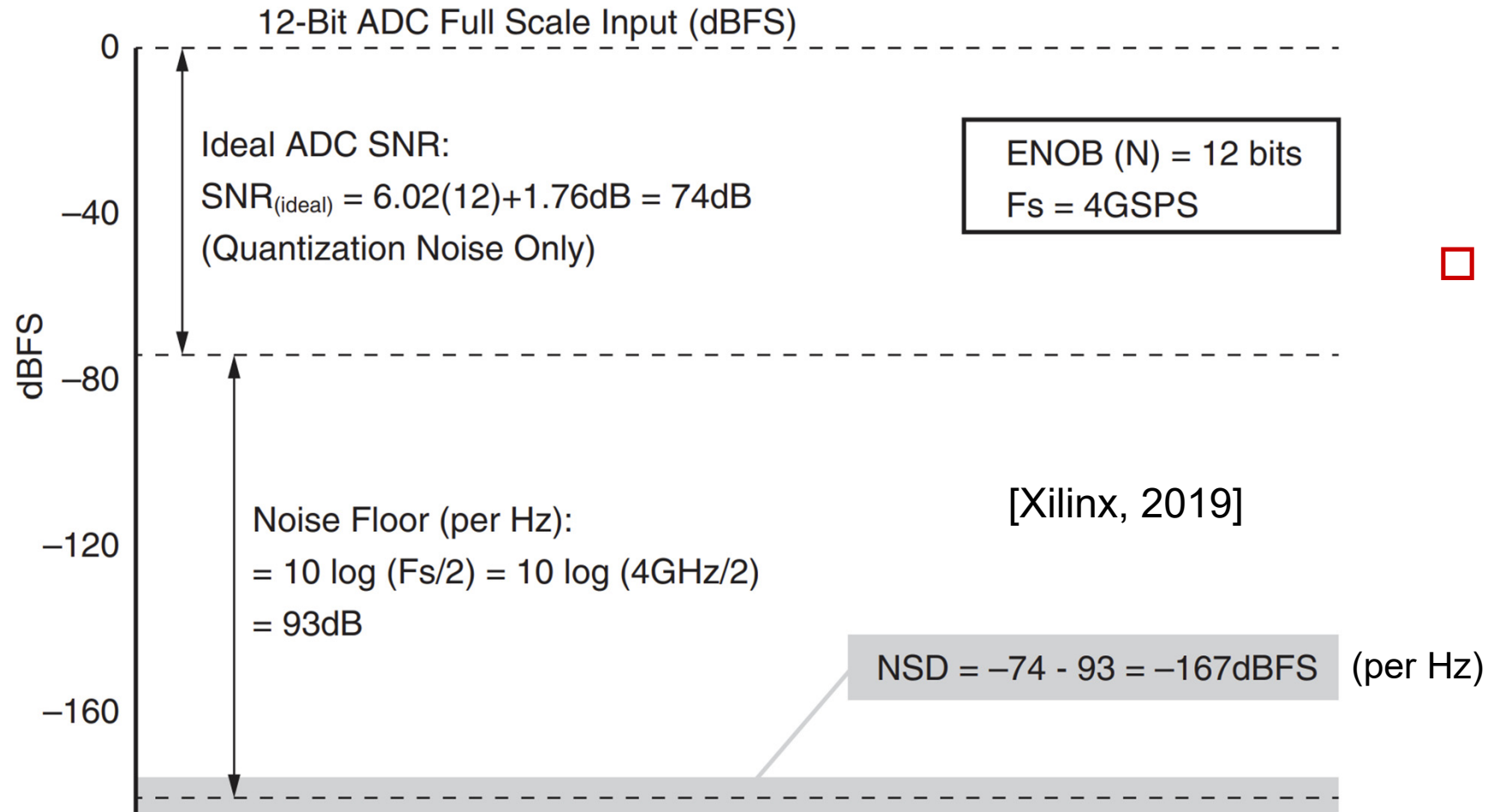


- Useful for estimating in-band noise within a fraction of the Nyquist band

Outline

- ADCs
 - Metrics ✓
 - Architectures
 - Speed, resolution, energy tradeoffs and trends
 - Building block considerations
 - Application aspects


- DACs
 - Output spectrum & metrics
 - Introduction to current steering
 - Timing and jitter requirements
 - Performance trends
 - Application aspects

Rudimentary Architecture: Flash ADC

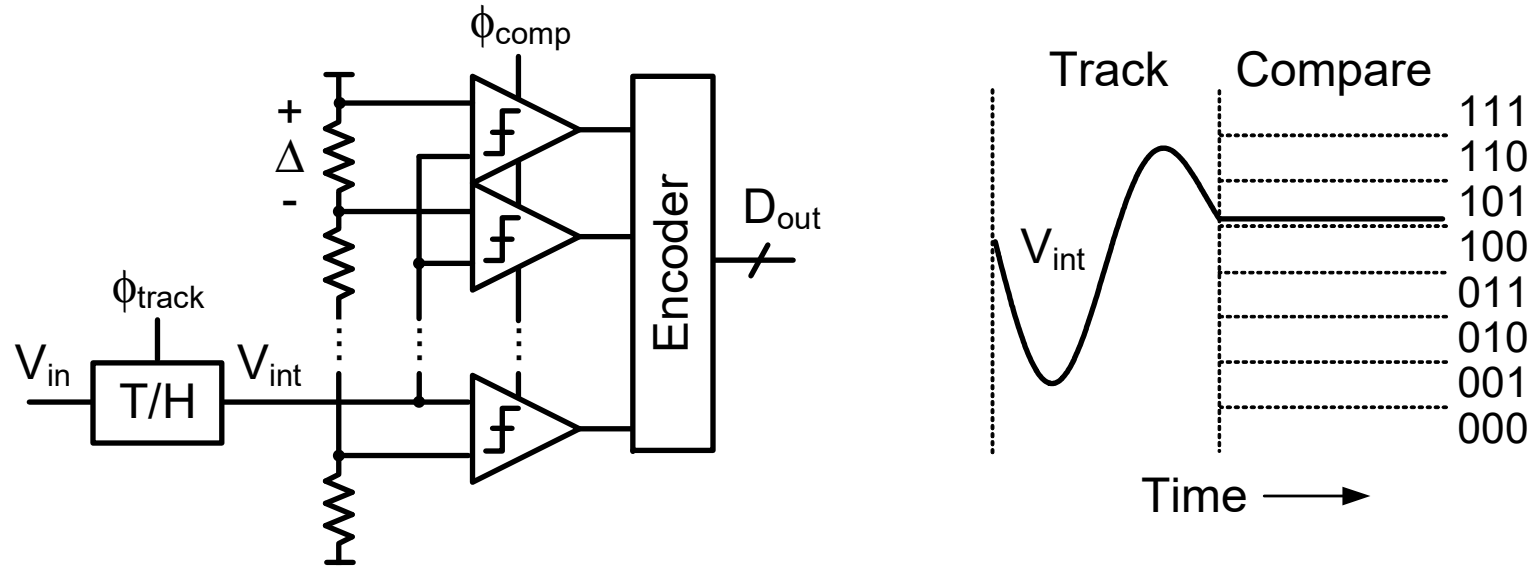


- ❑ Compare sampled input to all decision levels in parallel
- ❑ Fast, but requires $2^B - 1$ comparators
- ❑ Typically use for $B \leq 6$
 - Managing comparator offset becomes major challenge for larger B

Essence of Most Other ADC Architectures

 


- ❑ Fidelity typically limited by circuits connected to summing node
- ❑ DAC is usually a major pain point
 - Especially in CT $\Delta\Sigma$ modulators

Successive Approximation Register ADC

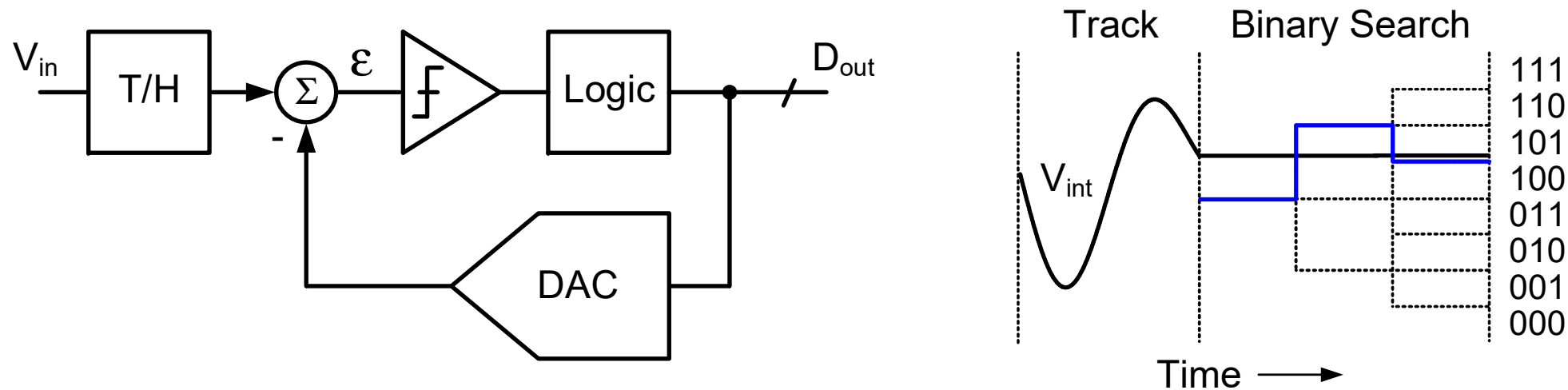

- ❑ Usually employ only one comparator
- ❑ Bits are determined sequentially; conversion time increases $\sim B$
- ❑ Linearity determined by sub-DAC
- ❑ Comparator noise a significant issue for $B > 10$
 - Can introduce redundancy to relax specs (see Pieter Harpe's talk)


Published Data (ISSCC & VLSI Symposium)

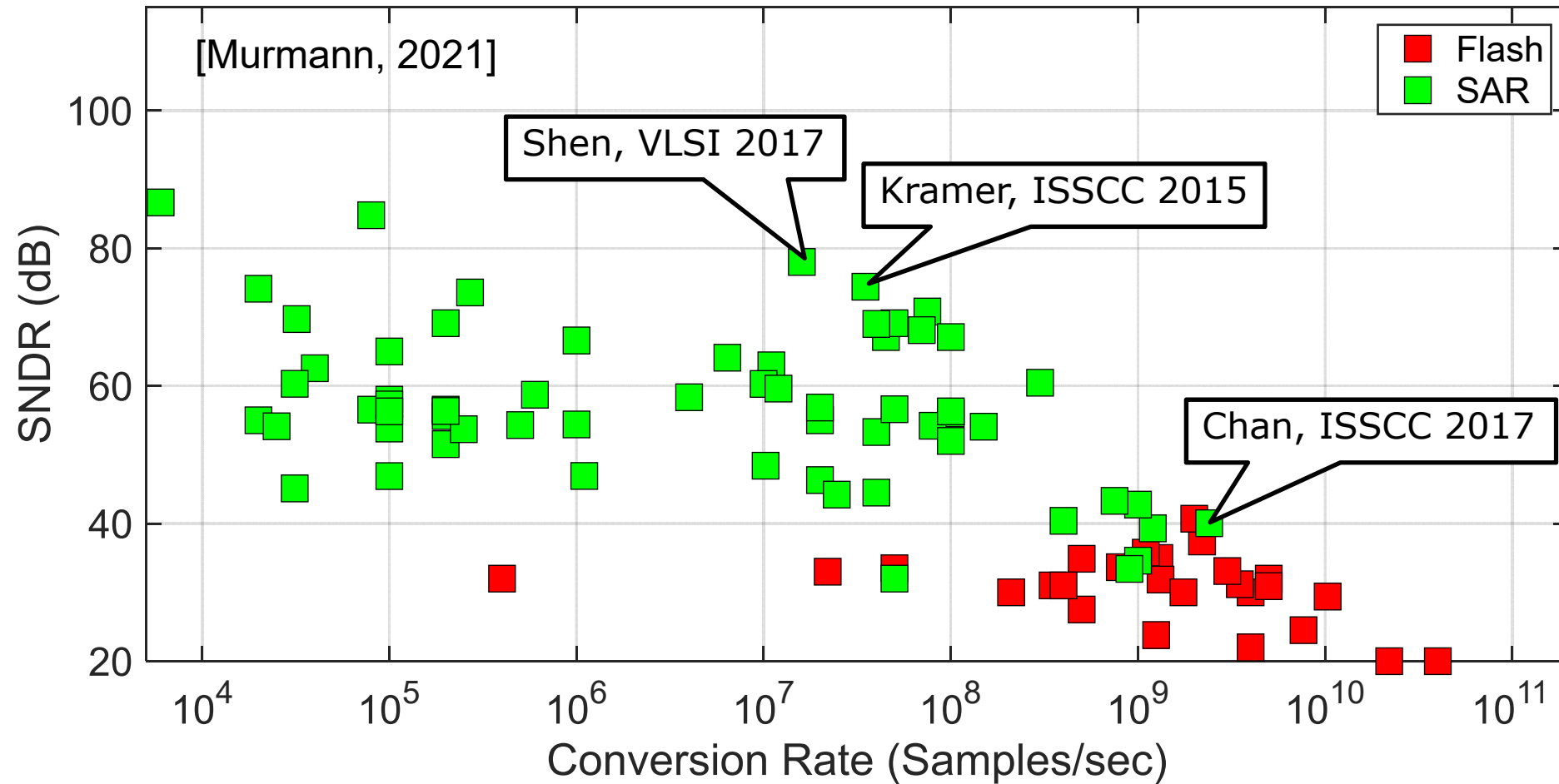

Pushing the Envelope


- Higher resolution
 - Oversampling and noise shaping ($\Delta\Sigma$ modulators)
- Higher speed
 - Pipelining
 - Time interleaving
- Current trend
 - Mixing and matching all the above options, and across all architectures
 - “Hybrid ADCs”

Oversampling and Noise Shaping

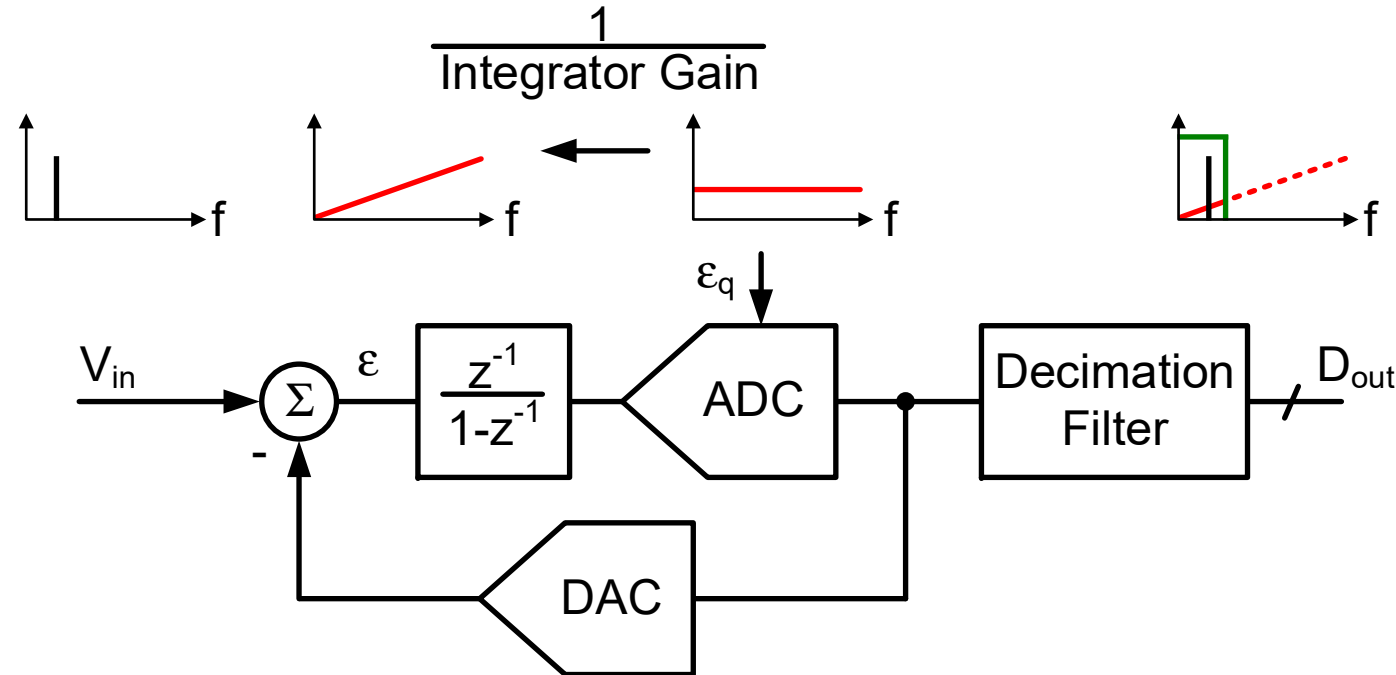

- ❑ Integrator forces ε to zero near DC
- ❑ Many variants exist (DT/CT, high-order loop filters, bandpass, ...)
- ❑ Performance typically set by DAC and first stage of loop filter


Equivalent Model Using Error Feedback

 

- ❑ Quantization error from previous input is subtracted from current input ($1-z^{-1}$)
 - Highpass filtering as shown on previous slide
- ❑ Previously used only for $\Delta\Sigma$ DACs, due to high feedback coefficient sensitivity
 - But, workable for low-order with high-resolution quantizers
 - First noise shaping SAR ADC by [Fredenburg & Flynn, ISSCC 2012]


Plugging in a SAR ADC

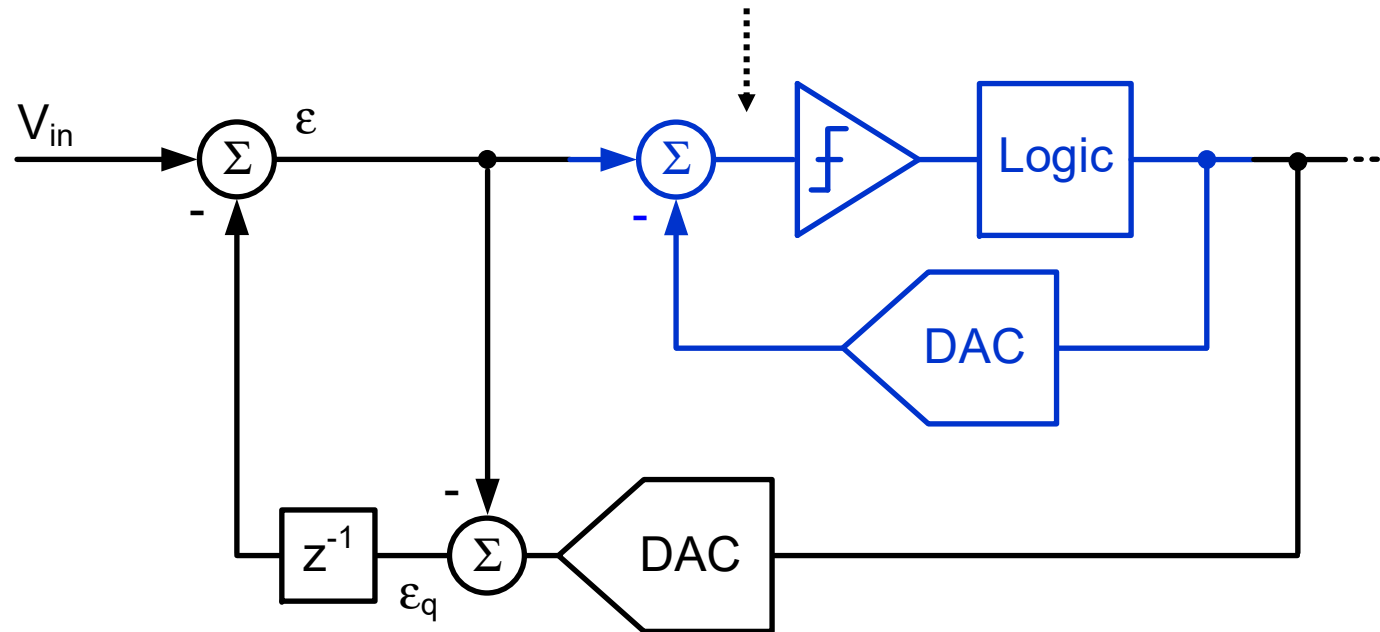ε_q is available here for free* after SAR iterations




*Typically need to run an extra cycle to feed back final bit decision

Plugging in a SAR ADC

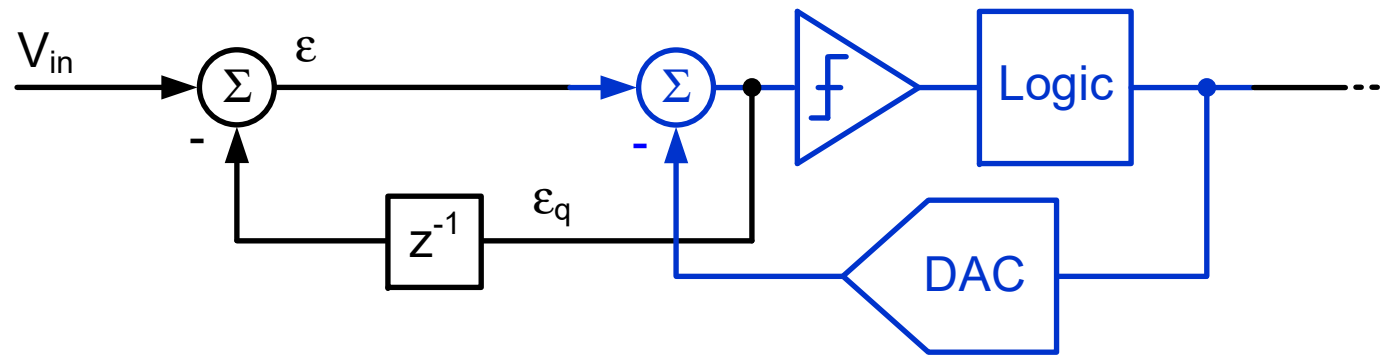


- Key is to find an efficient circuit realization that minimizes active components and allows for extensions such as second-order noise shaping
 - See e.g. [Li & Sun, ISSCC 2018]; more in Nan Sun's presentation


Published Data (ISSCC & VLSI Symposium)

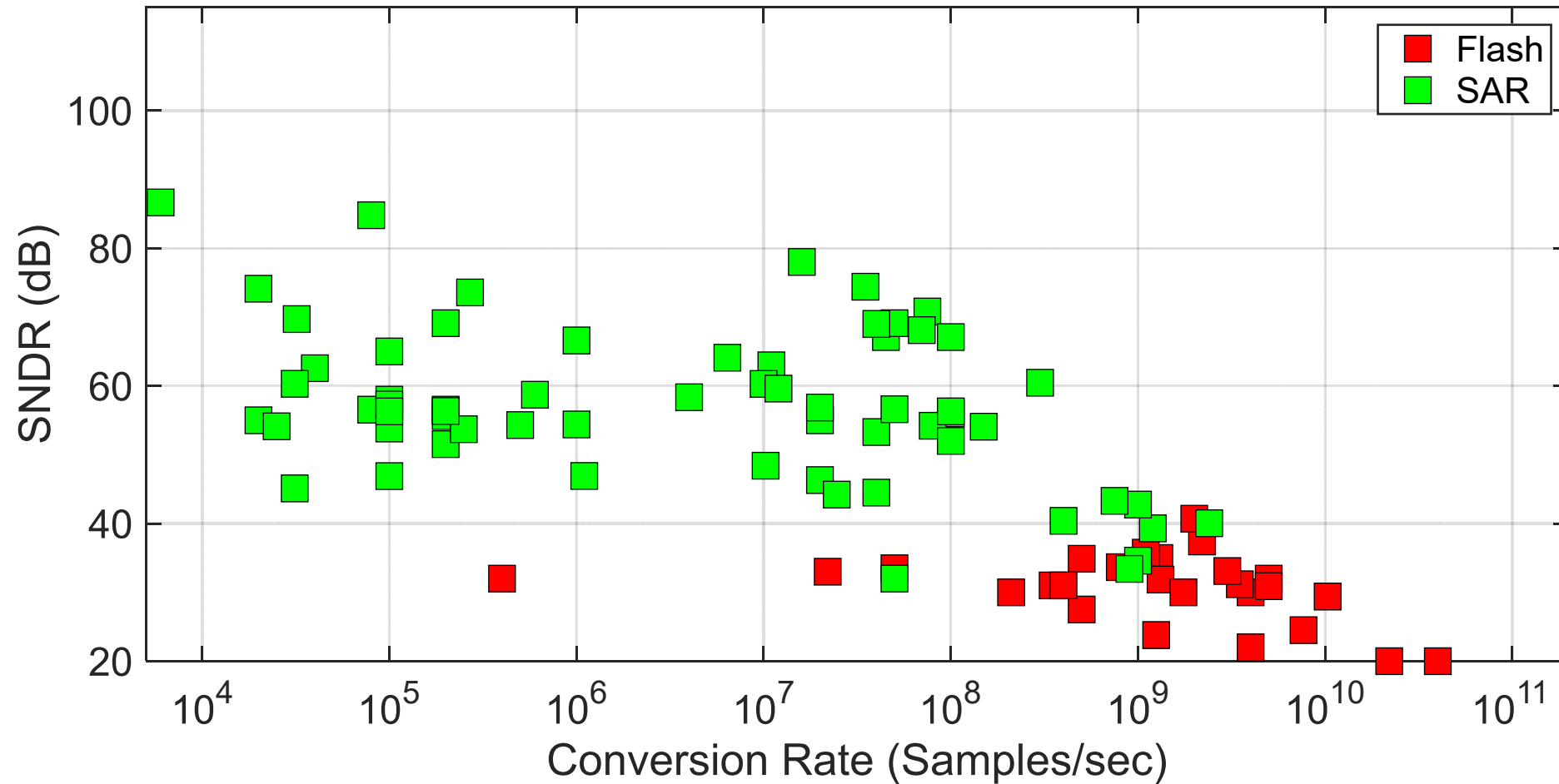

Adding "Standard" $\Delta\Sigma$ ADCs

 

Adding Noise-Shaped SAR ADCs

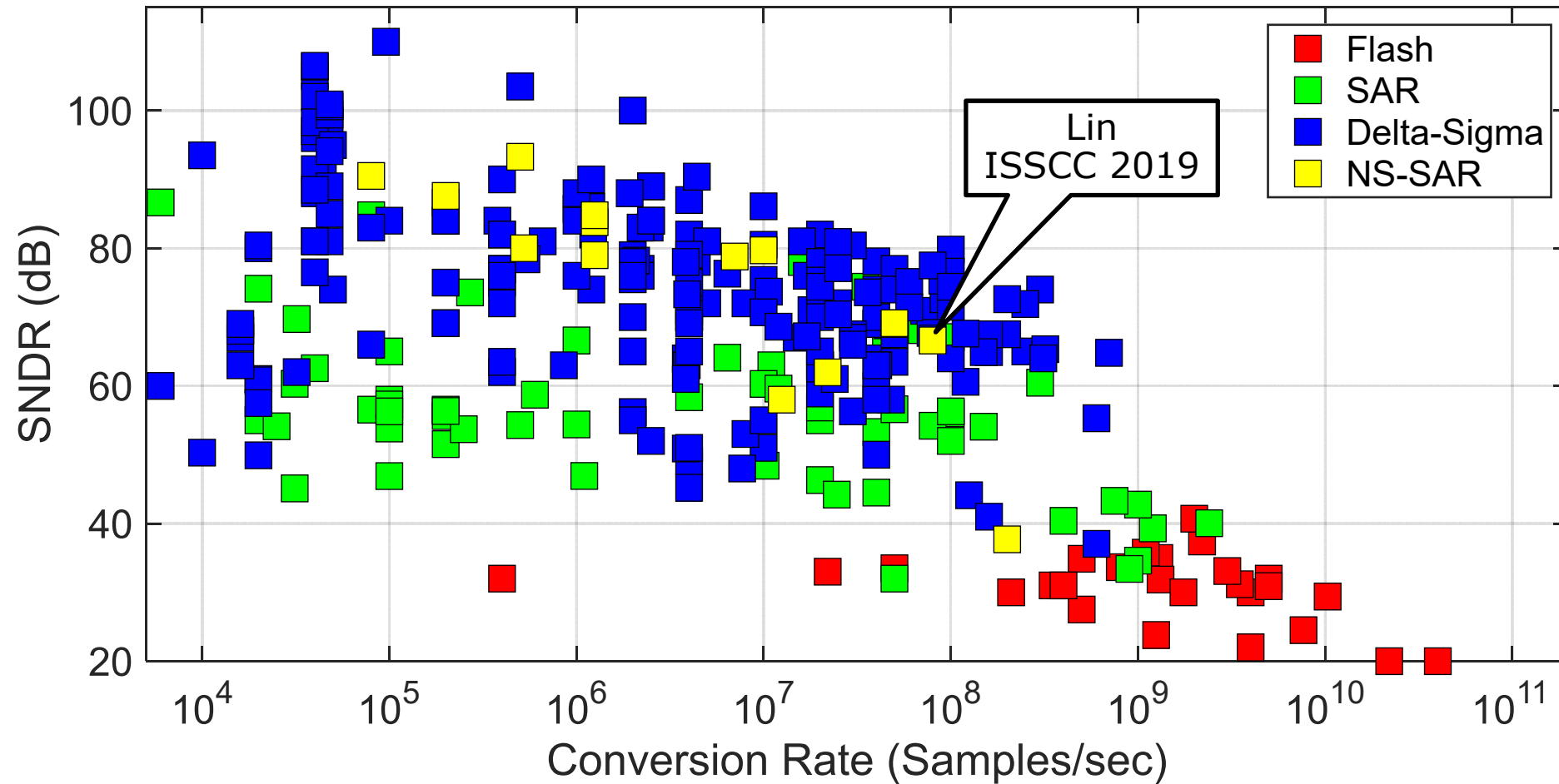

Higher Speed Through Pipelining





Ford assembly line in 1913
[Wikimedia Commons]

- ❑ Determine bits sequentially (as in a SAR ADC)
- ❑ But use concurrent “workers” (stages)
- ❑ Throughput set by one worker
- ❑ Latency set by number of workers


	Cycles per Conversion	Complexity
Flash	~ 1	$\sim 2^B$
Pipeline	~ 1	$\sim B$
SAR	$\sim B$	~ 1

From SAR to Pipeline (1)

  


- We can morph a SAR ADC into a pipeline by
 - Distributing the DAC across stages
 - Replicating the comparator in each stage
- Means that all known “calibration/correction tricks” apply to both topologies!

From SAR to Pipeline (2)

 

- Equivalent model with DAC broken up into its binary weights

From SAR to Pipeline (3)

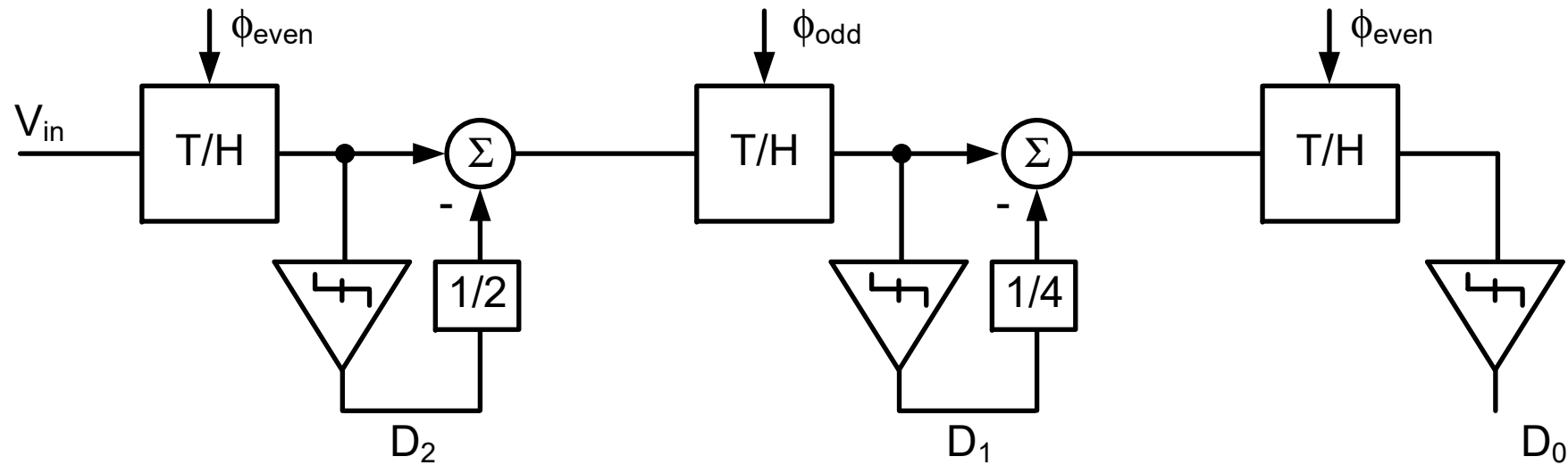

ϕ_{even} :

ACQUIRE

CONVERT

ACQUIRE


ϕ_{odd} :

CONVERT

ACQUIRE


CONVERT

From SAR to Pipeline (4)

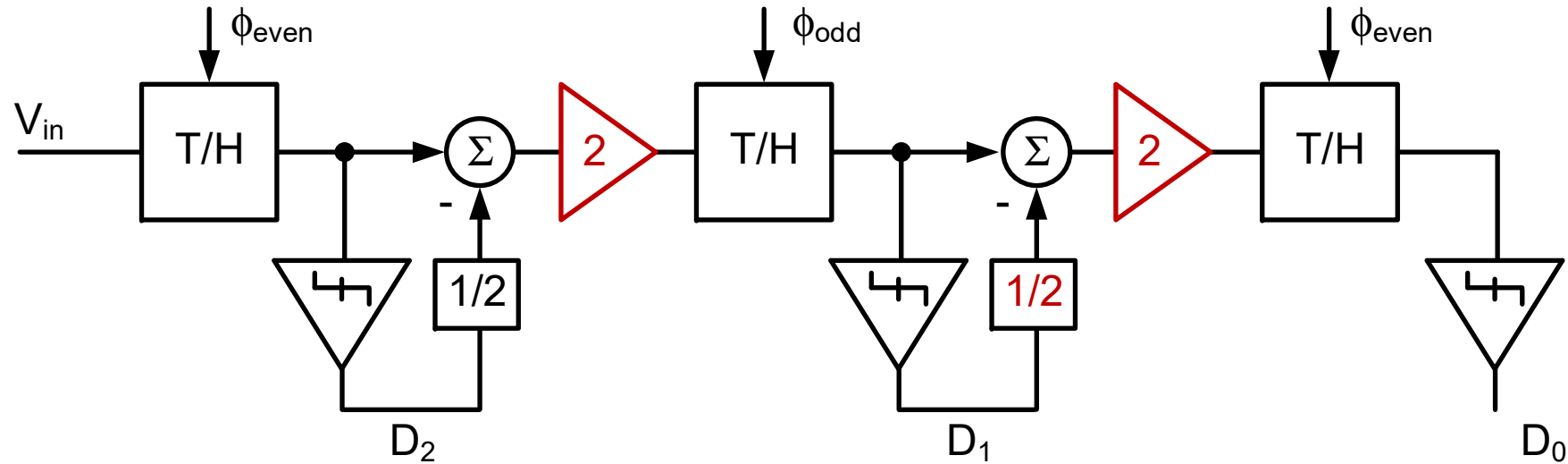


- Typically want to amplify residues back to full-scale to ease downstream circuit requirements

From SAR to Pipeline (5)

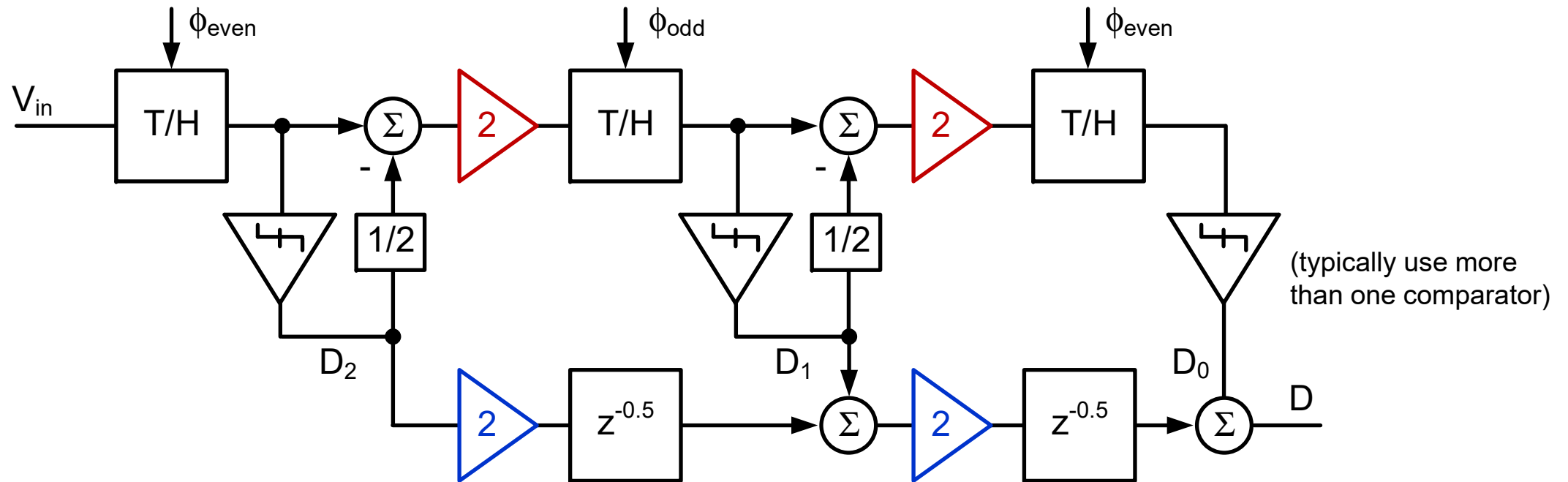


- ❑ Matching analog and digital front-end gains is a key issue
- ❑ Sometimes addressed through calibration

Pipelining SAR ADCs (!)

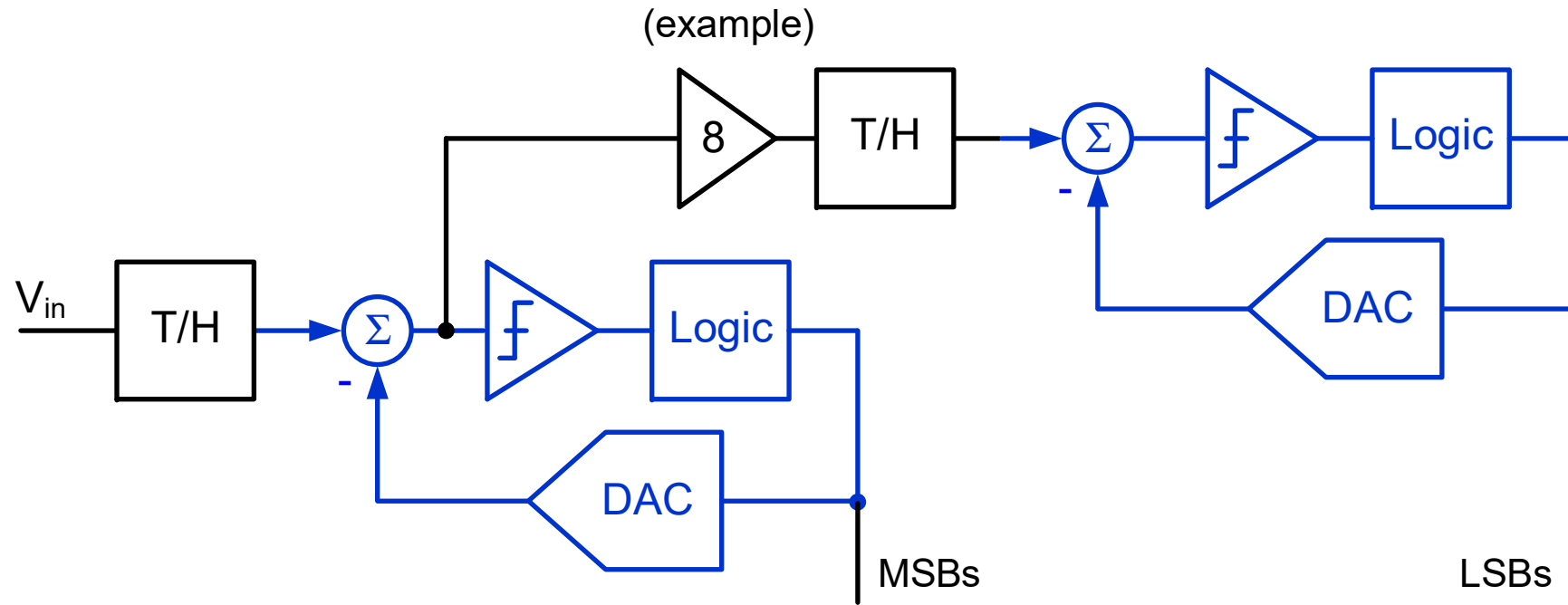


- Common to resolve more than one bit per stage in a pipeline
 - Conventionally this has been done using flash sub-ADCs
 - But SARs have become an attractive alternative
 - Can tap residue at comparator input


Published Data

 


Adding Pipelined ADCs

 


Adding "Other" Architectures

 

The Need for Time-Interleaving

 


Time Interleaving

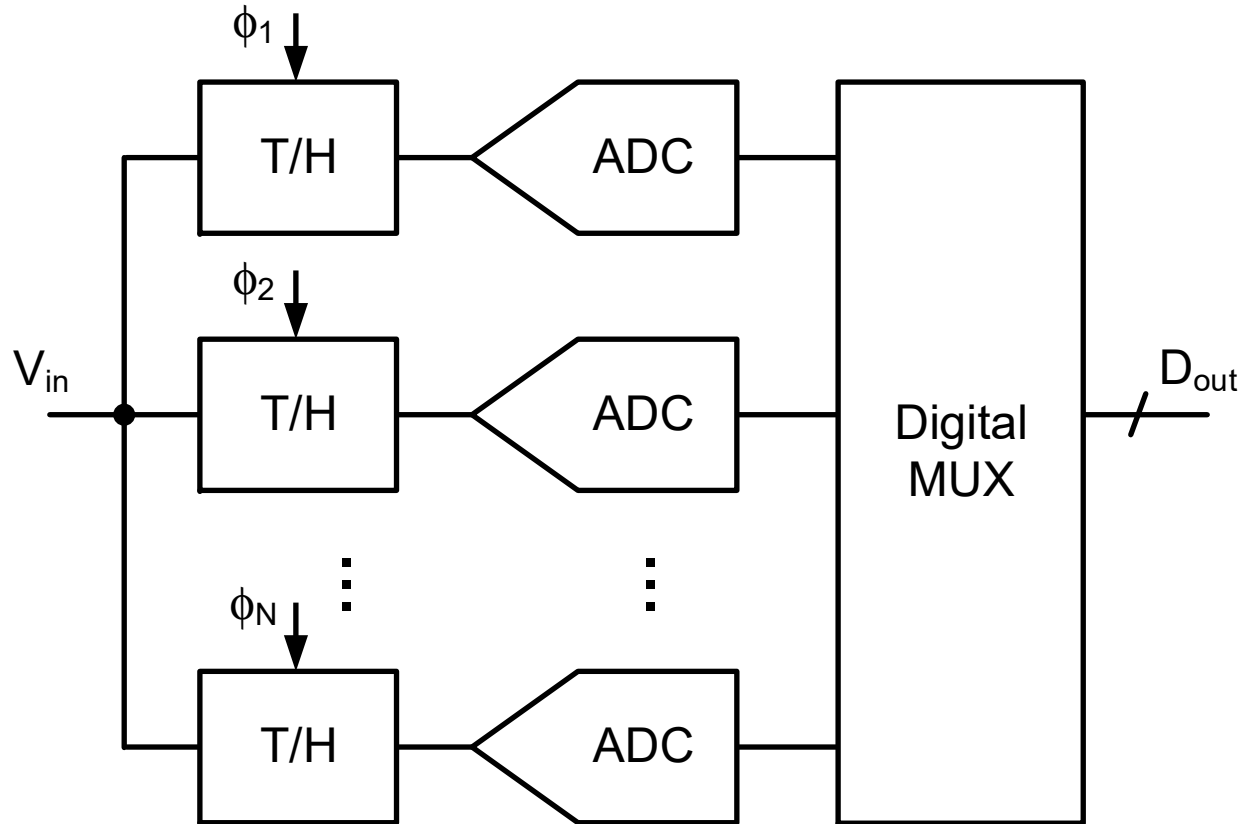


- N-fold increase in conversion rate
 - But each slice needs full acquisition bandwidth
- Sensitive to channel mismatches
 - Offset
 - Gain
 - Timing
 - Bandwidth
- Architectural variations
 - Global T/H
 - Hierarchical interleaving


Time-Interleaved ADCs

 

Application Driver Examples

 


Example: Biosensing SoC for Wearables

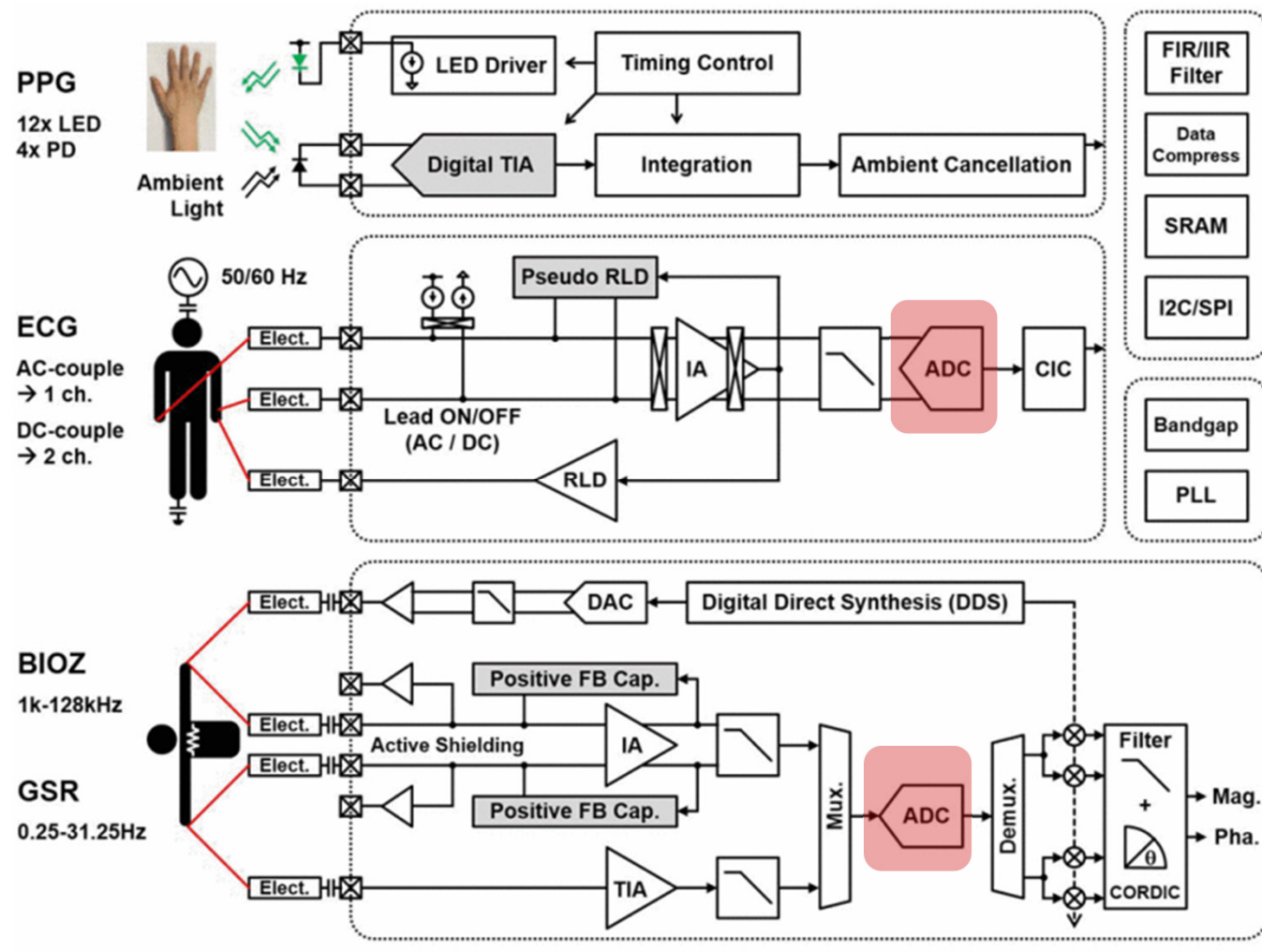

- Low to moderate speed
- Wide range of SNDR
- Low power is key

[Shu, ISSCC 2020]


Example: 5G RF and “Coax” ADCs

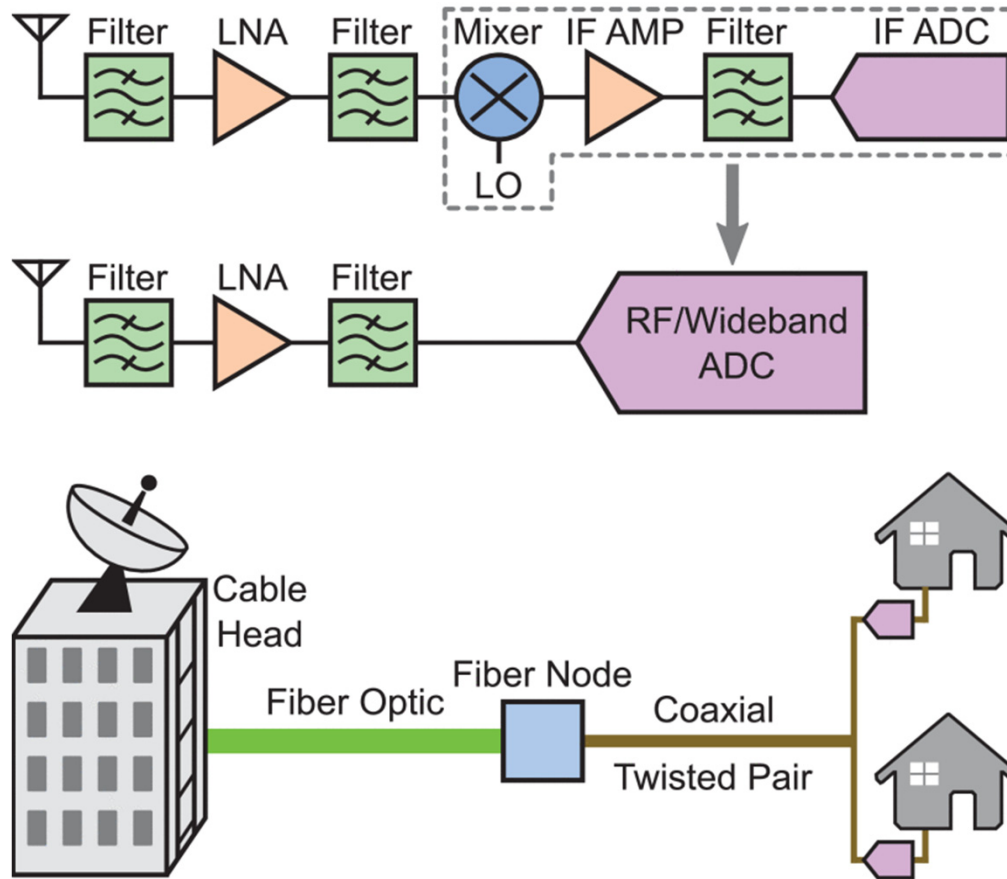

- 1-10 GS/s
- SNDR > 50...60 dB


[Ramkaj, ISSCC 2019]

Example: ADC-Based Wireline Transceiver

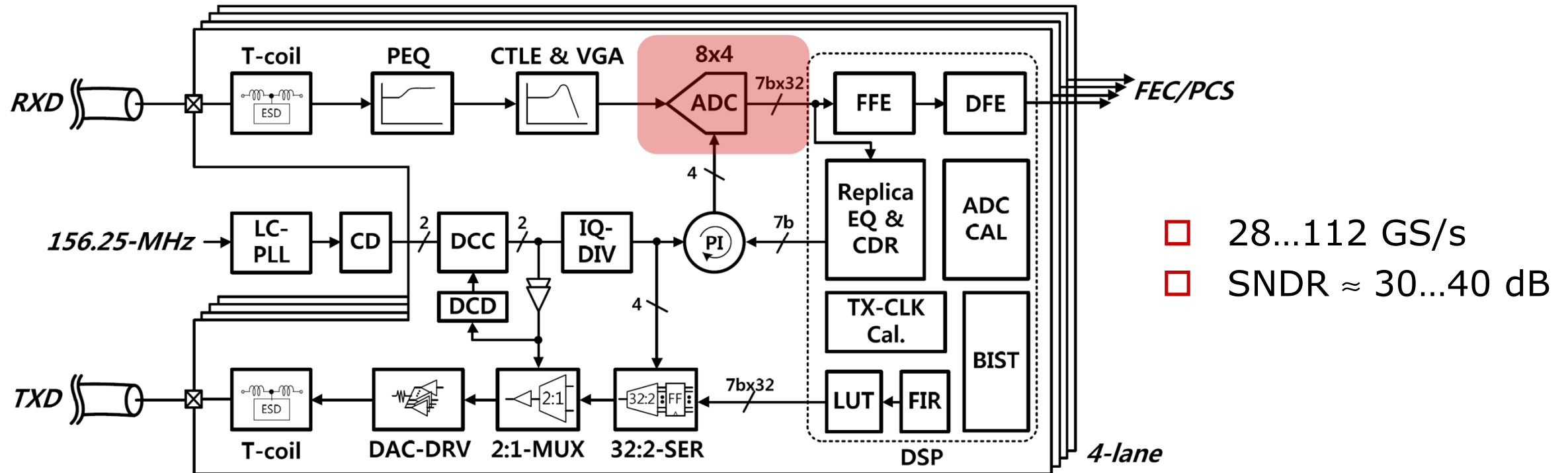


[Yoo, ISSCC 2020]


Speed-Resolution Frontier

 

Speed-Resolution & Process Node

 

Speed-Resolution Product over Time

 


□ See also [Murmann, 2016]

□ Step-like progress driven by application needs, investments?


Speed-Resolution Product Limiters

- Highly architecture and application dependent, but often related to
 - Device f_T
 - Input or drive impedance
 - Power constraints
 - Area constraints
 - Cost/ability to absorb output data
 - Input aperture
 - High-speed converters tend to process high-frequency inputs
 - Makes them sensitive to clock jitter
 - Metastability

Input Aperture

 

Sampling Jitter

 


$$\Delta V_{in} \approx \frac{dV_{in}}{dt} \Delta t$$

- SNR limit due to jitter follows from curvature of the signal's autocorrelation function [Da Dalt, 2002]

$$SNR_{jitter} = \frac{1}{\alpha_t \cdot \sigma_t^2} \quad \alpha_t = -\frac{R''(0)}{R(0)}$$

- Worst case is a single tone at HF (previous slide)
 - In this case $\alpha_t = \omega_{in}^2$
- Wideband or lowpass inputs are less affected
 - Uniform spectrum between 0 ... $\omega_{in} \rightarrow 4.8\text{dB}$
 - Wireline channel, 30 dB loss at $\omega_{in} \rightarrow \sim 10\text{dB}$

Jitter Frontier over Time

 


- Plot shows average of three best designs up to respective year
- Input is typically HF sinusoid near $f_s/2$
- Jitter estimated using

$$\sigma_t^2 \approx \frac{1}{\omega_{in,HF}^2 \cdot SNDR_{HF}}$$

- Role of test equipment?


Implications on VCO Power Consumption

 

- Plots is for a 10 GS/s ADC with m-dB SNR penalty due to jitter
- Input is a sinusoid at Nyquist

[Razavi, 2021]

Metastability

 


$$\tau \approx \frac{C_{gg} + C_L}{g_m} = \frac{k}{\omega_T}$$

In leading-edge technology:

$$\tau \approx \frac{3}{2\pi \cdot 150\text{GHz}} \approx 3\text{ps}$$

 - ❑ Comparators use cross-coupled pairs for fast exponential regeneration
- ❑ Small inputs (v_{od0}) lead to long decision times and potential metastability



$$\frac{t_{reg}}{\tau} = -\ln\left(\frac{v_{od0}}{V_{DD}}\right)$$



Metastability in a Flash ADC

- Smallest input that can be regenerated

$$v_{od0} = \frac{V_{DD}}{e^{T_s/2\tau}}$$


- Probability that a smaller input occurs for comparator at decision boundary
  
$$P_{meta} = \frac{v_{od0}}{\frac{\Delta}{2}} \approx \frac{v_{od0}}{\frac{1}{2} \frac{V_{DD}}{2^B}} = 2 \cdot 2^B e^{-T_s/2\tau}$$




- Difficult to go beyond 10 GS/s
→ Time interleaving

Metastability in an Asynchronous SAR ADC

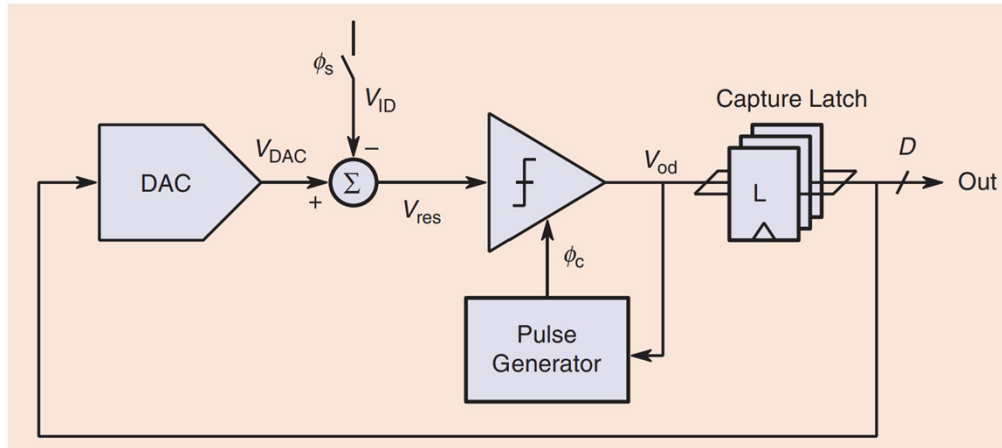

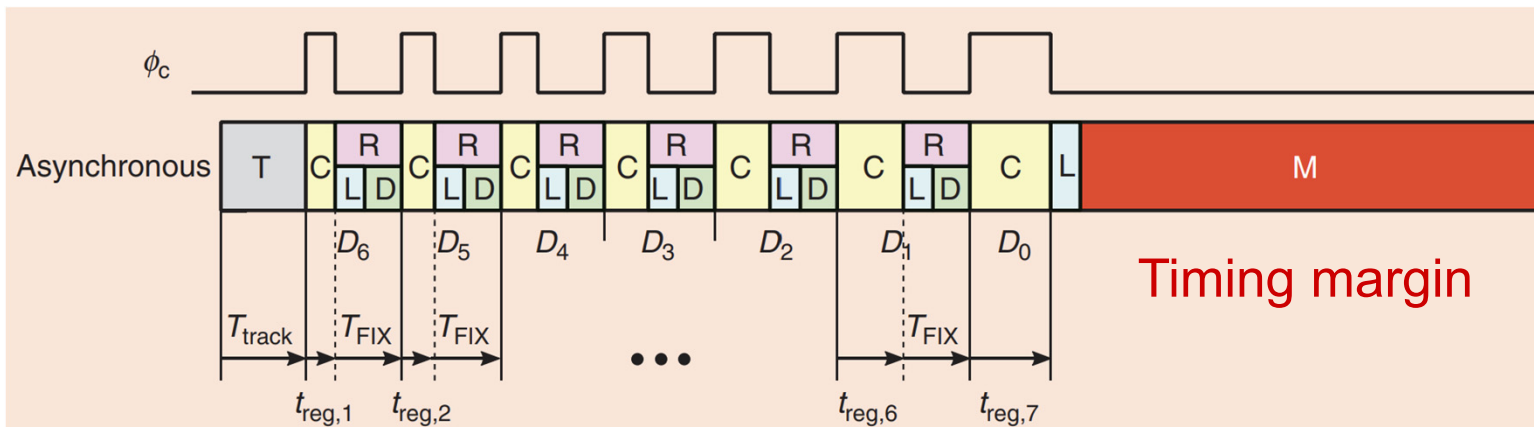- Key insight: Need only small timing margin to avoid large metastability errors
- MSBs can borrow time from LSBs
- Error is small when 1-2 LSBs are skipped




[Yu, 2019]


ADC Power Dissipation

- We have so far only looked at conversion rate and resolution, but power dissipation is equally (or often more) important
- To evaluate trends without complex 3D plots, we must agree on first-order dependencies between these metrics
- Straightforward for power and conversion rate
 - $\text{Power} = \text{Energy/Conversion} \times \text{Conversion Rate}$
- How does Energy/Conversion (P/f_s) scale with resolution (SNDR)?


Energy per Conversion (1997-2005)

 

Energy per Conversion (1997-2013)

 


Energy per Conversion (1997-2021)

 

Trend Toward Noise Limited Designs

 - Relentless optimization and technology scaling has resulted in mostly noise-limited designs above SNDR $\approx 50\text{dB}$
- Resulting slope coincides with tradeoffs in elementary ADC building blocks




$$SNR \propto \left(\frac{kT}{C}\right)^{-1} \quad f_s \propto \frac{g_m}{C} \quad P \propto I_D \propto \frac{g_m}{g_m/I_D} \propto \frac{g_m}{const.}$$

$$\boxed{\frac{P}{f_s} \propto kT \times SNR}$$

Energy increases 4x per 6 dB

ADC Figures of Merit

FoMs

 

Commonly Used FoMs

□ Walden FoM [Walden, 1999]

- 2x per bit

$$FoM_W = \frac{P}{f_s \cdot 2^{ENOB}}$$

□ Schreier FoM (DR) [Schreier, 2005]

- 4x per bit
- Ignores distortion


$$FoM_{S,DR} = DR + 10\log\left(\frac{BW}{P}\right)$$

□ Schreier FoM (SNDR) [Ali, 2010]


- 4x per bit
- Includes distortion
- Typically use SNDR for near-Nyquist input

$$FoM_S = SNDR + 10\log\left(\frac{f_s/2}{P}\right)$$

Example FoM Lines

 


FoM_S vs. Conversion Rate

 

FoM_S Roll-Off

- Transistors become less efficient at high speed
 - Required transistor $f_T \uparrow \rightarrow g_m/I_D \downarrow$
 - Assumption of linear power scaling with f_s in FoM_S equation falls apart
- Many high-speed designs tend to lie in the “technology limited” region
 - Assumption of 4x power scaling per 6 dB in FoM_S does not apply
- Other factors include overhead due to interleaving, low-jitter clocking, ...
- **Generally (independent of FoM choice), limit comparisons to designs with similar speeds and resolution!**

Low-Frequency FoM_S over Time

 


$$P/f_s = 8kT \times SNR$$


~Practical limit (?)

- $8kT \times SNR$ limit corresponds to rail-to-rail class-B circuits [Vittoz, 1990]
- Difficult to surpass!


FoM_S vs. Conversion Rate & Process Node

 

FoM_S for SAR-Based Converters

 

How Do You Like Your SAR ADCs Served?

 

- ☐ Plain?
- ☐ Noise-shaped?
- ☐ Pipelined?
- ☐ Interleaved?
- ☐ Pipelined & interleaved?

Outline


□ ADCs

- Metrics
- Architectures
- Speed, resolution, energy tradeoffs and trends
- Building block considerations
- Application aspects

□ DACs


- Output spectrum & metrics
- Introduction to current steering
- Timing and jitter requirements
- Performance trends
- Application aspects

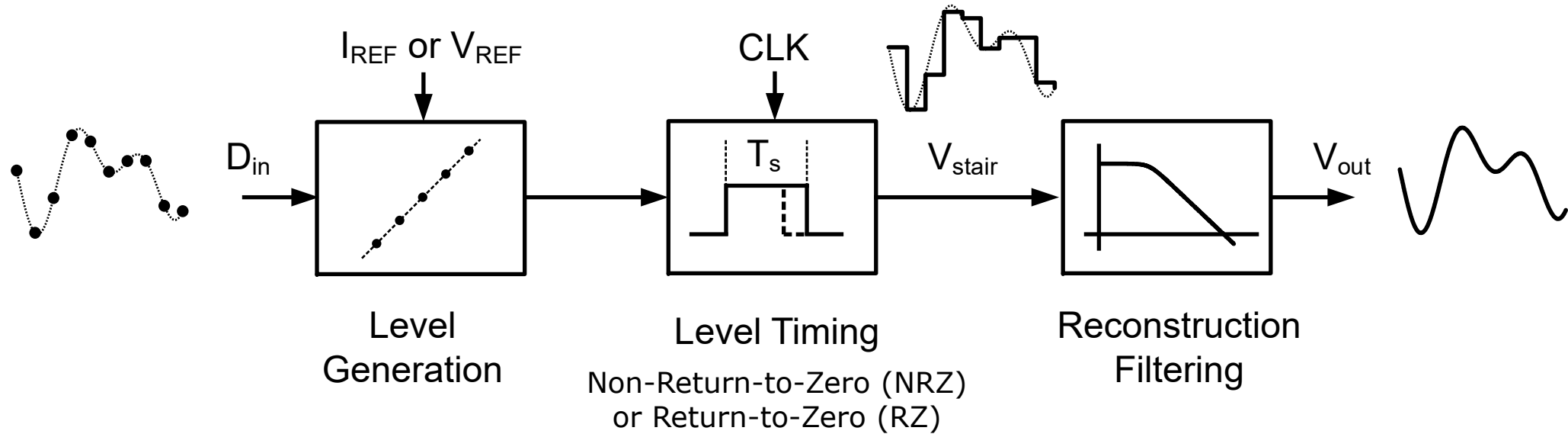Conceptual View of a Nyquist D/A Interface




- Two challenges
 - Accurate mapping of digital input to analog levels
 - Accurate timing of level transitions

Spectral Images For NRZ Output

 



[Kester, 2005]

Oversampling Reduces Filter Requirements

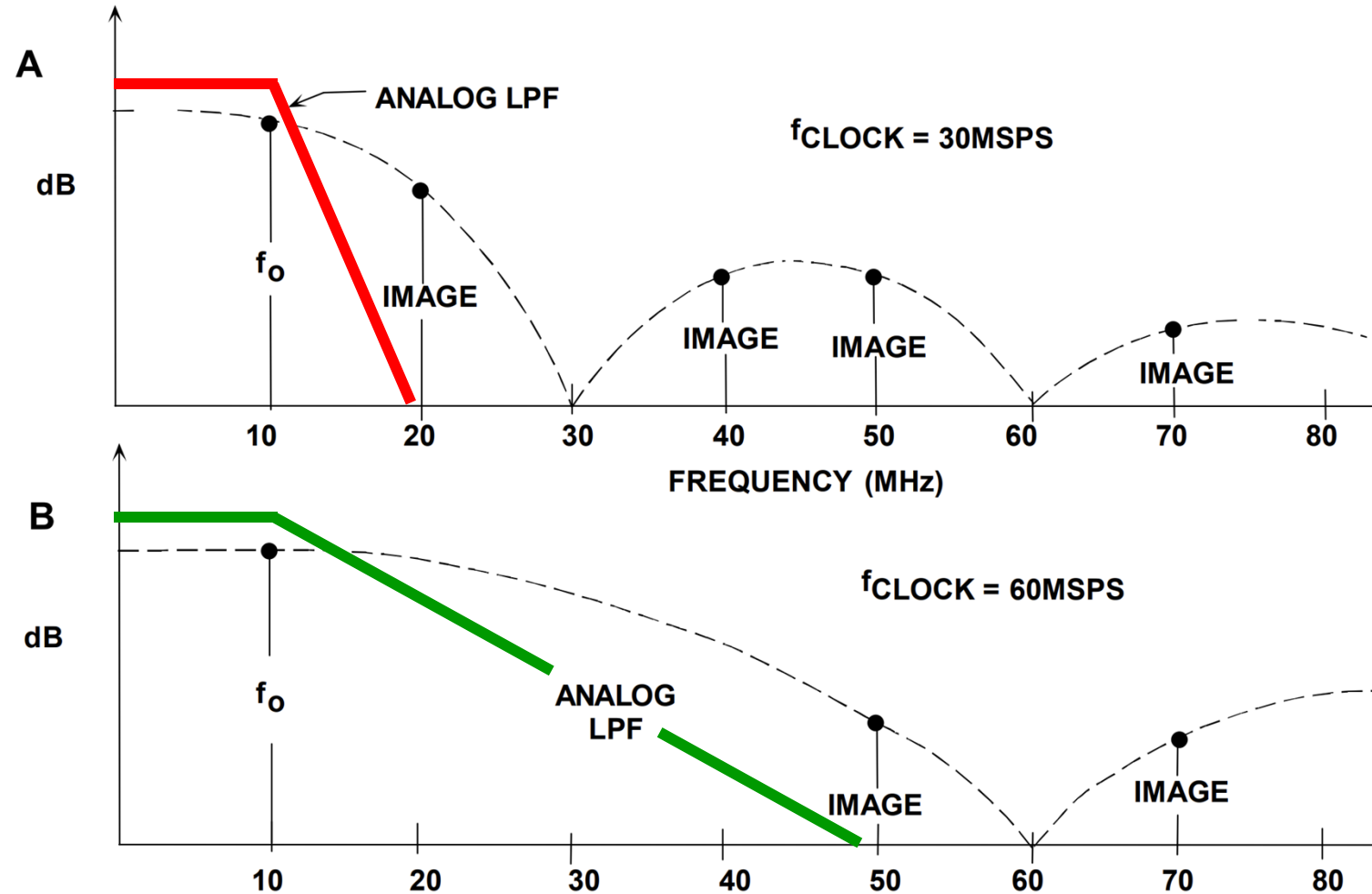

[Kester, 2005]

Current Steering Architecture

 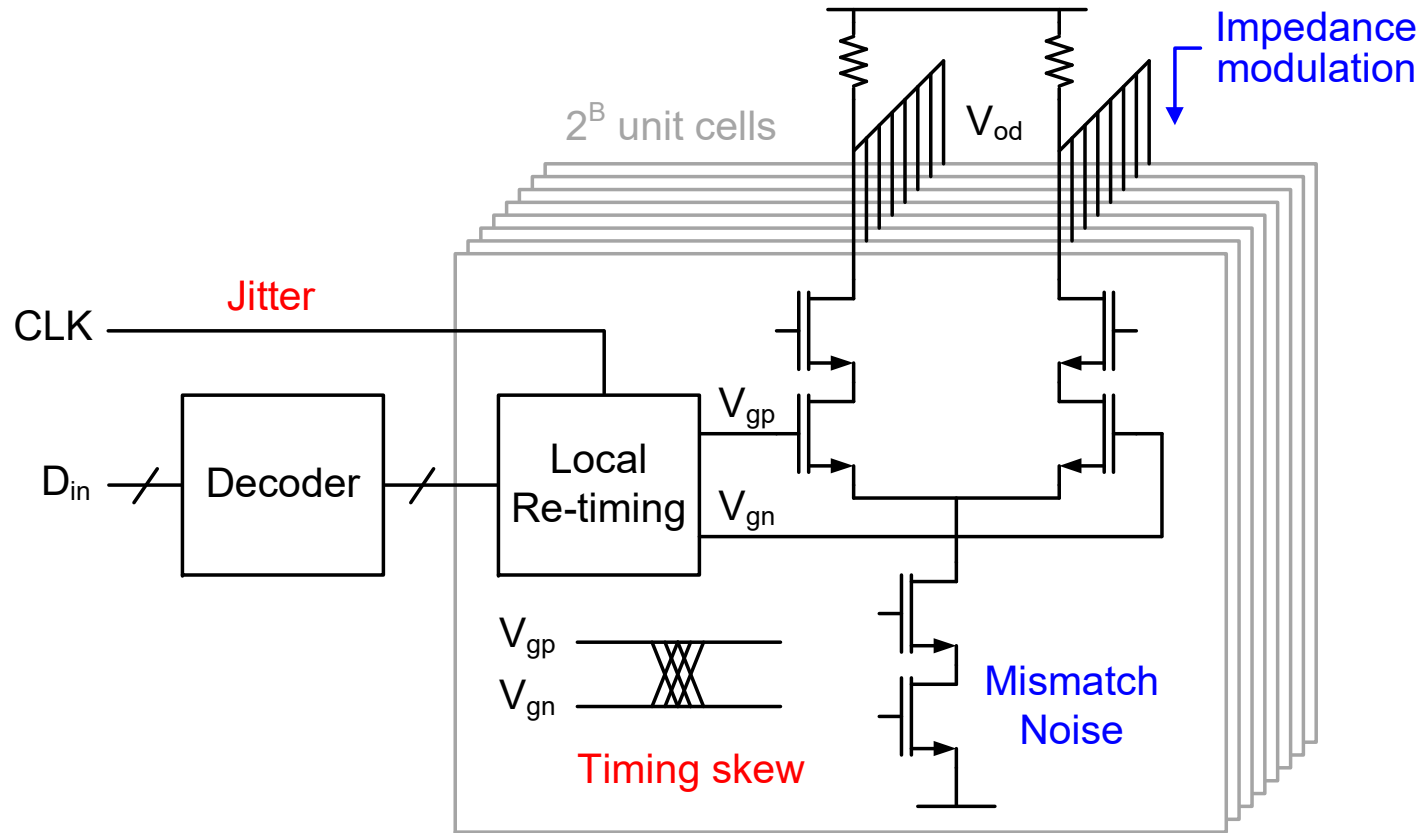


[Lin, ISSCC 2018]


- Unit cell grouping has significant effect on achievable performance

Binary Grouping

 - ❑ No decoder needed, but MSB transition is a major issue
- ❑ Consider 4-bit example below
 - Turn off 7, turn on 8 to go from 7 to 8
 - Both amplitude and timing errors are a significant problem



Timing Glitch for Binary Grouping

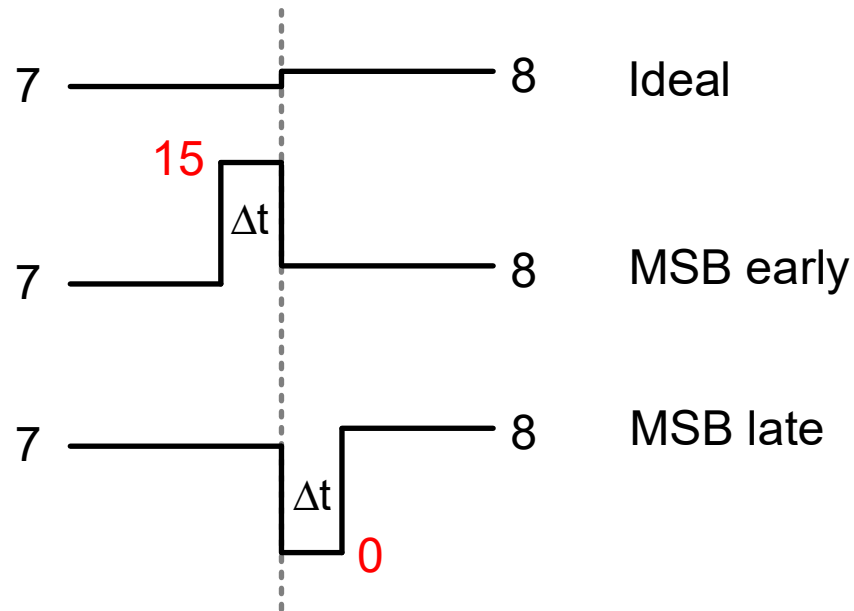

For single-tone input, can show


$$SFDR \geq \frac{3 T_s}{2 \Delta t}$$

Update Rate (f_s)	SFDR Target	Tolerable skew (Δt)
1 GS/s	60 dB	1.5 ps
10 GS/s	60 dB	150 fs
64 GS/s	40 dB	230 fs

- ❑ Skew requirements not manageable in practice
- ❑ Hence, most high-speed DACs use other grouping strategies

Alternative Grouping Strategies

 - ❑ No grouping (“thermometer DAC”) is typically impractical
 - Large decoder, too many wires
- ❑ Typically look for golden middle: LSBs binary, MSBs thermometer encoded
 - More in Gabriele Manganaro’s presentation




<p> 1.1 Introduction 1.2 Background 1.3 Objectives 1.4 Scope 1.5 Methodology 1.6 Results 1.7 Conclusion 1.8 References 1.9 Appendix 1.10 Index 1.11 Glossary 1.12 Abbreviations 1.13 Acronyms 1.14 Footnotes 1.15 Endnotes 1.16 References 1.17 Appendix 1.18 Index 1.19 Glossary 1.20 Abbreviations 1.21 Acronyms 1.22 Footnotes 1.23 Endnotes 1.24 References 1.25 Appendix 1.26 Index 1.27 Glossary 1.28 Abbreviations 1.29 Acronyms 1.30 Footnotes 1.31 Endnotes 1.32 References 1.33 Appendix 1.34 Index 1.35 Glossary 1.36 Abbreviations 1.37 Acronyms 1.38 Footnotes 1.39 Endnotes 1.40 References 1.41 Appendix 1.42 Index 1.43 Glossary 1.44 Abbreviations 1.45 Acronyms 1.46 Footnotes 1.47 Endnotes 1.48 References 1.49 Appendix 1.50 Index 1.51 Glossary 1.52 Abbreviations 1.53 Acronyms 1.54 Footnotes 1.55 Endnotes 1.56 References 1.57 Appendix 1.58 Index 1.59 Glossary 1.60 Abbreviations 1.61 Acronyms 1.62 Footnotes 1.63 Endnotes 1.64 References 1.65 Appendix 1.66 Index 1.67 Glossary 1.68 Abbreviations 1.69 Acronyms 1.70 Footnotes 1.71 Endnotes 1.72 References 1.73 Appendix 1.74 Index 1.75 Glossary 1.76 Abbreviations 1.77 Acronyms 1.78 Footnotes 1.79 Endnotes 1.80 References 1.81 Appendix 1.82 Index 1.83 Glossary 1.84 Abbreviations 1.85 Acronyms 1.86 Footnotes 1.87 Endnotes 1.88 References 1.89 Appendix 1.90 Index 1.91 Glossary 1.92 Abbreviations 1.93 Acronyms 1.94 Footnotes 1.95 Endnotes 1.96 References 1.97 Appendix 1.98 Index 1.99 Glossary 1.100 Abbreviations 1.101 Acronyms 1.102 Footnotes 1.103 Endnotes 1.104 References 1.105 Appendix 1.106 Index 1.107 Glossary 1.108 Abbreviations 1.109 Acronyms 1.110 Footnotes 1.111 Endnotes 1.112 References 1.113 Appendix 1.114 Index 1.115 Glossary 1.116 Abbreviations 1.117 Acronyms 1.118 Footnotes 1.119 Endnotes 1.120 References 1.121 Appendix 1.122 Index 1.123 Glossary 1.124 Abbreviations 1.125 Acronyms 1.126 Footnotes 1.127 Endnotes 1.128 References 1.129 Appendix 1.130 Index 1.131 Glossary 1.132 Abbreviations 1.133 Acronyms 1.134 Footnotes 1.135 Endnotes 1.136 References 1.137 Appendix 1.138 Index 1.139 Glossary 1.140 Abbreviations 1.141 Acronyms 1.142 Footnotes 1.143 Endnotes 1.144 References 1.145 Appendix 1.146 Index 1.147 Glossary 1.148 Abbreviations 1.149 Acronyms 1.150 Footnotes 1.151 Endnotes 1.152 References 1.153 Appendix 1.154 Index 1.155 Glossary 1.156 Abbreviations 1.157 Acronyms 1.158 Footnotes 1.159 Endnotes 1.160 References 1.161 Appendix 1.162 Index 1.163 Glossary 1.164 Abbreviations 1.165 Acronyms 1.166 Footnotes 1.167 Endnotes 1.168 References 1.169 Appendix 1.170 Index 1.171 Glossary 1.172 Abbreviations 1.173 Acronyms 1.174 Footnotes 1.175 Endnotes 1.176 References 1.177 Appendix 1.178 Index 1.179 Glossary 1.180 Abbreviations 1.181 Acronyms 1.182 Footnotes 1.183 Endnotes 1.184 References 1.185 Appendix 1.186 Index 1.187 Glossary 1.188 Abbreviations 1.189 Acronyms 1.190 Footnotes 1.191 Endnotes 1.192 References 1.193 Appendix 1.194 Index 1.195 Glossary 1.196 Abbreviations 1.197 Acronyms 1.198 Footnotes 1.199 Endnotes 1.200 References</</p>
--

© 2022 IEEE Introduction to ADCs/DACs 78 of 93



Error Spectrum

 

[Kurosawa, 2002]

- ❑ Spurious components lie outside first Nyquist zone
- ❑ In-band SNR (between $0 \dots f_s/2$) follows from same equation as ADC sampling jitter

$$SNR_{jitter} \approx \frac{1}{\omega_{sig}^2 \sigma_t^2}$$

- ❑ Example
 - $f_{sig} = 5 \text{ GHz}$, $\sigma_t = 100 \text{ fs}$
 - $SNR_{jitter} = 50 \text{ dB}$


Application Classes and Specs

- Traditional precision and baseband applications
 - Static errors like offset, DNL, INL
 - THD, SFDR

- RF DACs
 - Noise spectral density (NSD)
 - Intermodulation distortion (IM3, also called IMD or IMD3)
 - SFDR impairments are out of band (reduced by equipment & DAC's finite BW)



- DAC-based wireline transmitters
 - Eye diagram quality metrics (random jitter, etc.)
 - In-band SNDR

Heterodyning versus Direct RF Synthesis

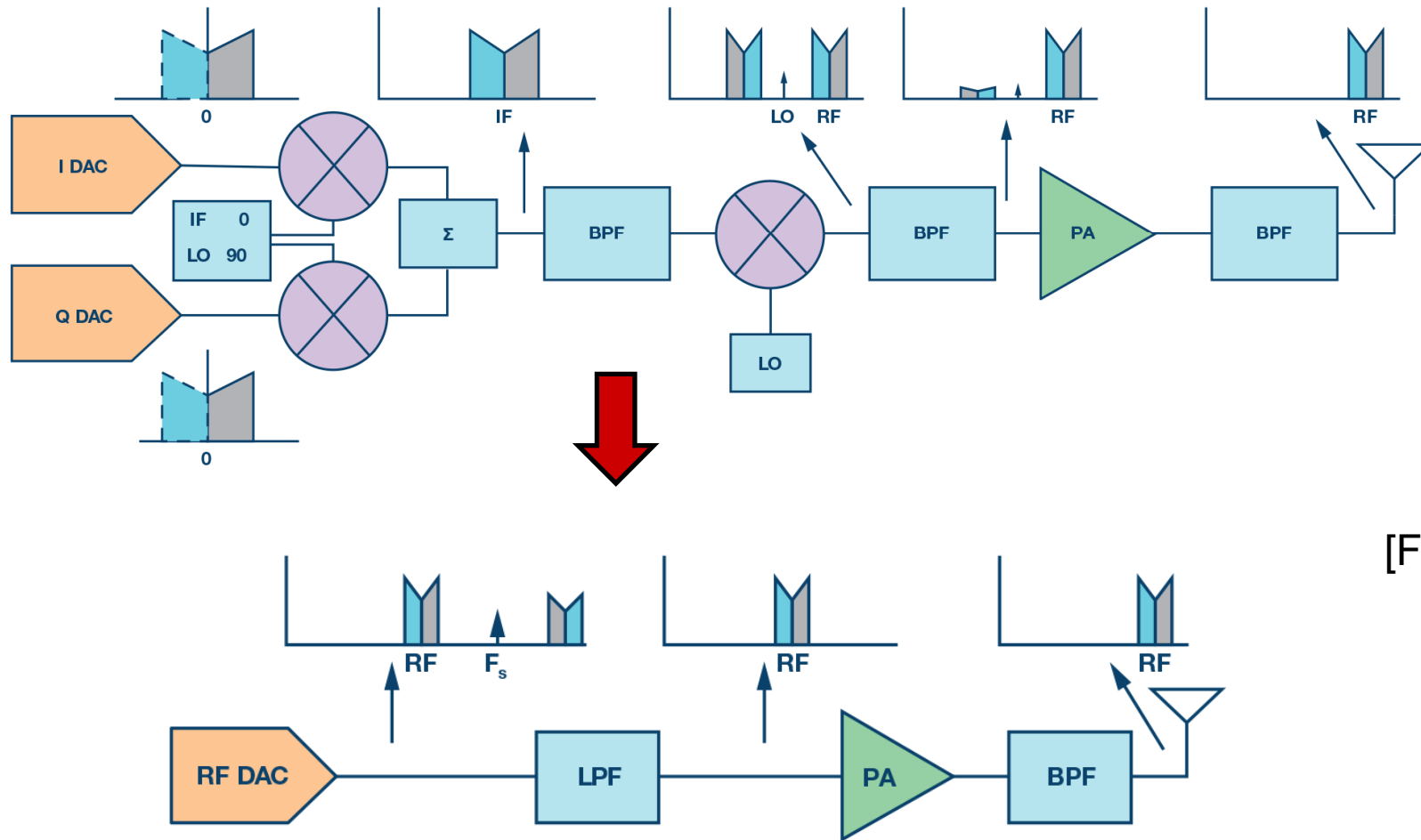

[Fague, 2016], [Engel 2012]

State-of-the-Art RF DAC

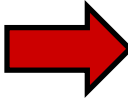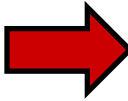


Process node	nm	16
Resolution	b	16
Sampling Rate	GS/s	6
Supply	V	1.0/3.0
Full Scale	mA	40
Area	mm ²	0.52
Power	mW	350
IMD@1.9GHz	dBc	-91
IMD@3.9GHz	dBc	-80
SFDR@0.4GHz	GHz	88
SFDR@2GHz	dBc	74
NSD@250MHz FS=3.5dBm	dBm/Hz	-165 (DEM=0) -162 (DEM=1)
NSD@2.6GHz FS= -3.7dBm	dBm/Hz	-162 (DEM=0) -159 (DEM=1)

[Lin, ISSCC 2018]

- IMD set by
 - Unit element matching
 - Segmentation scheme
 - Calibration and dynamic element matching (DEM) schemes

- NSD set by
 - Thermal noise
 - Jitter
 - Quantization noise (small for 16b)
 - DNL noise, DEM noise

Thermal NSD

 

$$\overline{v_o^2} = 4kTR(1 + g_m R) = 4kTR \left(1 + \frac{g_m}{I_D} I_D R \right)$$



$$NSD_{th} = -174 \frac{dBm}{Hz} + 10 \log \left(\frac{g_m}{I_D} I_D R \right)$$

Example: $\frac{g_m}{I_D} I_D R = 10 \frac{S}{A} \times 10mA \times 50\Omega = 5$

$$\Rightarrow NSD_{th} = -167 \frac{dBm}{Hz} = -170.5 \frac{dBFS}{Hz} @FS=3.5 \text{ dBm}$$

Measured NSD

Thermal
limit

  


Jitter NSD

$$SNR_{jitter} \approx \frac{1}{\omega_{sig}^2 \sigma_t^2} = \frac{1}{(2\pi \times 2GHz \times 50fs)^2} = 64dB$$

$$NSD_{jitter} \approx P_{sig} - SNR_{jitter} - 10 \log\left(\frac{f_s}{2}\right)$$


$$NSD_{jitter} \approx P_{sig} - 64dB - 10 \log\left(\frac{6GHz}{2}\right)$$

$$NSD_{jitter} \approx -159 dBFS/Hz$$

 


□ Very difficult to improve this DAC further!

DAC Performance Survey

 


Possible Explanation for 40dB/dec Roll-Off?


Time varying impedance

 


[Clara, 2013], [van den Bosch, 1999]

 

DAC Technology Landscape

 

DAC Area

 


CS DAC Area Scaling?


Greshishchev
BCICTS 2019

Greshishchev
ISSCC 2011

	This Work	[5]	[6]	[4]
Technology	7nm	14nm	20nm	65nm
Sampling Rate (GS/s)	60	56	64	56
Resolution	8b	8b	8b	6b
SINAD (dB)	29.5	n/a	n/a	27.7
Full Scale Output	800 mVppd	920 mVppd	700 mVppd	600mVppd
Switch	CML	SST	CML	CML
Supply Voltage (V)	0.9 + 1.9	0.95	1 + 1.8	1.1 + 2.5
Power Consumption	560 mW (Memory included)	286 mW	620 mW	750 mW

 

65nm \rightarrow 0.24 mm²

 

7nm \rightarrow 0.31 mm²

Some Take-Aways

- Symbiotic interplay between technology push and application pull has led to remarkable performance gains in data converters
- Today's data converters operate close to practical limits
 - Low-speed ADCs: $8kT \times \text{SNR}$ energy limit
 - High-speed ADCs and DACs: Tens of femtoseconds timing jitter
- Architecture trends
 - ADCs: Going hybrid & dominance of SAR-based architectures
 - DACs: Current steering dominates, but some alternatives emerging
- Application trends
 - RF ADCs and DACs
 - Ultra-high-speed wireline ADCs and DACs

Selected References (1)

- ❑ Xilinx, Understanding Key Parameters for RF-Sampling Data Converters, 2019
https://www.xilinx.com/support/documentation/white_papers/wp509-rfsampling-data-converters.pdf
- ❑ B. Murmann, "ADC Performance Survey 1997-2021," [Online]. Available:
<http://web.stanford.edu/~murmman/adcsurvey.html>
- ❑ D. Robertson, "Problems and Solutions: How Applications Drive Data Converters (and How Changing Data Converter Technology Influences System Architecture)," SSCS Magazine, 2015
- ❑ B. Murmann, "The successive approximation register ADC: a versatile building block for ultra-low-power to ultra-high-speed applications," IEEE Comm. Magazine, Apr. 2016
- ❑ N. Da Dalt et al., "On the jitter requirements of the sampling clock for analog-to-digital converters," IEEE TCAS1, pp. 1354-1360, Sep. 2002
- ❑ B. Razavi, "Jitter-Power Trade-Offs in PLLs", Circuits and Systems I: Regular Papers IEEE Transactions on, vol. 68, no. 4, pp. 1381-1387, 2021
- ❑ A. Yu et al. "Understanding Metastability in SAR ADCs: Part II: Asynchronous," SSCS Magazine, Summer 2019
- ❑ R. H. Walden, "Analog-to-digital converter survey and analysis," IEEE J. Select. Areas in Communication, Apr. 1999
- ❑ R. Schreier and G. C. Temes, Understanding Delta-Sigma Data Converters, Wiley, 2005

Selected References (2)

- ❑ A.M.A. Ali, et al., "A 16-bit 250-MS/s IF Sampling Pipelined ADC With Background Calibration," JSSC, Dec. 2010
- ❑ E. A. Vittoz, "Future of analog in the VLSI environment," Proc. ISCAS, 1990
- ❑ W. Kester, The Data Conversion Handbook, Analog Devices, 2004
- ❑ Kurosawa, "Sampling clock jitter effects in digital-to-analog converters," Elsevier Measurement, vol. 31, 2002
- ❑ S. Kim, et al., "Modeling Random Clock Jitter Effect of High-Speed Current-Steering NRZ and RZ DAC," TCAS I, Sep. 2018
- ❑ D.E. Fague, New RF DAC Broadens Software-Defined Radio Horizon, Analog Dialog, Jul. 2016
<https://www.analog.com/en/analog-dialogue/articles/new-rf-dac-broadens-sdr-horizon.html>
- ❑ G. Engel et al., "RF digital-to-analog converters enable direct synthesis of communications signals," IEEE Communications Magazine, Oct. 2012
- ❑ P. Caragiulo, C. Daigle, B. Murmann, "DAC Performance Survey 1996-2020," [Online]. Available:
<https://github.com/pietro-caragiulo/survey-DAC>
- ❑ M. Clara, "Dynamic linearity" in High-Performance D/A-Converters, Springer, 2013
- ❑ A. van den Bosch et al., "SFDR-bandwidth limitations for high-speed high resolution current steering CMOS D/A converters," ICECS 1999